

Analog Electronics Circuits

18EI31

SRIDEVI N

ASSOCIATE PROFESSOR


DEPT. OF EIE

DR AIT

A solid green horizontal bar spanning the width of the slide at the bottom.


Kirchhoff's Voltage Law

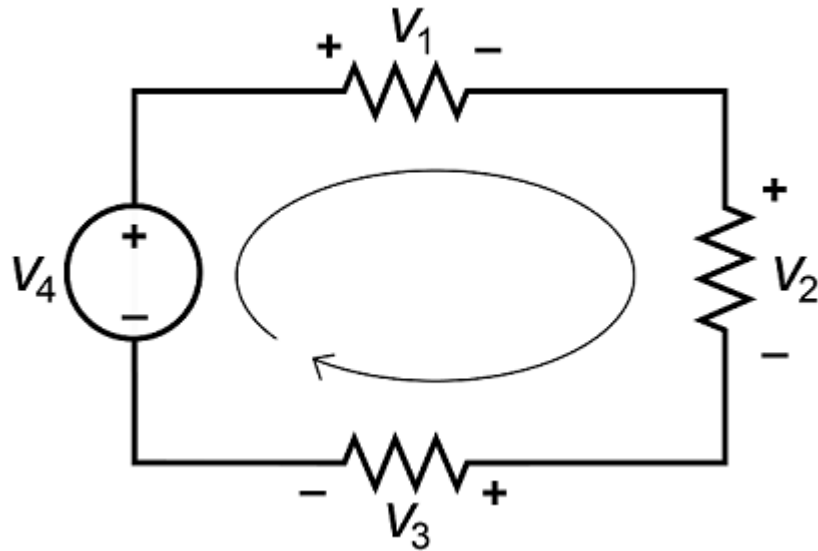The algebraic sum of all the voltages around any closed loop in a circuit is equal to zero




$$-V_1 - V_2 + V_3 + V_4 = 0$$

Continued..

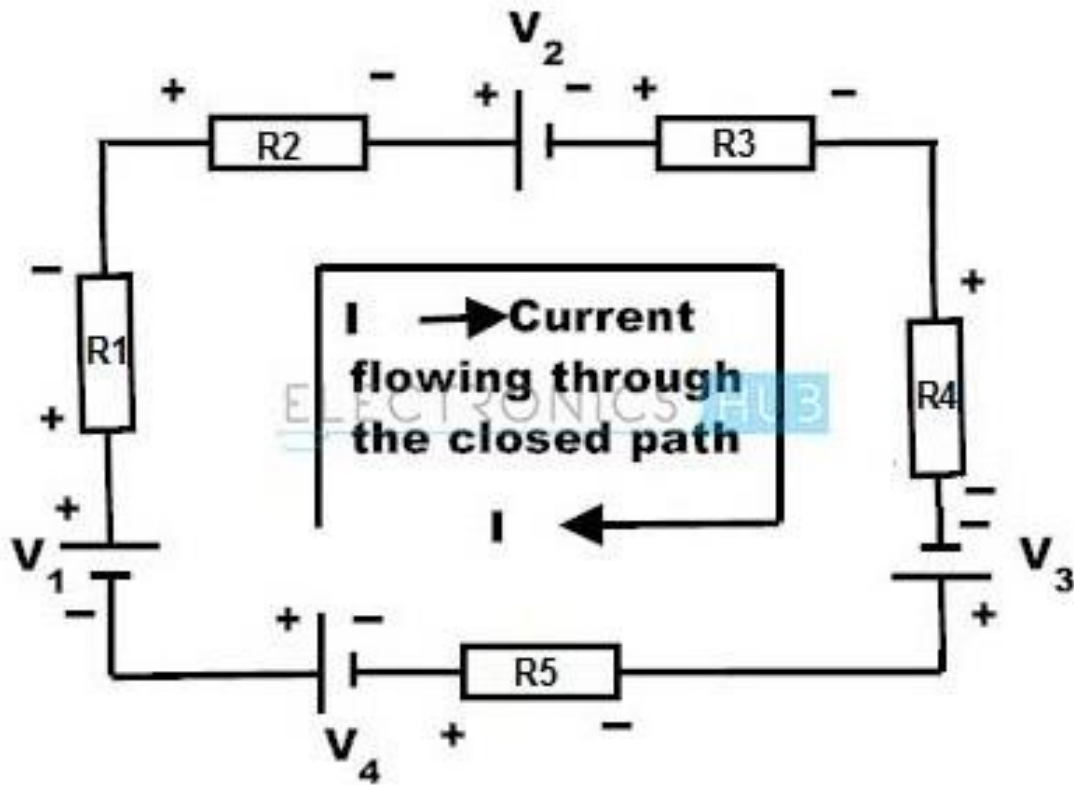

$$V_1 - IR_1 - IR_2 - V_2 - IR_3 - IR_4 + V_3 + IR_5 + V_4 = 0$$

Continued..

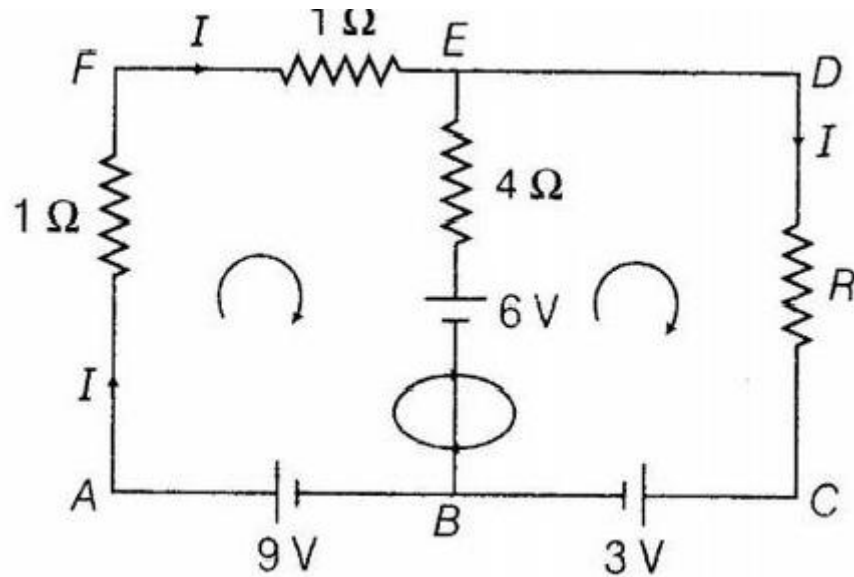


Applying Kirchhoff's 2nd law in mesh *AFDCA*

$$-1 \times I - 1 \times I - I \times R - 3 + 9 = 0$$

$$-2I - IR + 6 = 0$$

$$2I + IR = 6$$

Continued..

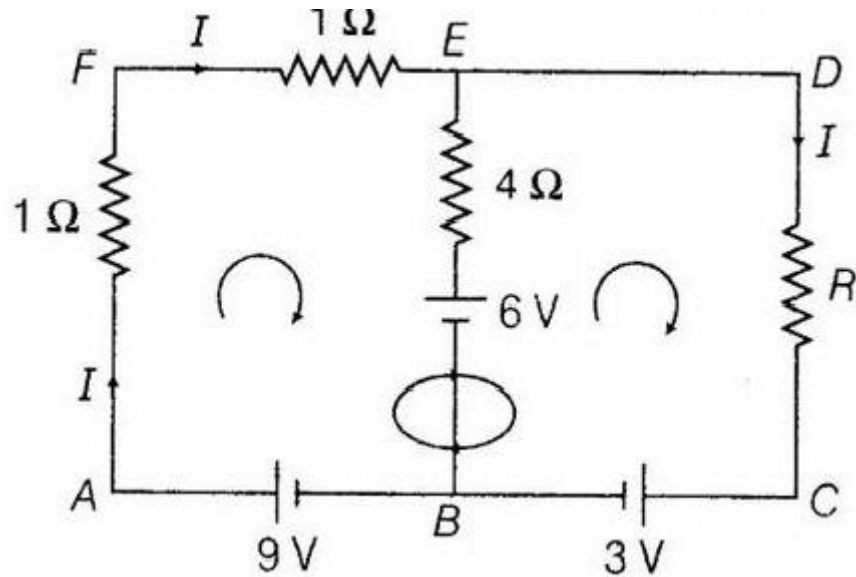

Applying Kirchhoff's second law in mesh AFEBA

$$-1 \times I - 1 \times I - 6 + 9 = 0$$


$$-2I + 3 = 0$$

$$I = \frac{3}{2} \text{ A}$$


Kirchhoff's Current Law

The total current entering a circuits junction is exactly equal to the total current leaving the same junction.

A Single Junction

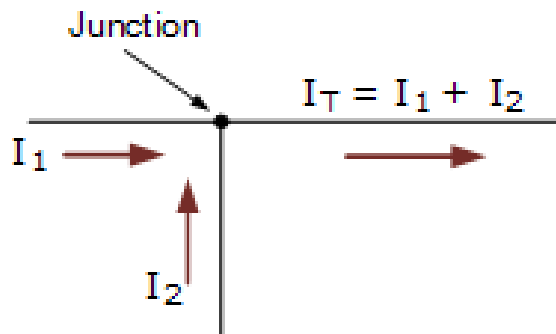


Continued..

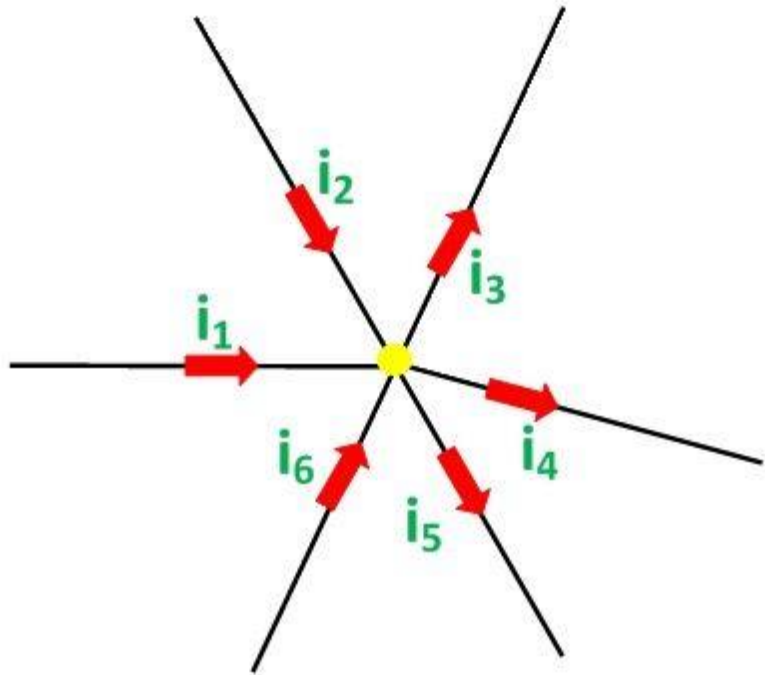

Circuit Globe

$$i_1 + i_2 - i_3 - i_4 - i_5 + i_6 = 0$$


Continued..

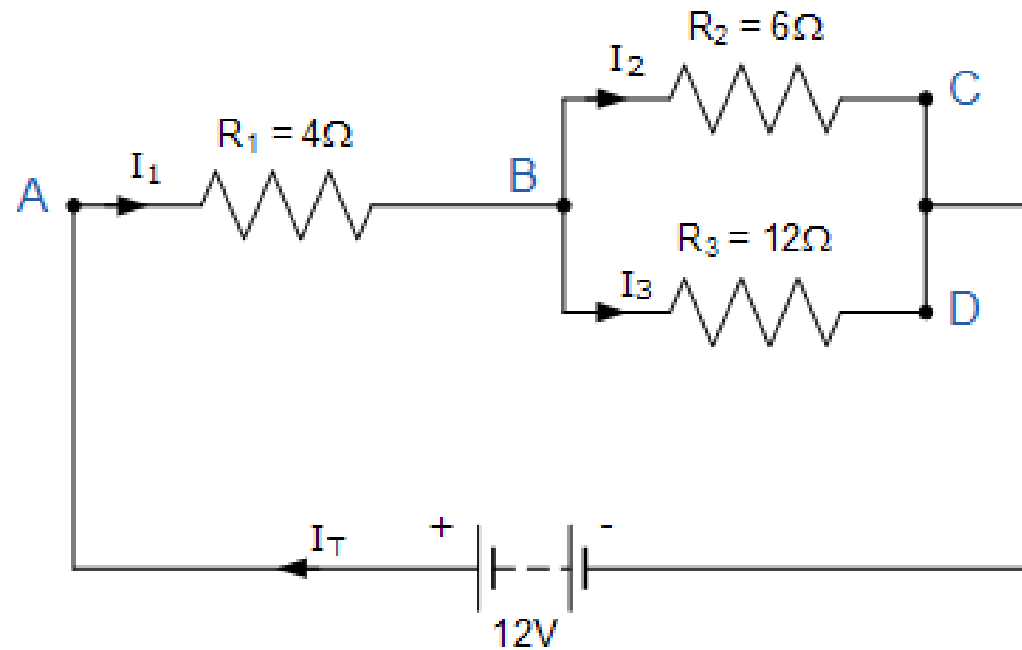

$$\text{Loop ABC} \Rightarrow 12 = 4I_1 + 6I_2$$


$$\text{Loop ABD} \Rightarrow 12 = 4I_1 + 12I_3$$

Voltage Divider Rule

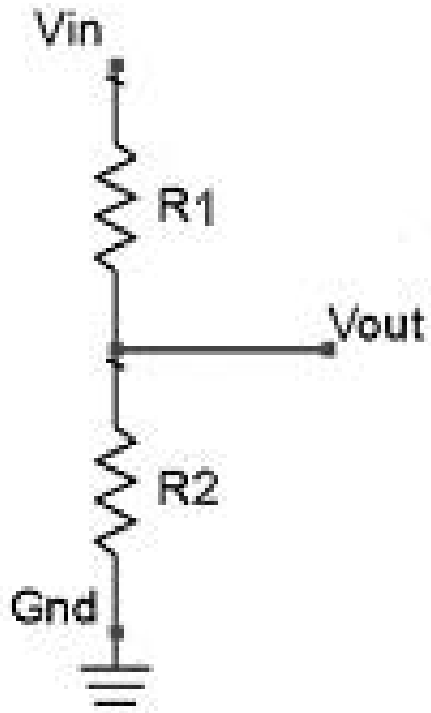

$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

Continued..

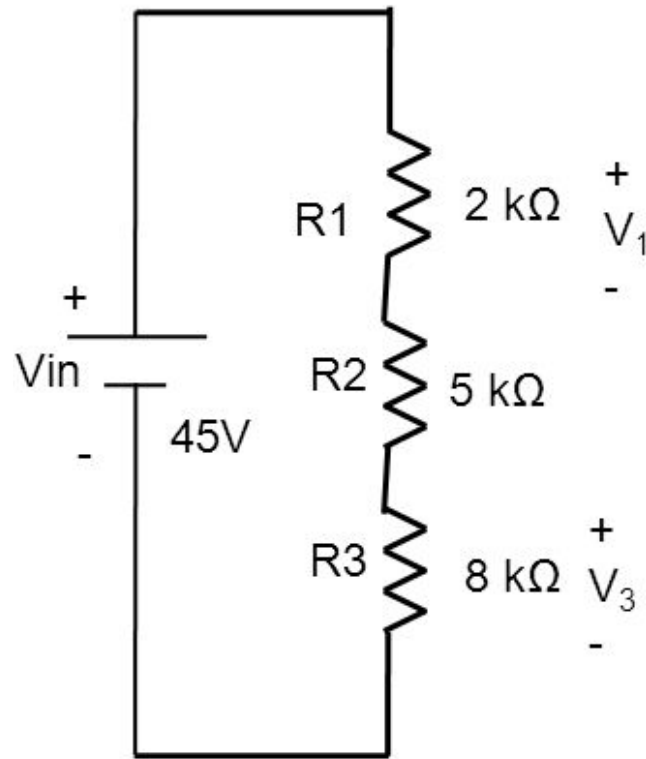

$$V_1 = \frac{R_1 V_{in}}{R_T}$$

$$\frac{(2k\Omega)(45V)}{2k\Omega + 5k\Omega + 8k\Omega} = \frac{(2k\Omega)(45V)}{15k\Omega}$$


$= 6V$

$$V_3 = \frac{R_3 V_{in}}{R_T}$$

$$= 24V$$


Ideal Diode

Forward Biased

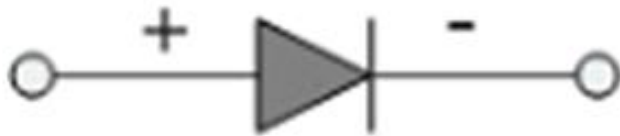

Forward Bias
(switch closed)



Reversed Biased

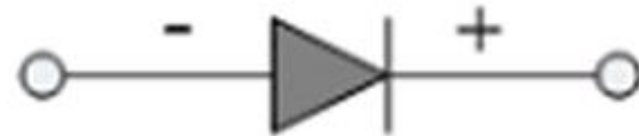


Reverse Bias
(switch open)

Silicon Diode

Forward Biased

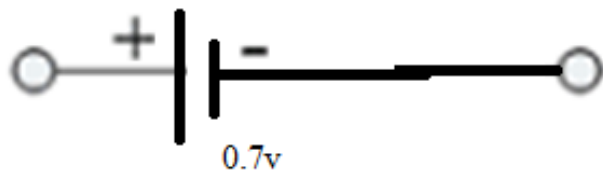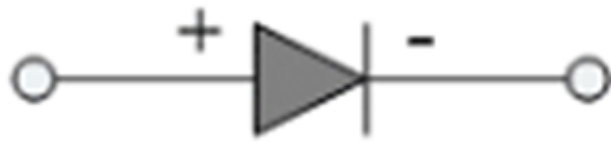



Reversed Biased

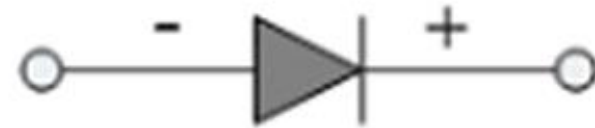


Reverse Bias
(switch open)

Forward Bias

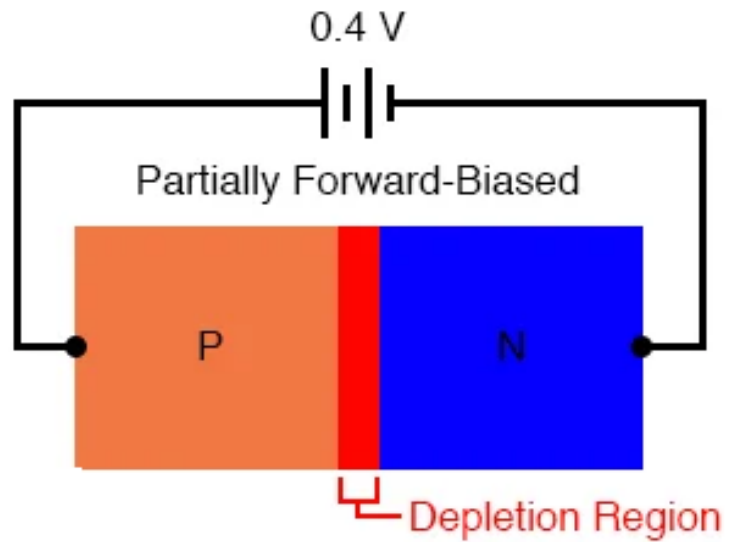

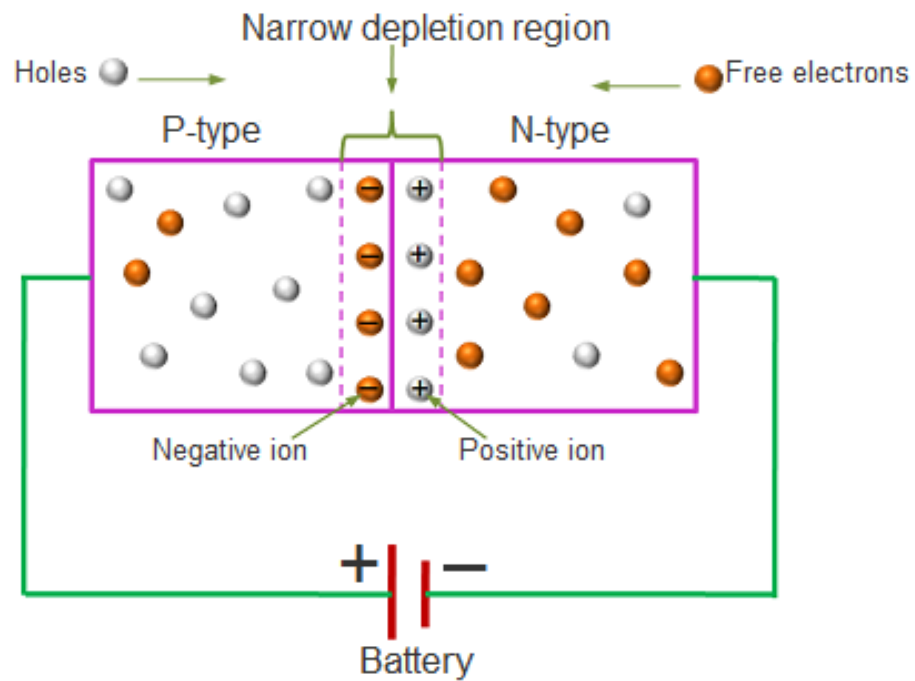


Forward bias

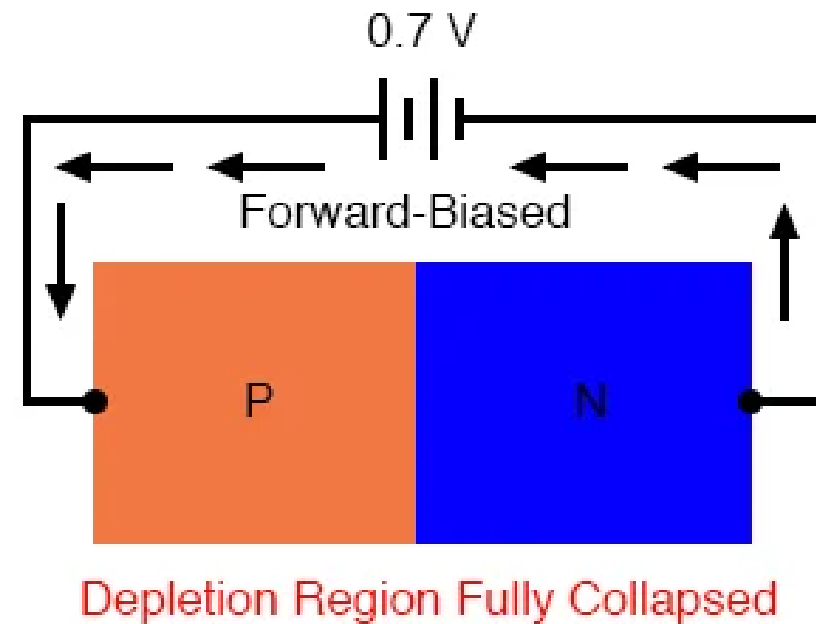

Copyright © Physics and Radio-Electronics, All rights reserved


Reverse Bias

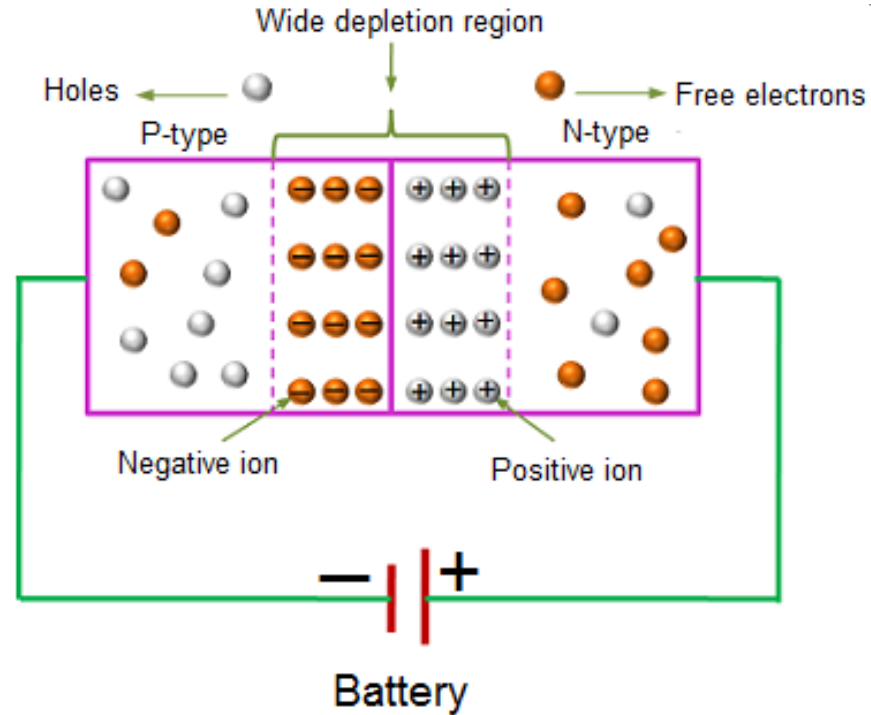




Reverse bias

Copyright © Physics and Radio-Electronics, All rights reserved


Characteristics

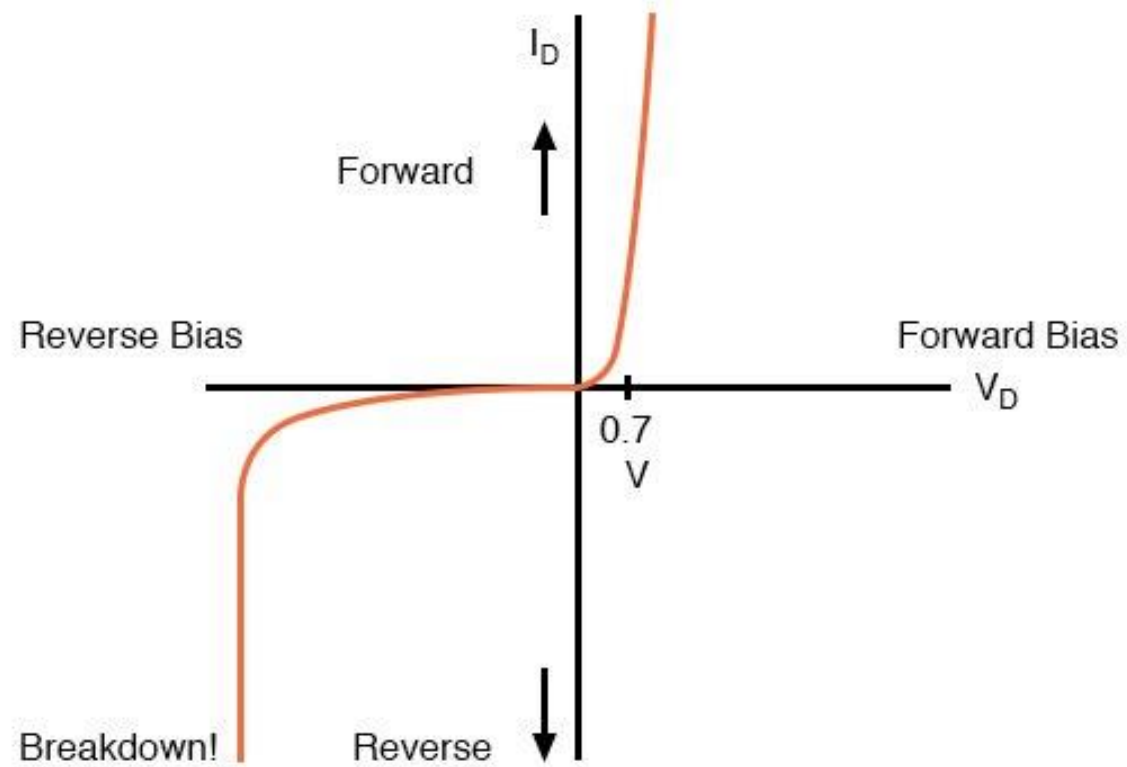


Reverse Bias

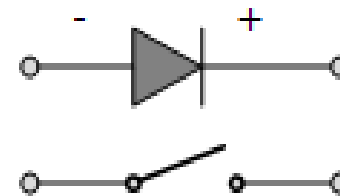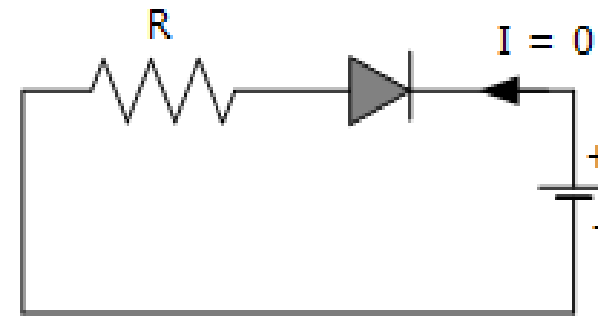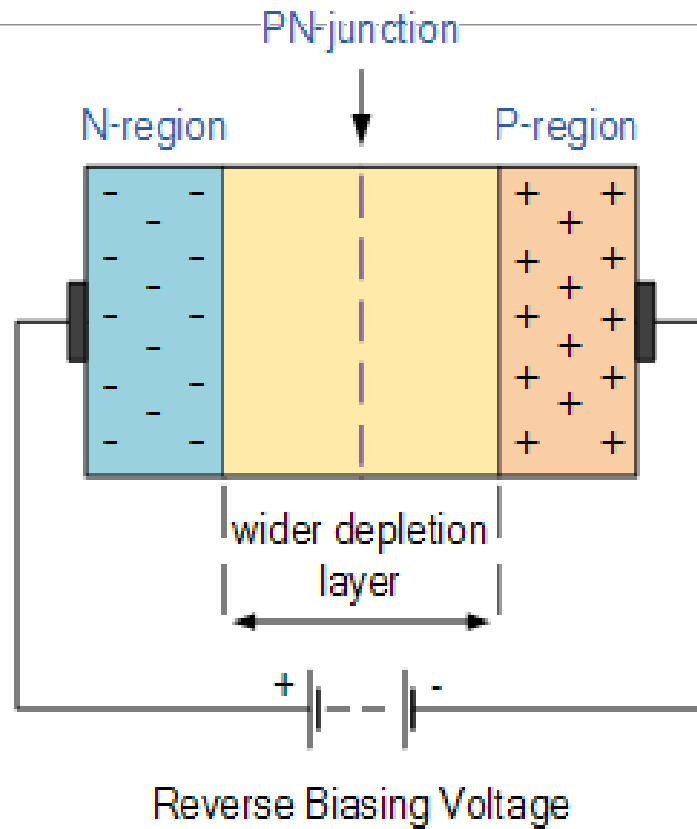

Reverse Biased Forward Biased

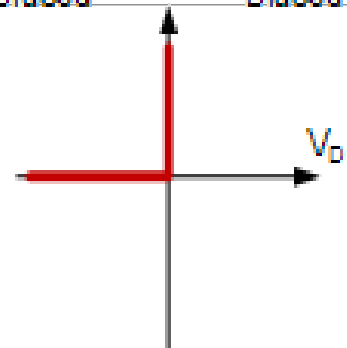

Ideal Diode

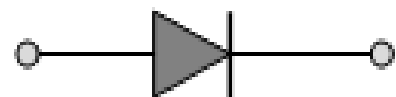


Forward Biased




Reverse Biased

Reverse Biased Forward Biased

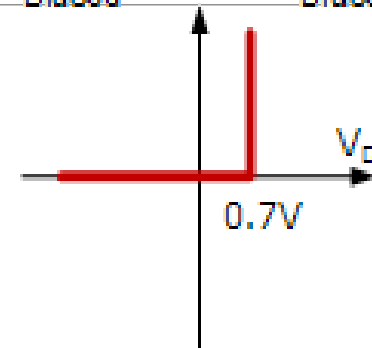

Real Diode


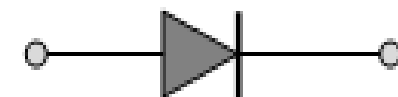


Forward Biased







Reverse Biased



Example

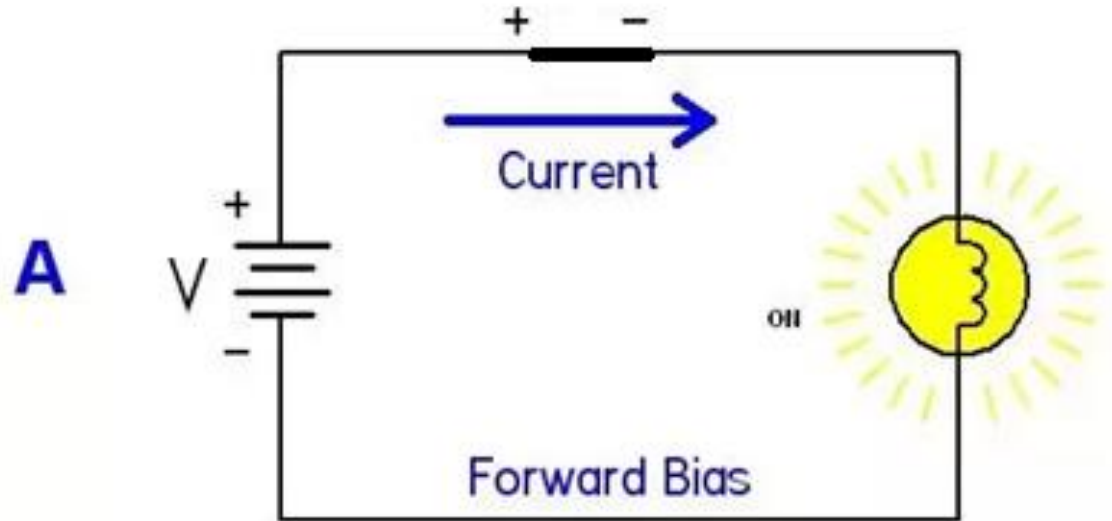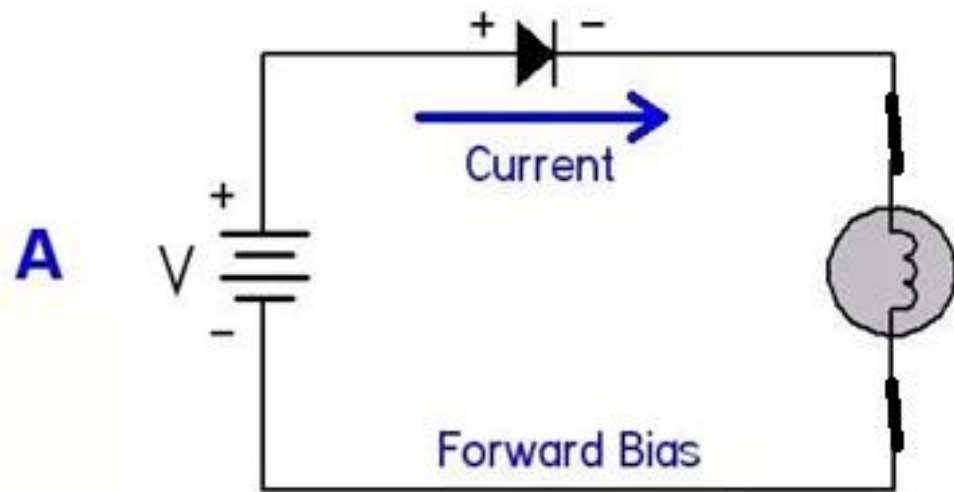

Example

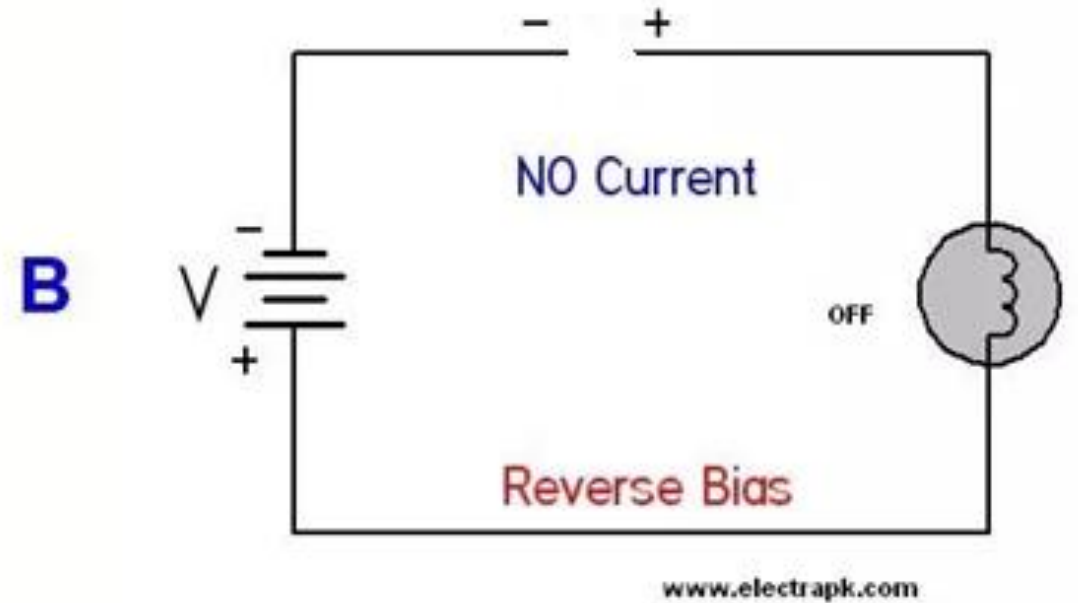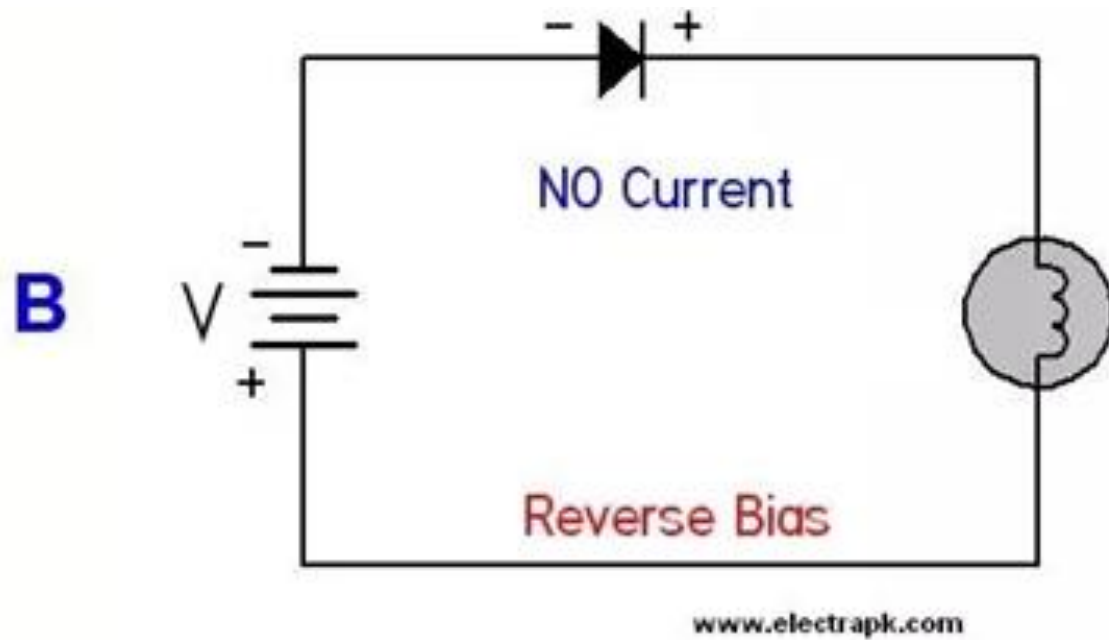

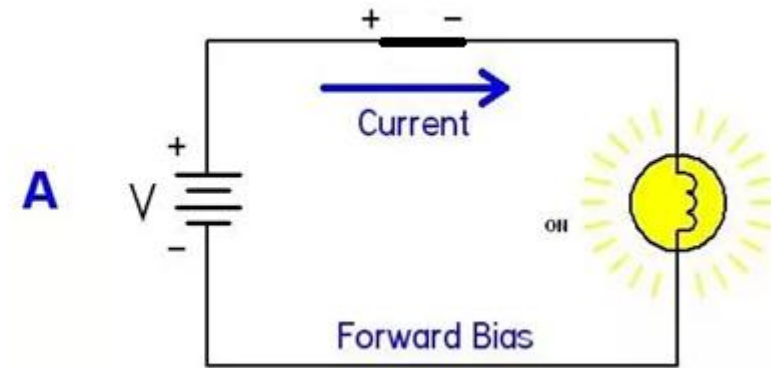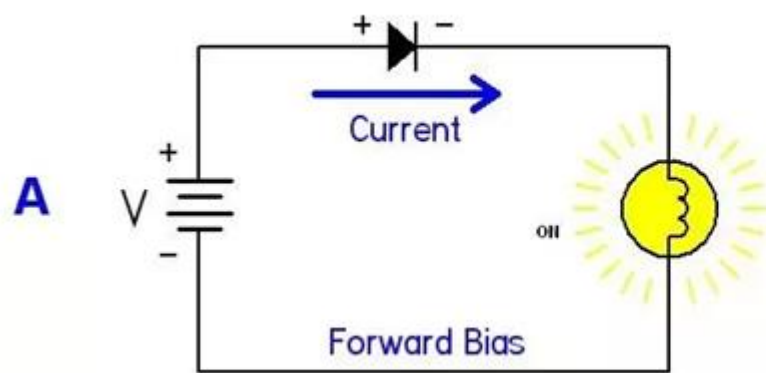

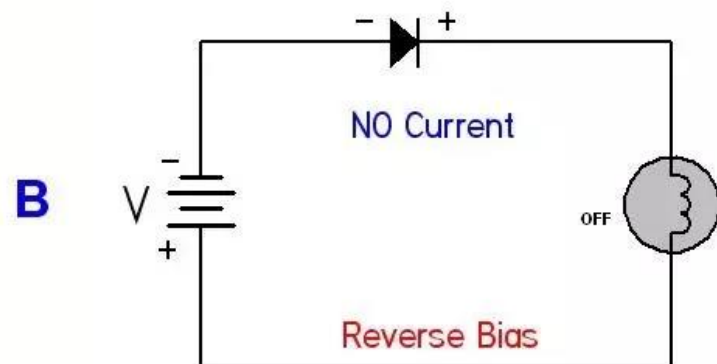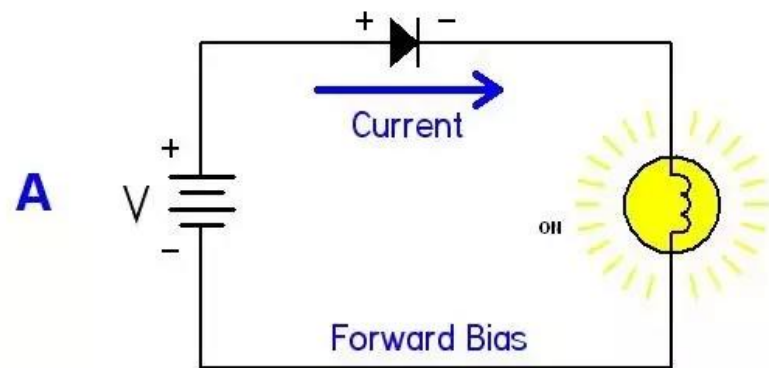

www.electrapk.com

Diode Clipper

A clipper is a type of diode network that has the ability to “clip off” a portion of the input signal without distorting the remaining part of the alternating waveform.



Types of Clipper: series clippers, shunt clippers and dual (combination) clippers.

Contd..



Series clippers: the **diode** is connected in **series** with the output load resistance.

Shunt clippers: the **diode** is connected in parallel with the output load resistance.



Ideal Diode

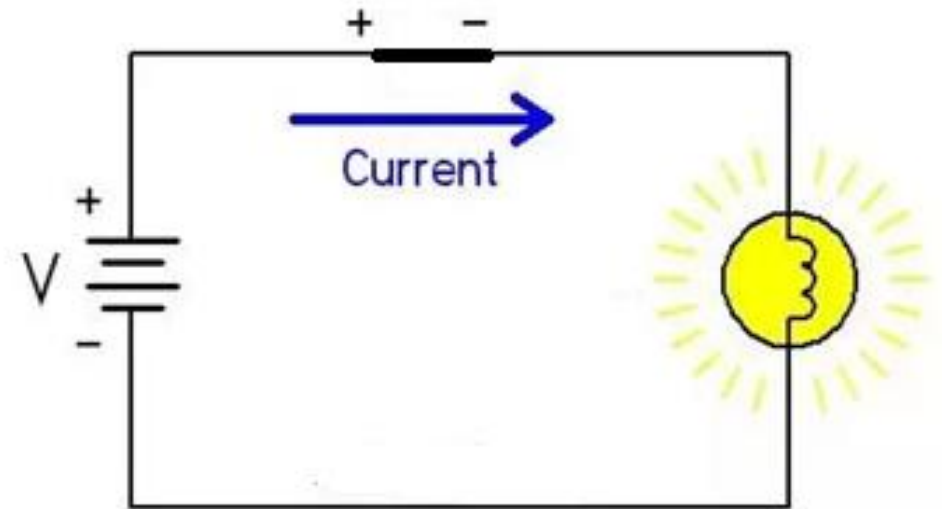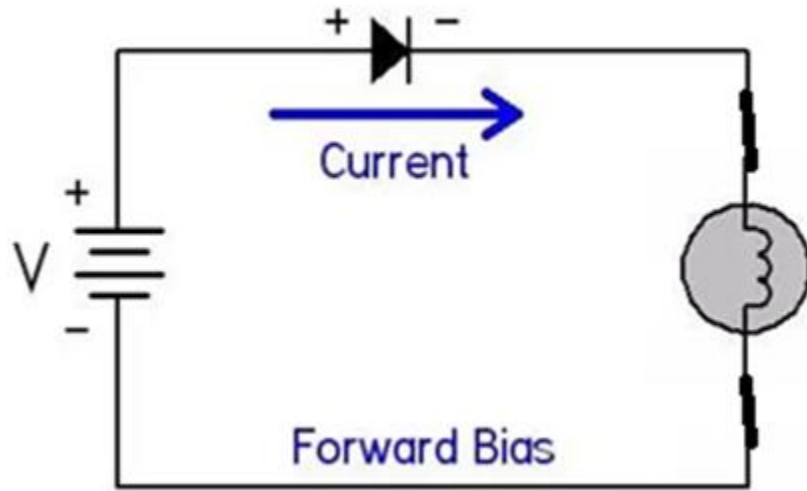



Silicon Diode

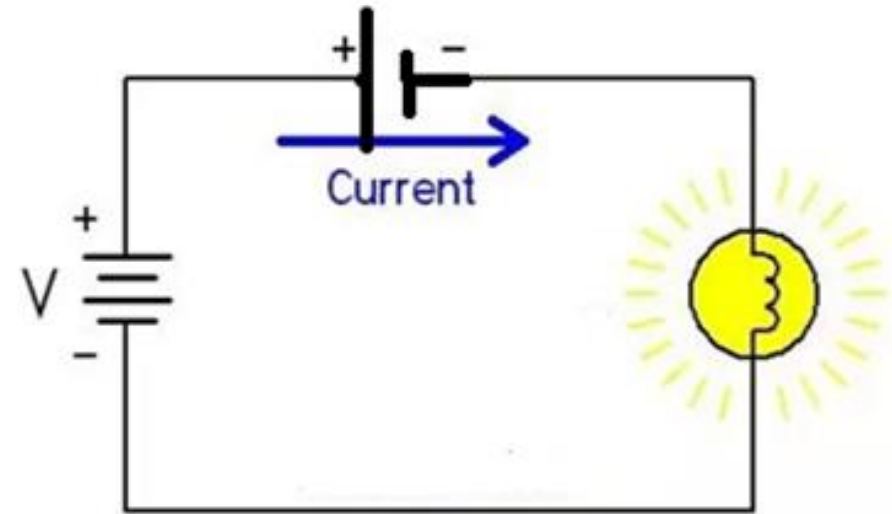
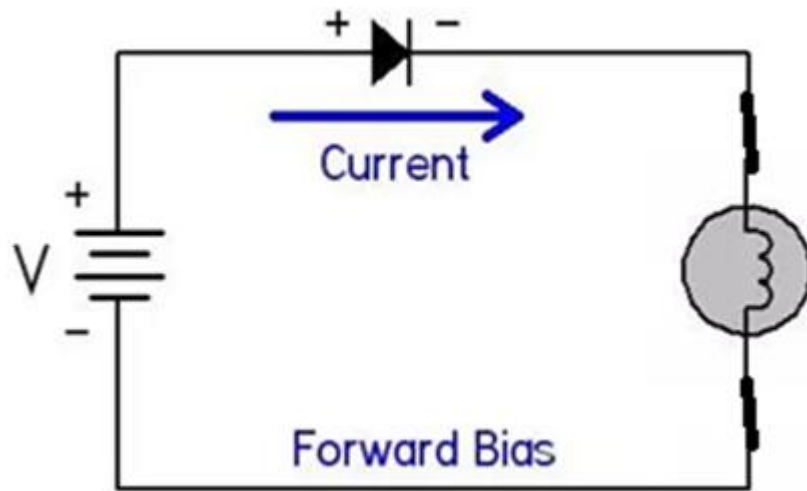




Example

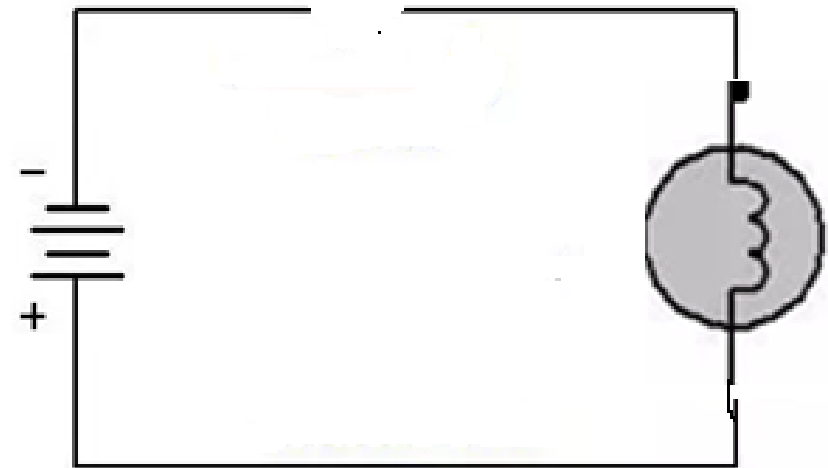
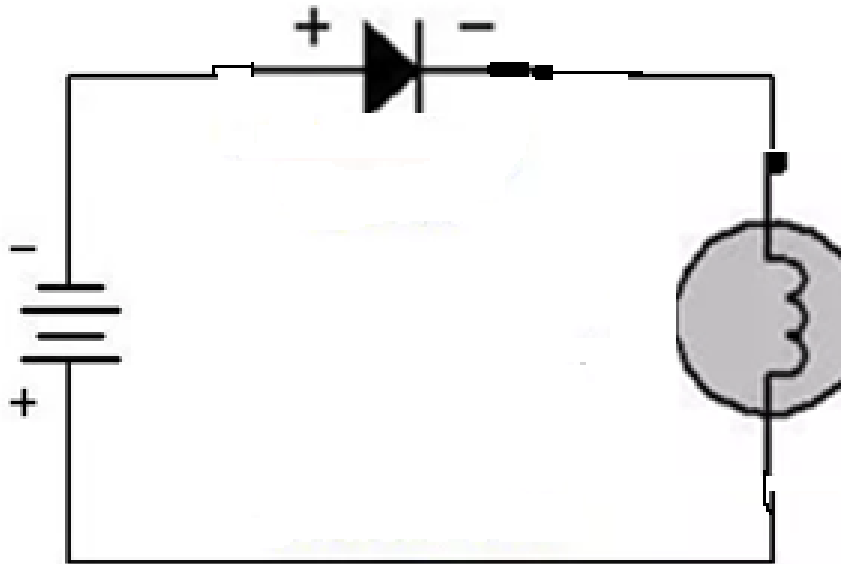


Ideal Diode

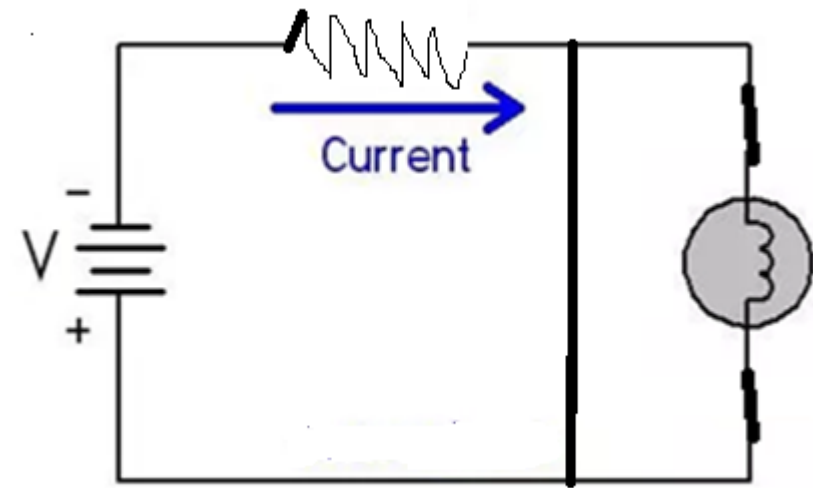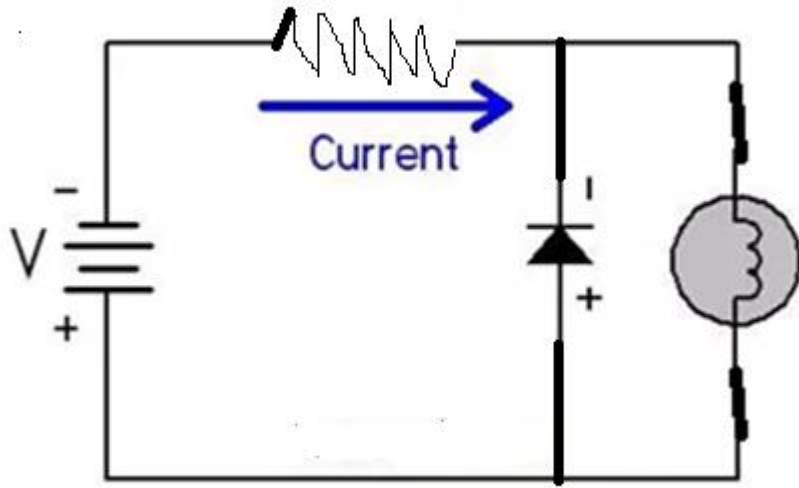


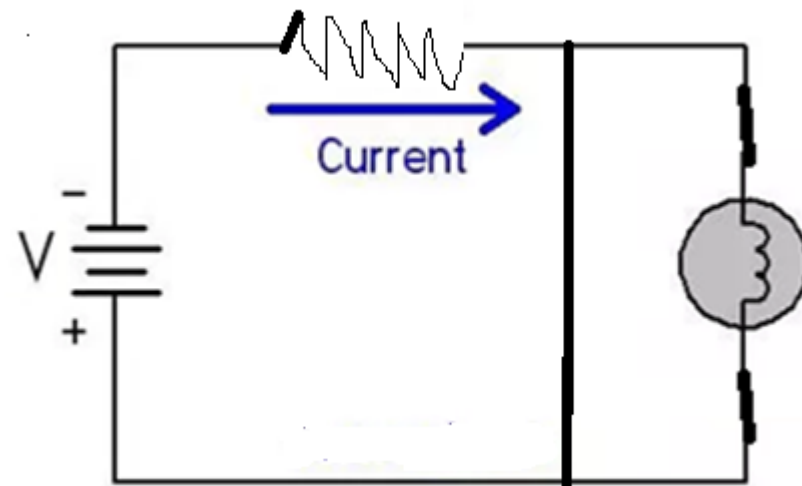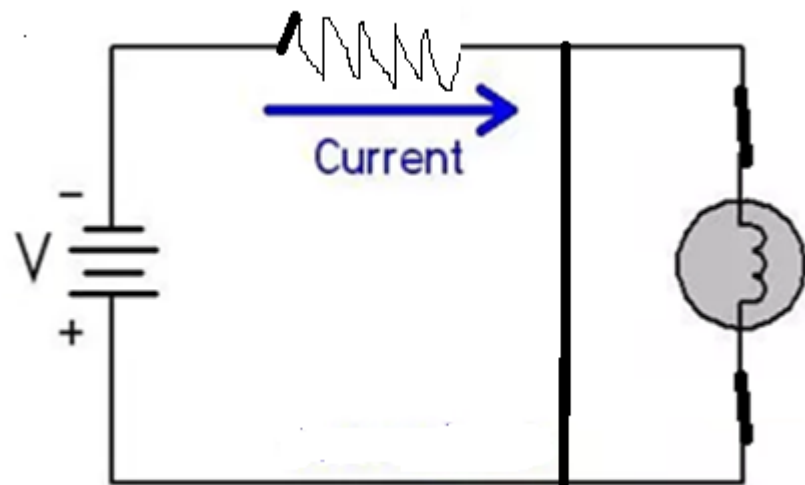

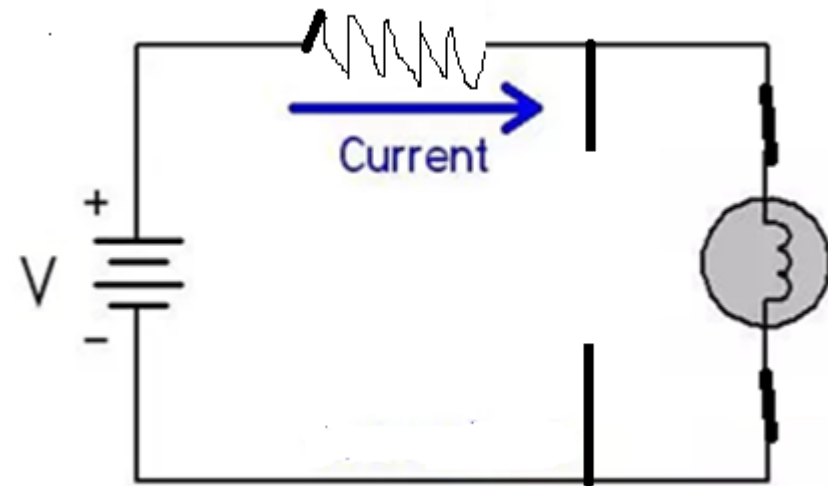
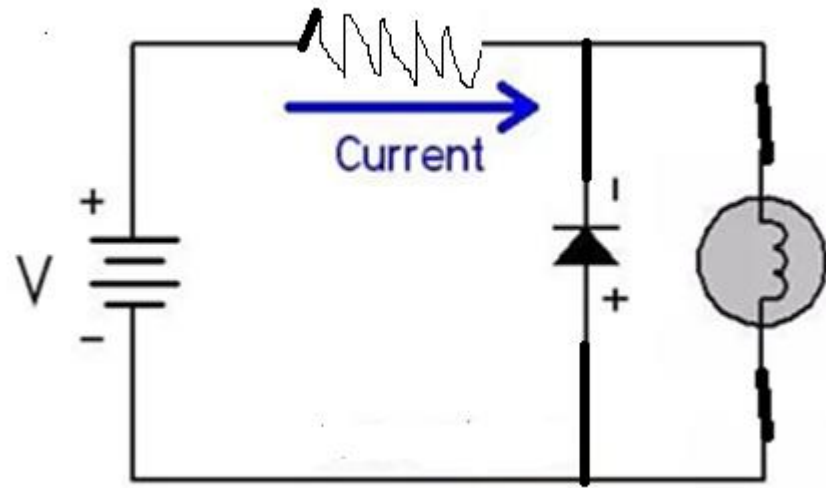


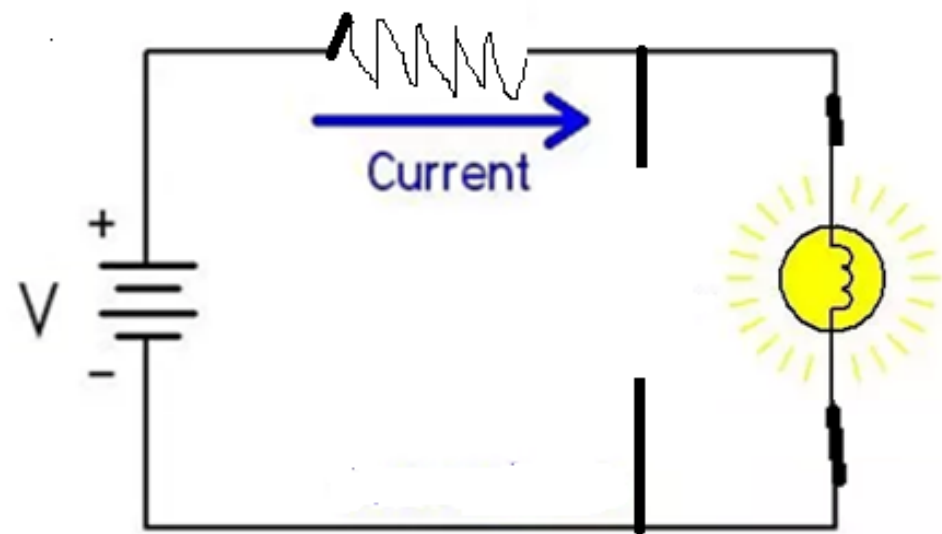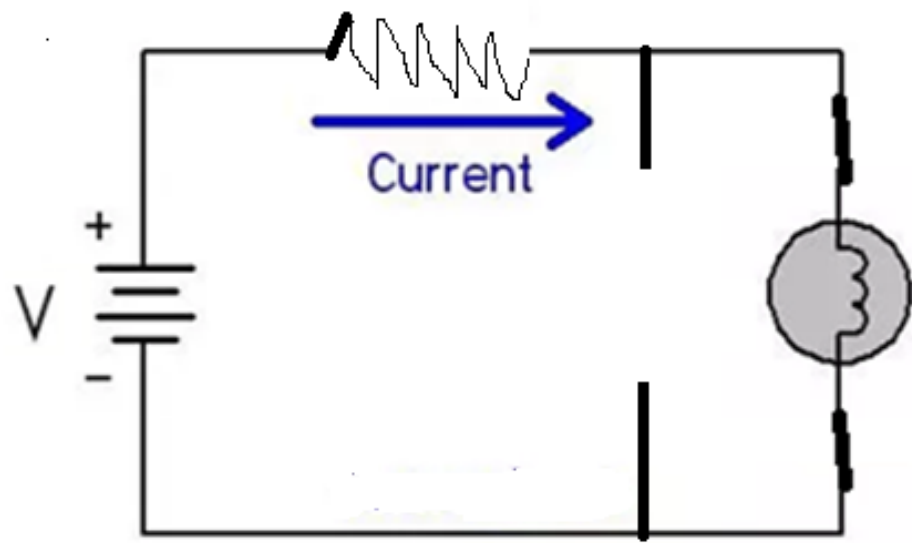



Series clippers

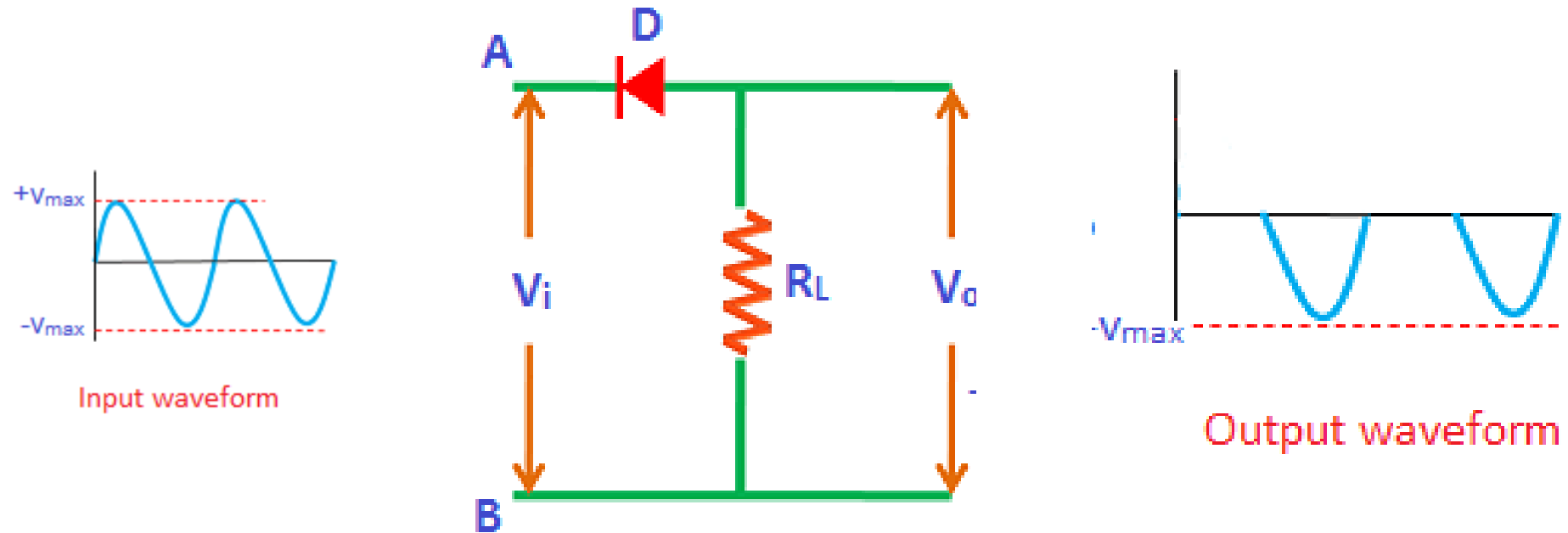



Positive Half Cycle

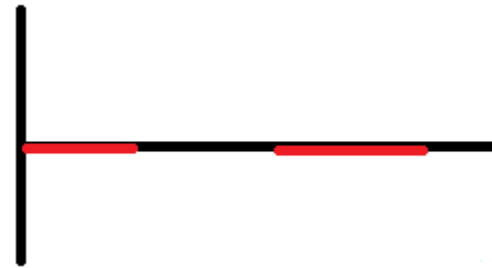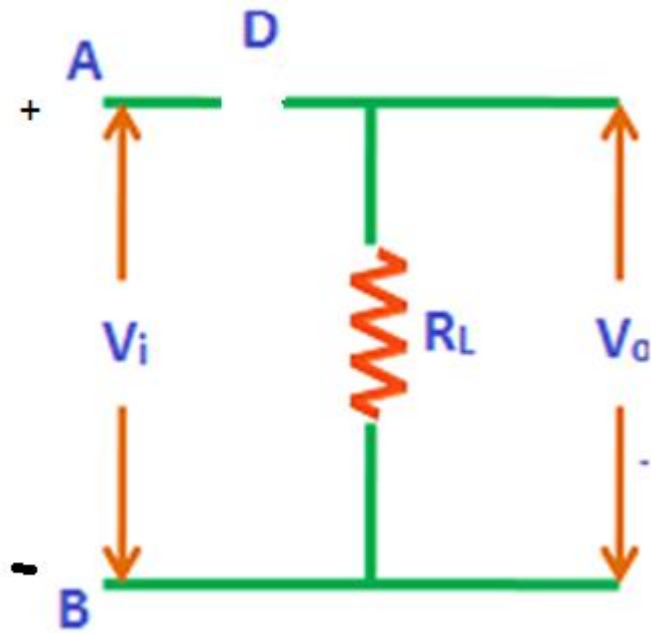



Negative Half Cycle

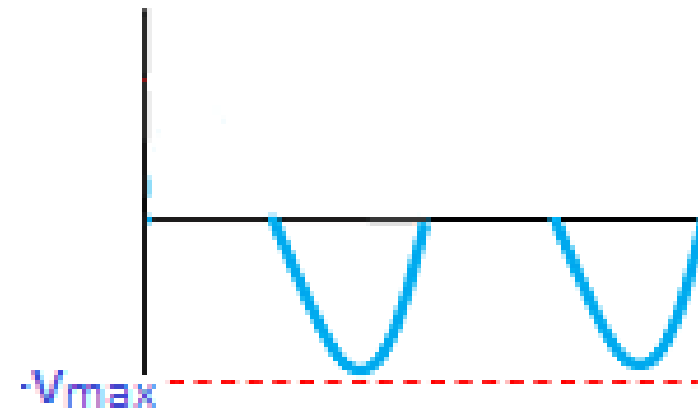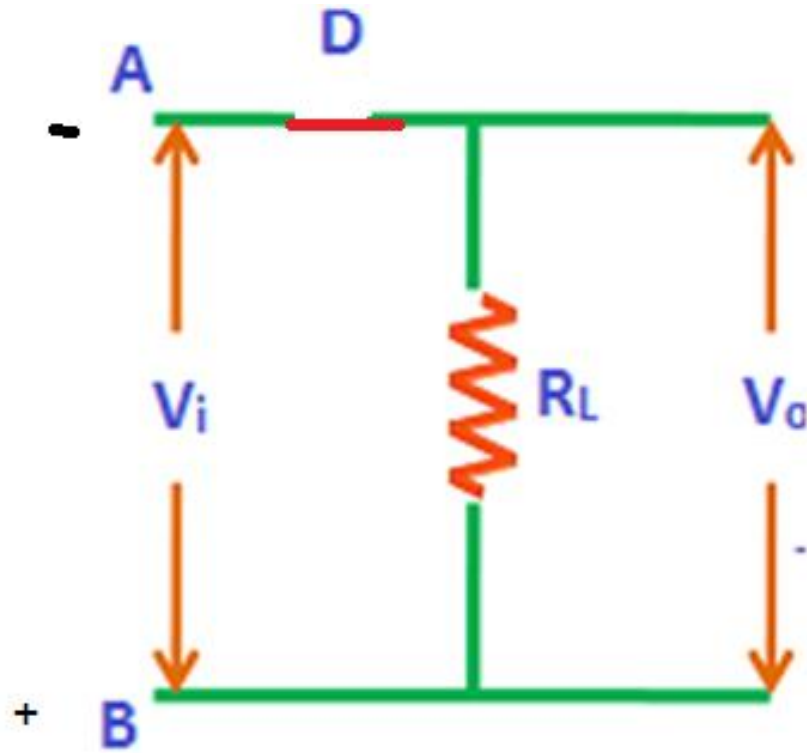



Contd..

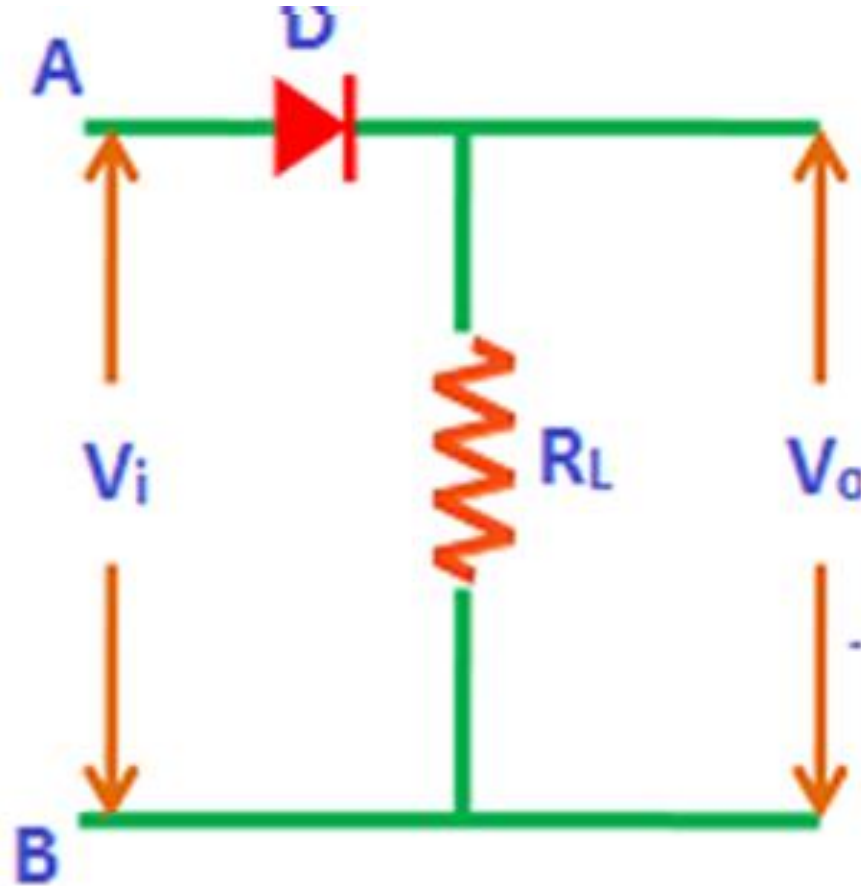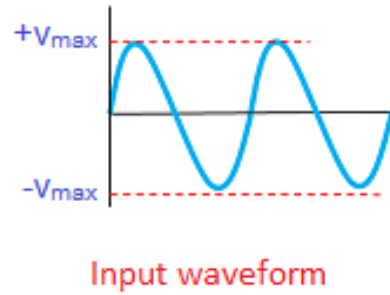


Contd..

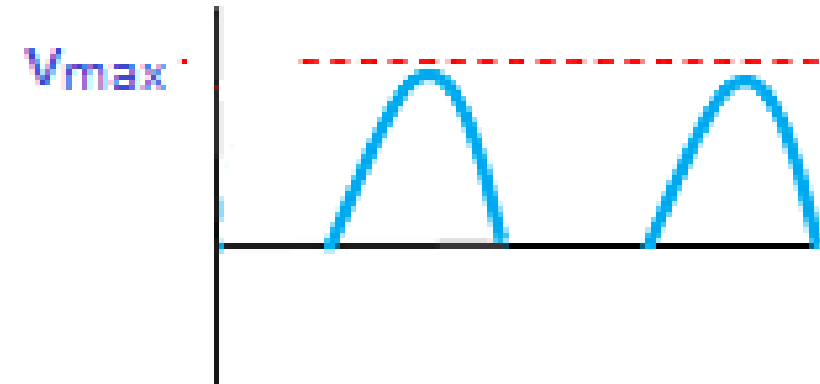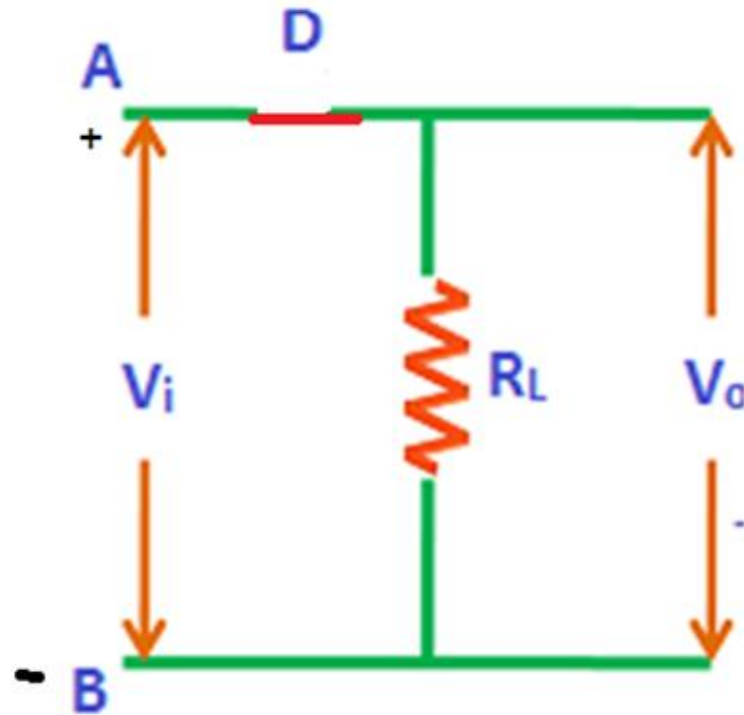


Negative Half Cycle

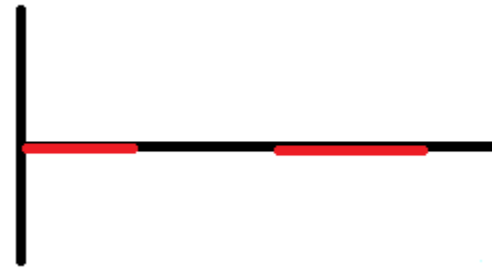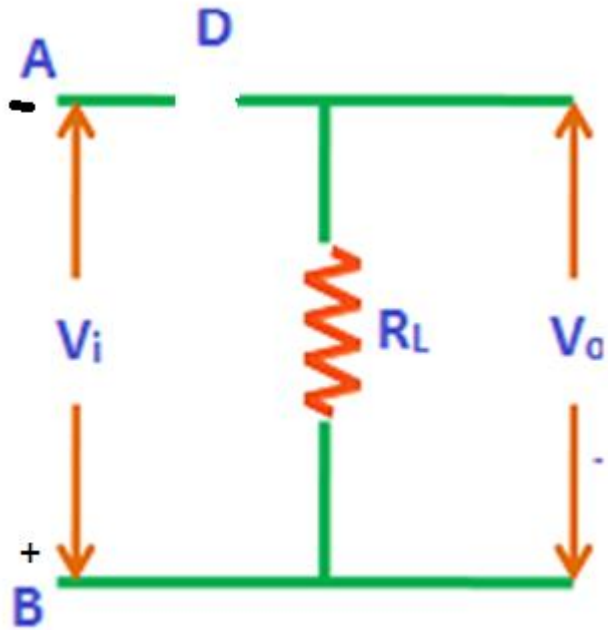



Parallel Clipper

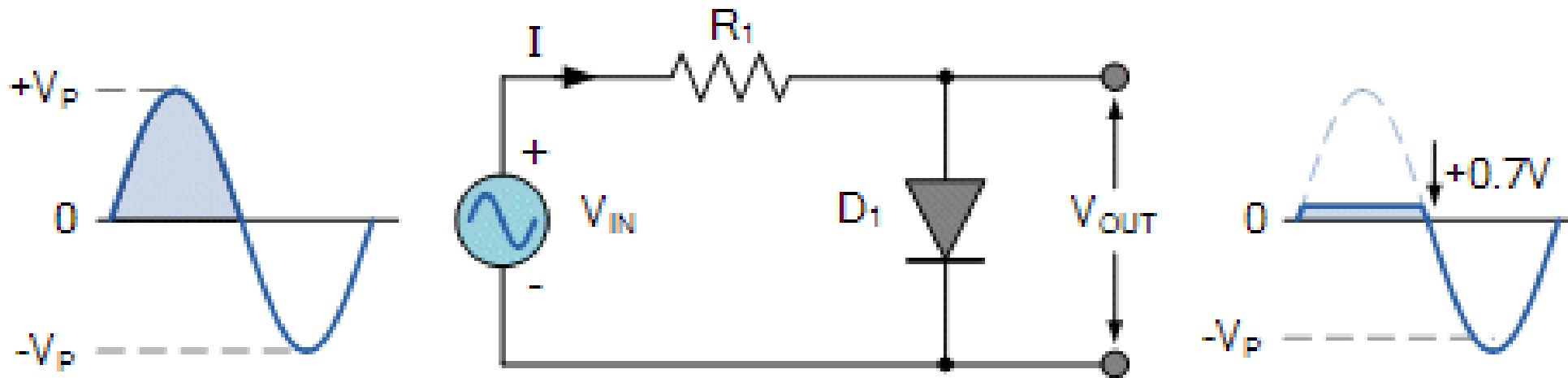



Positive Half Cycle

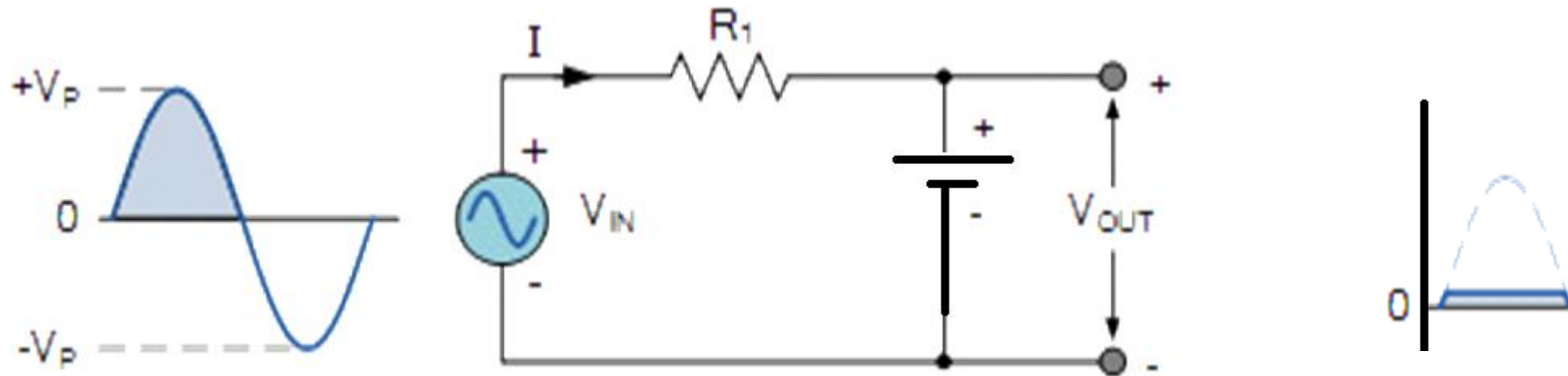


Negative Half Cycle

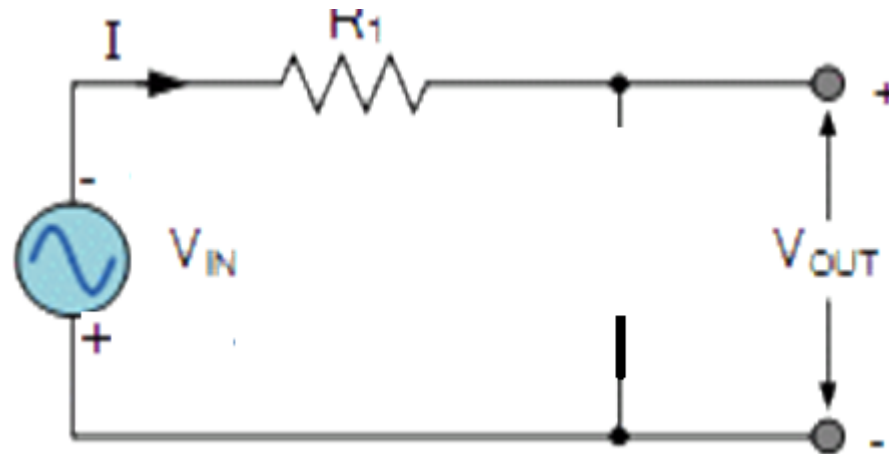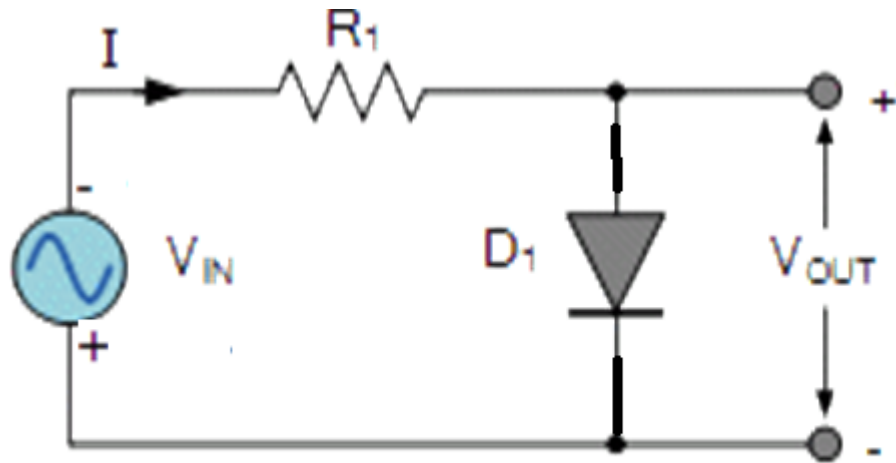


Contd..

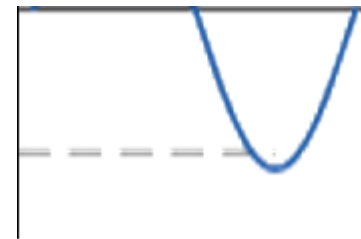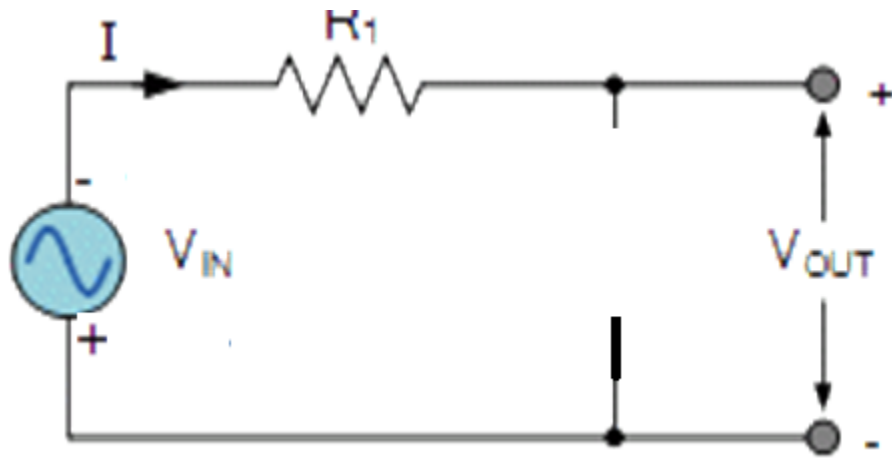



Example

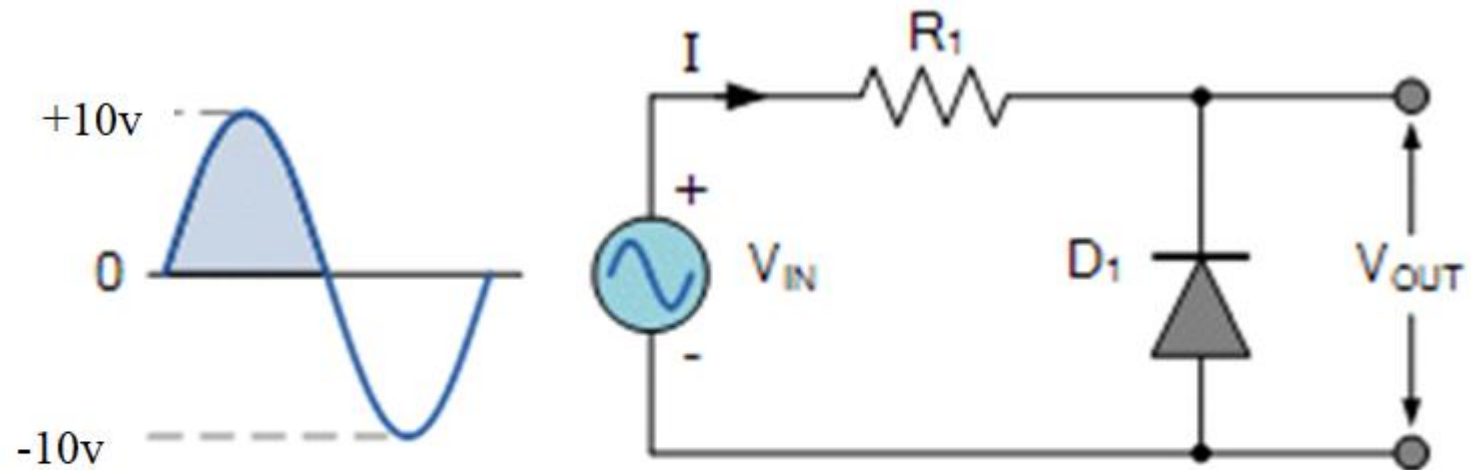


Contd..

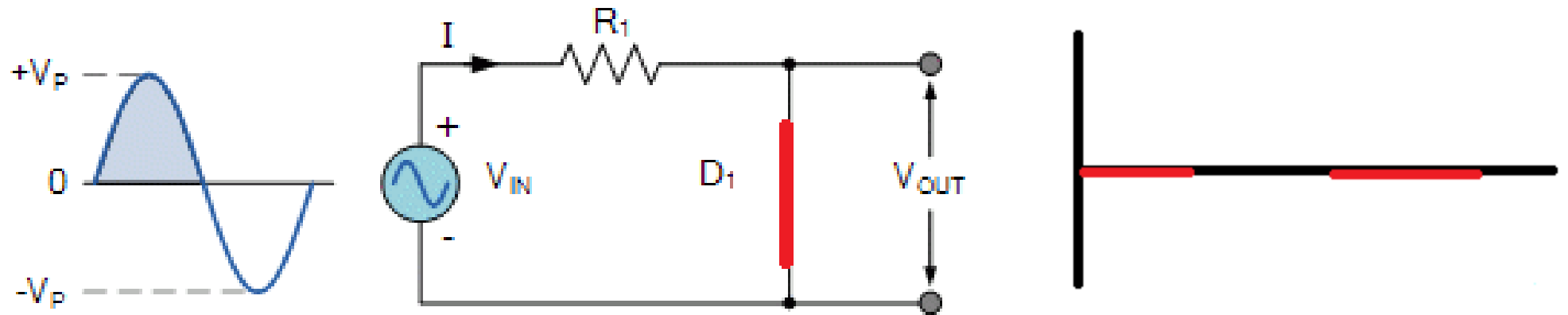


Contd..

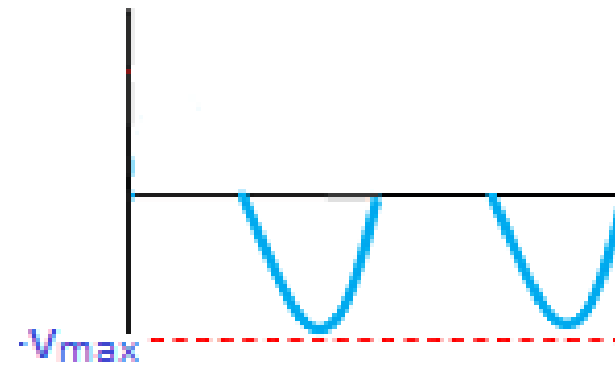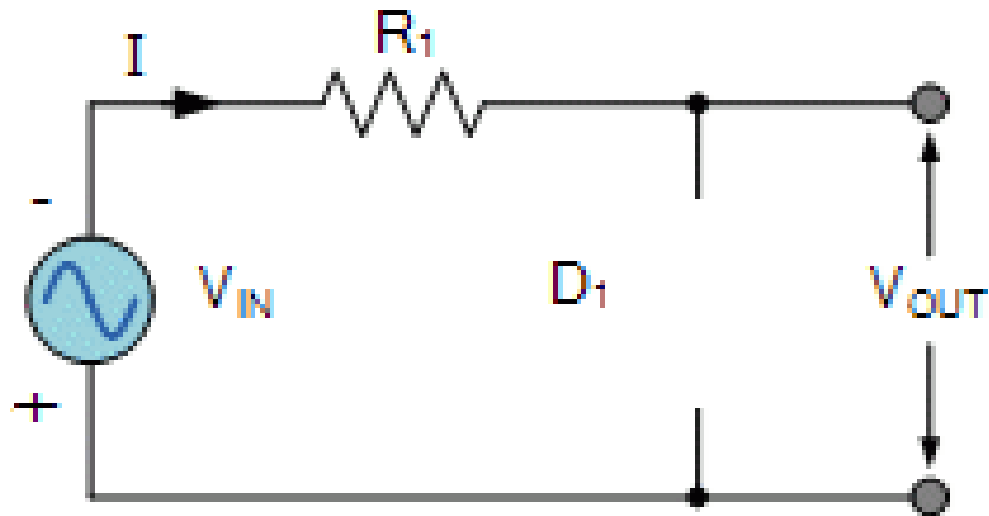



Example (ideal diode)

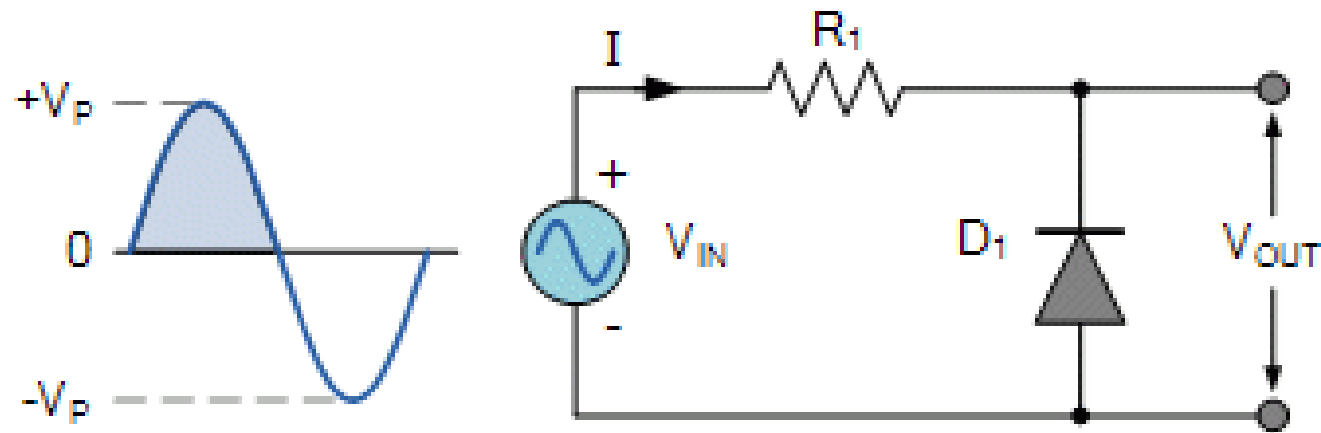


Negative Half Cycle

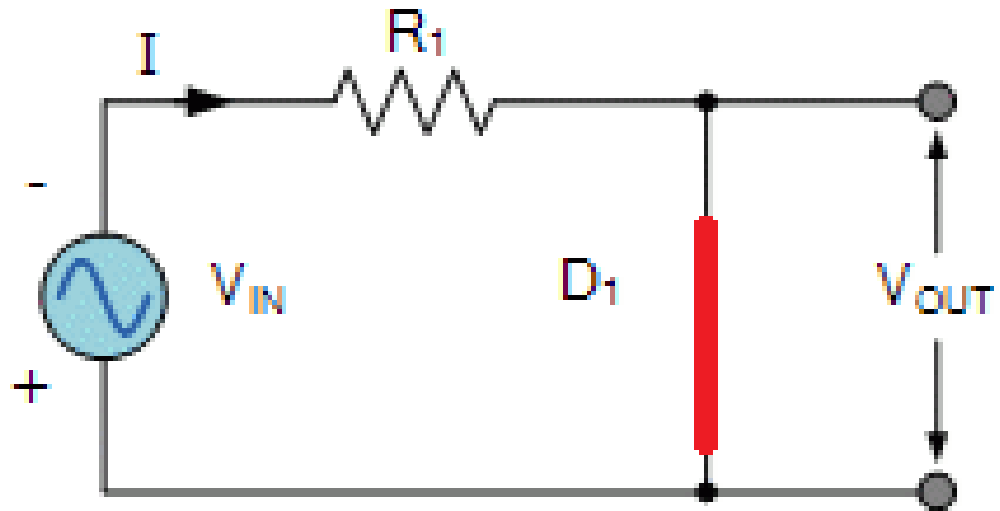


Positive half cycle

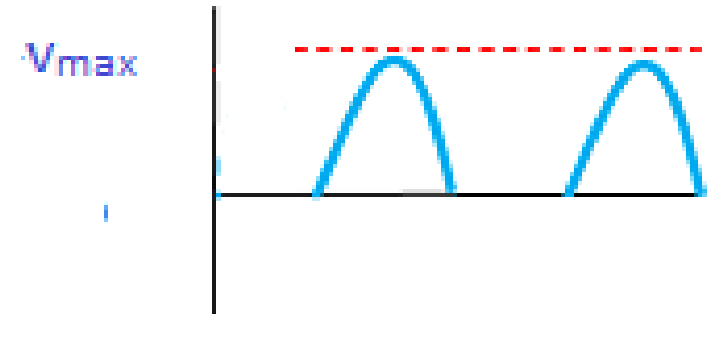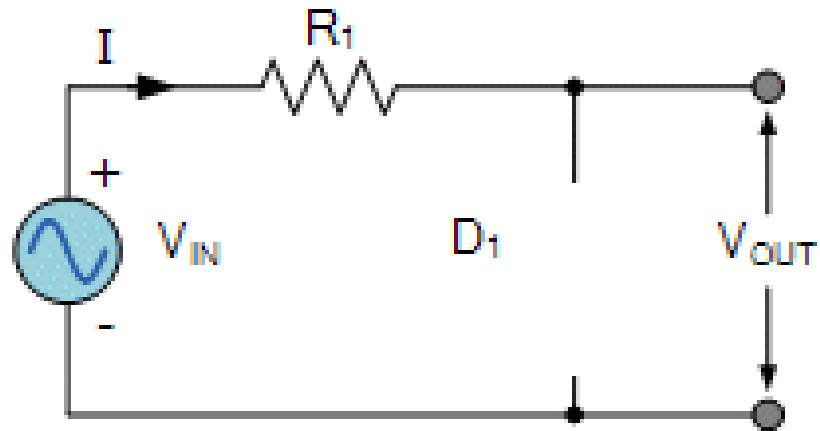


Positive Half Cycle

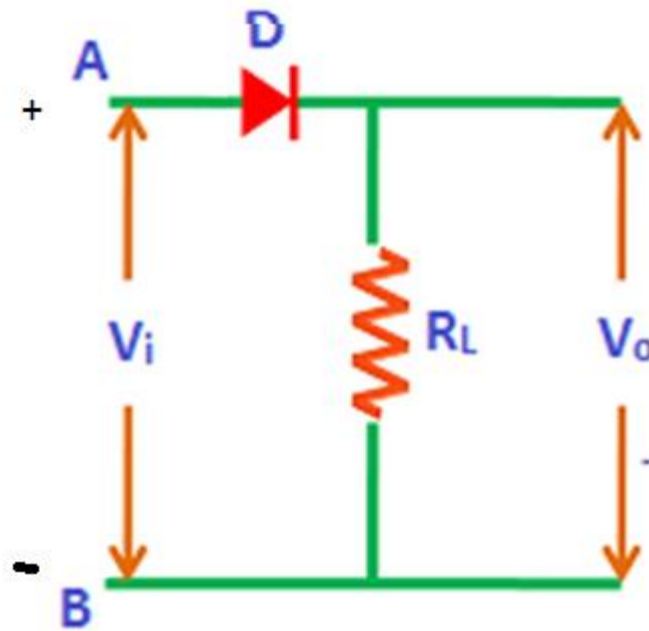

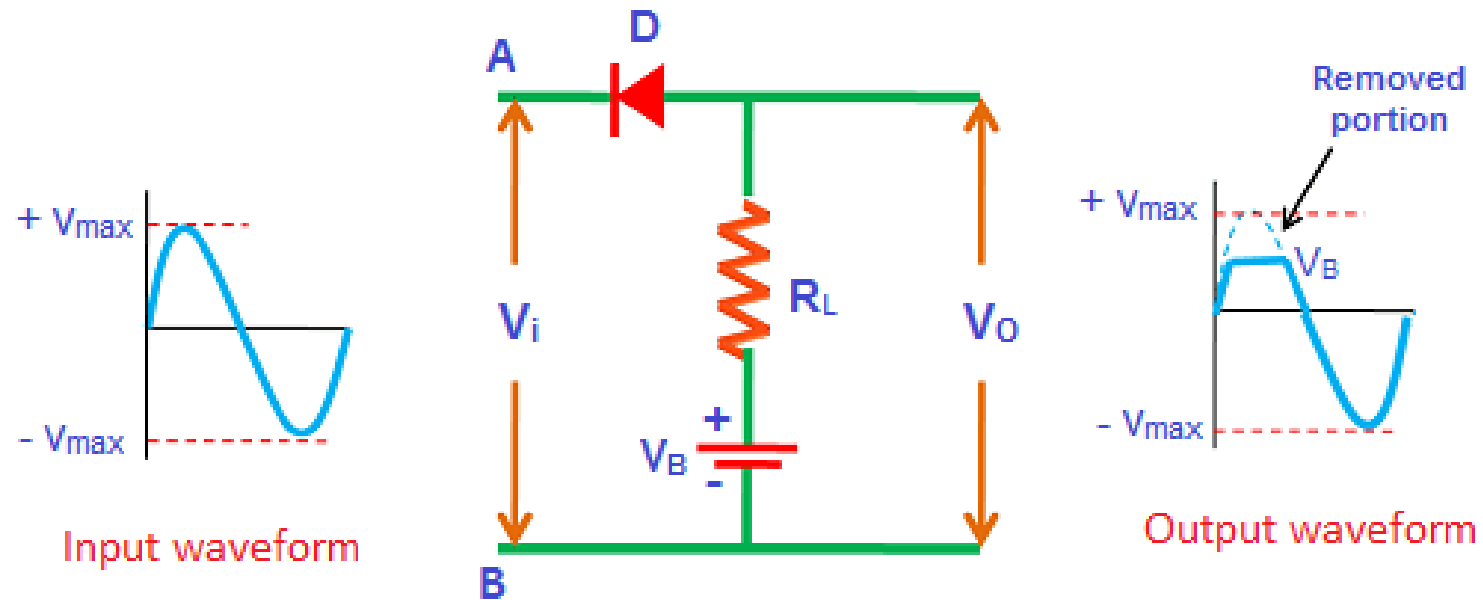


Series positive clipper with positive bias

Physics and Radio-Electronics

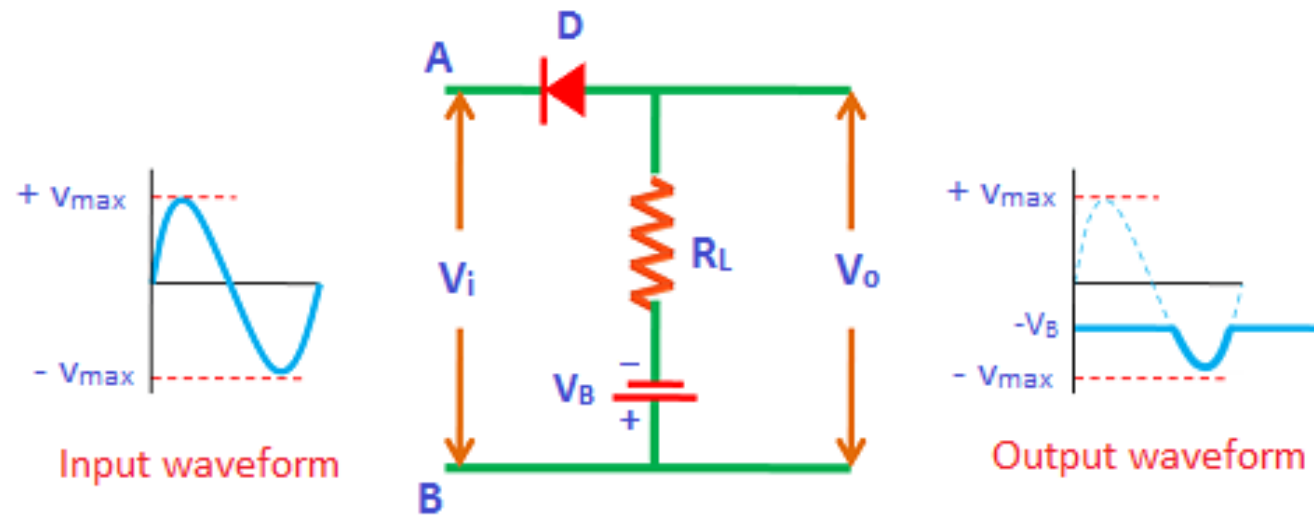


Series positive clipper with negative bias

Physics and Radio-Electronics

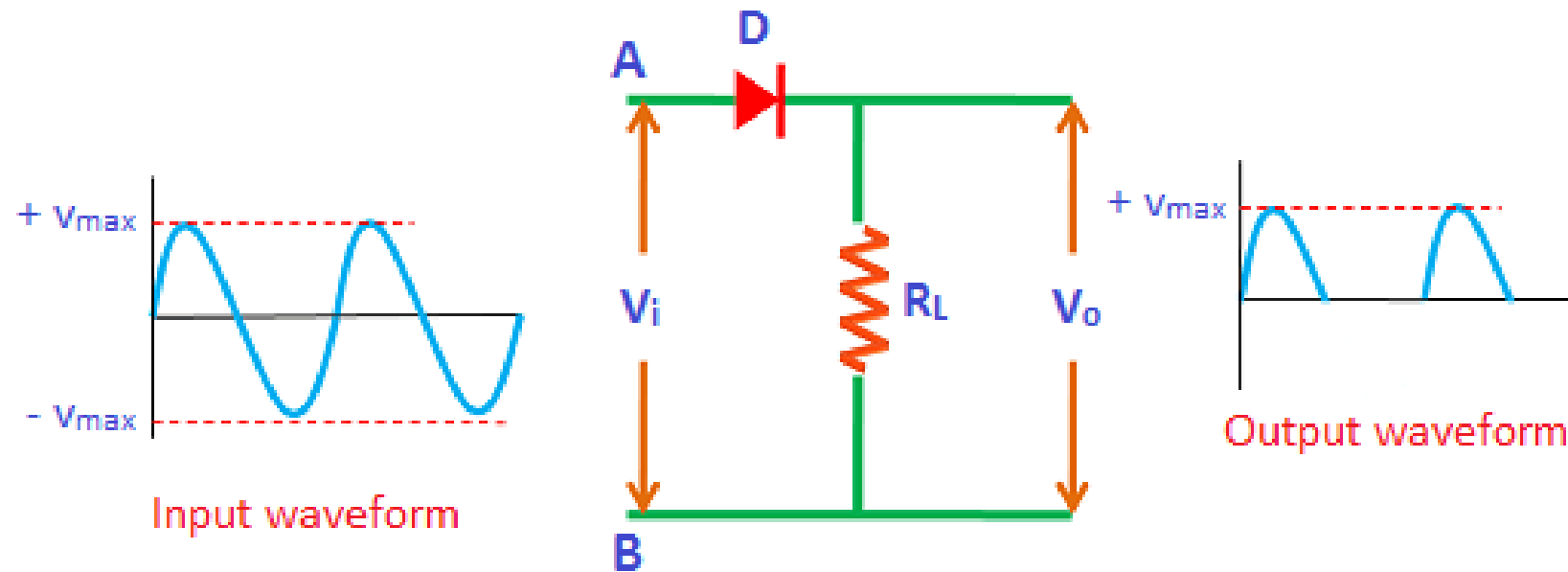


Series negative clipper

Physics and Radio-Electronics

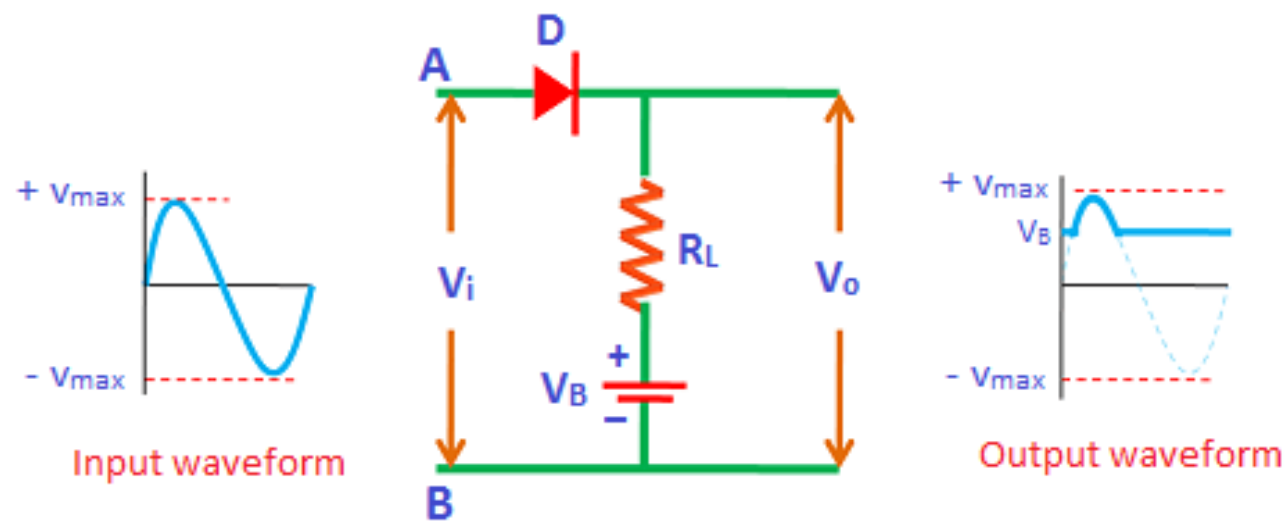


Series negative clipper with positive bias

Physics and Radio-Electronics

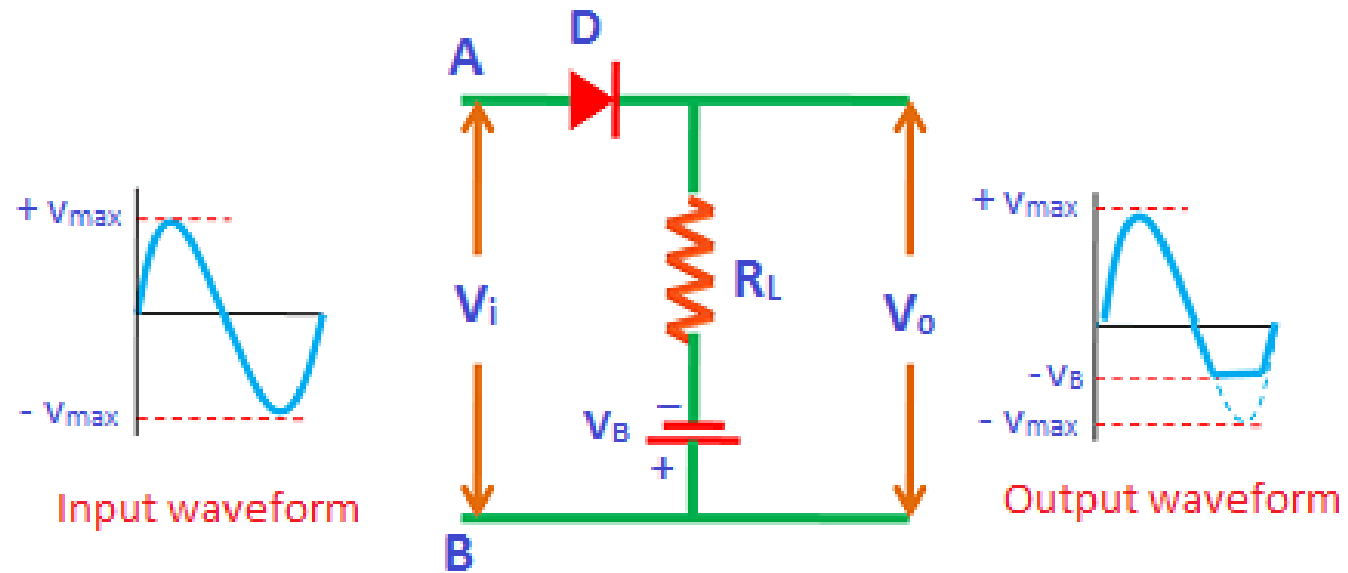


Series negative clipper with negative bias

Physics and Radio-Electronics

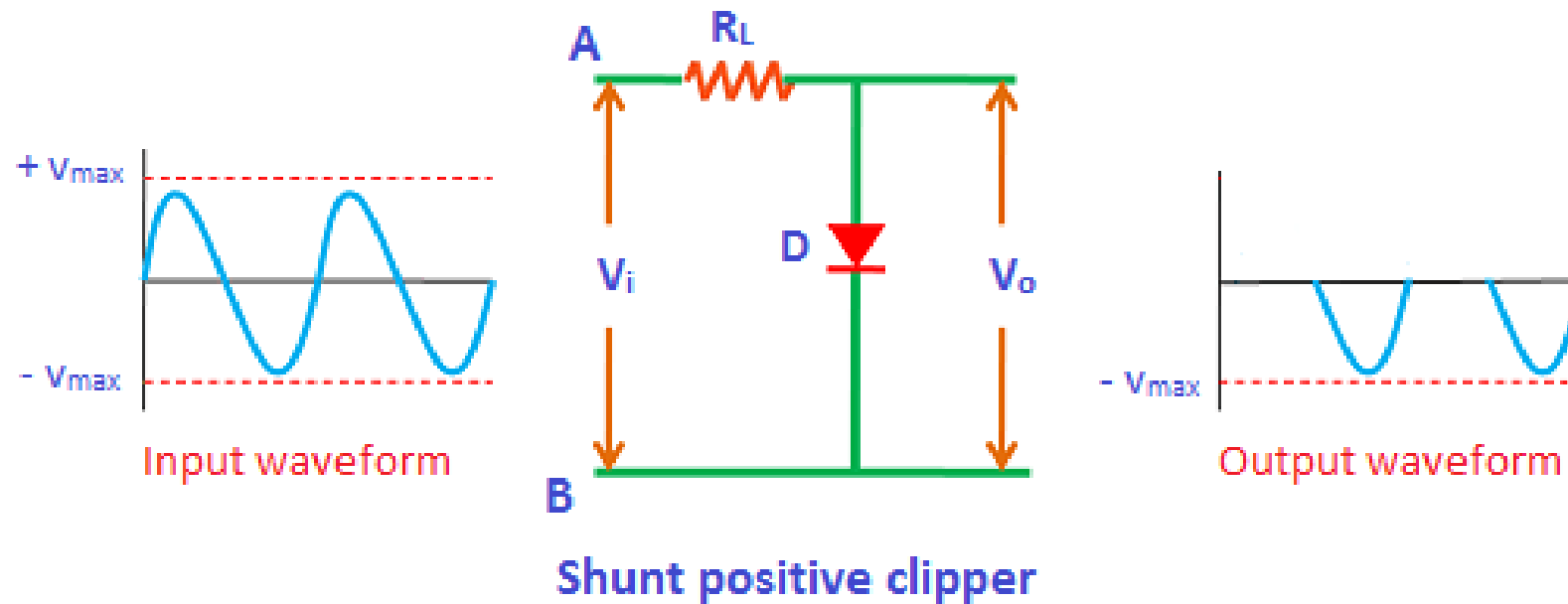


Physics and Radio-Electronics

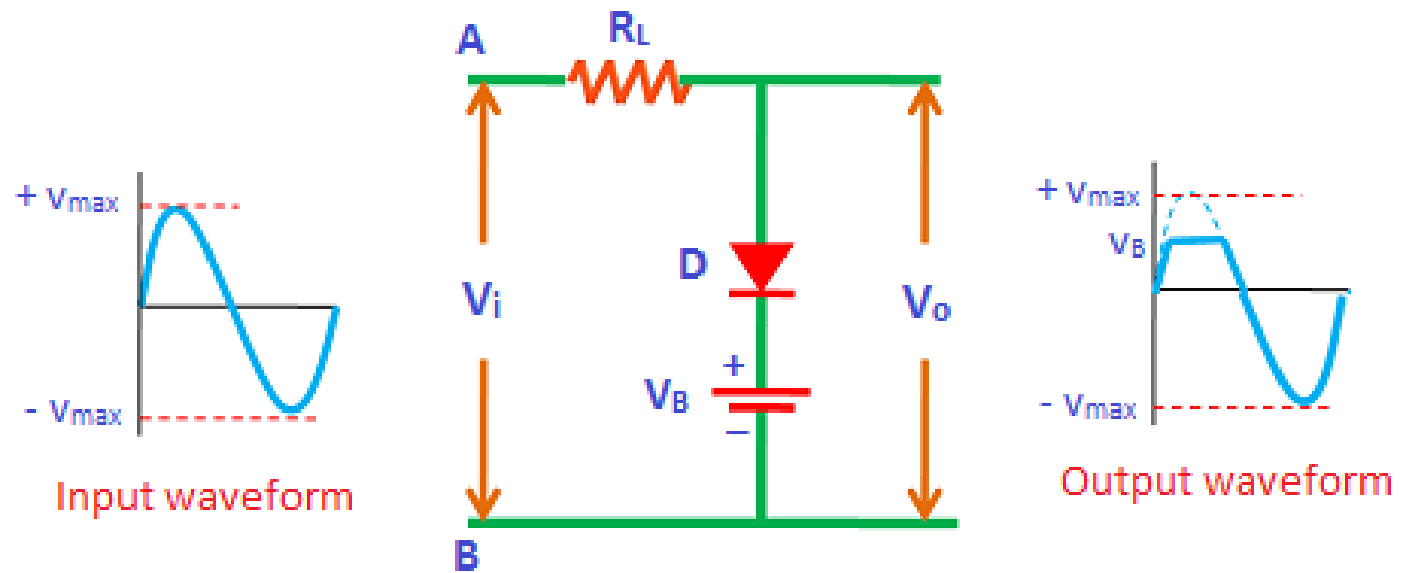

Shunt positive clipper with positive bias

Physics and Radio-Electronics

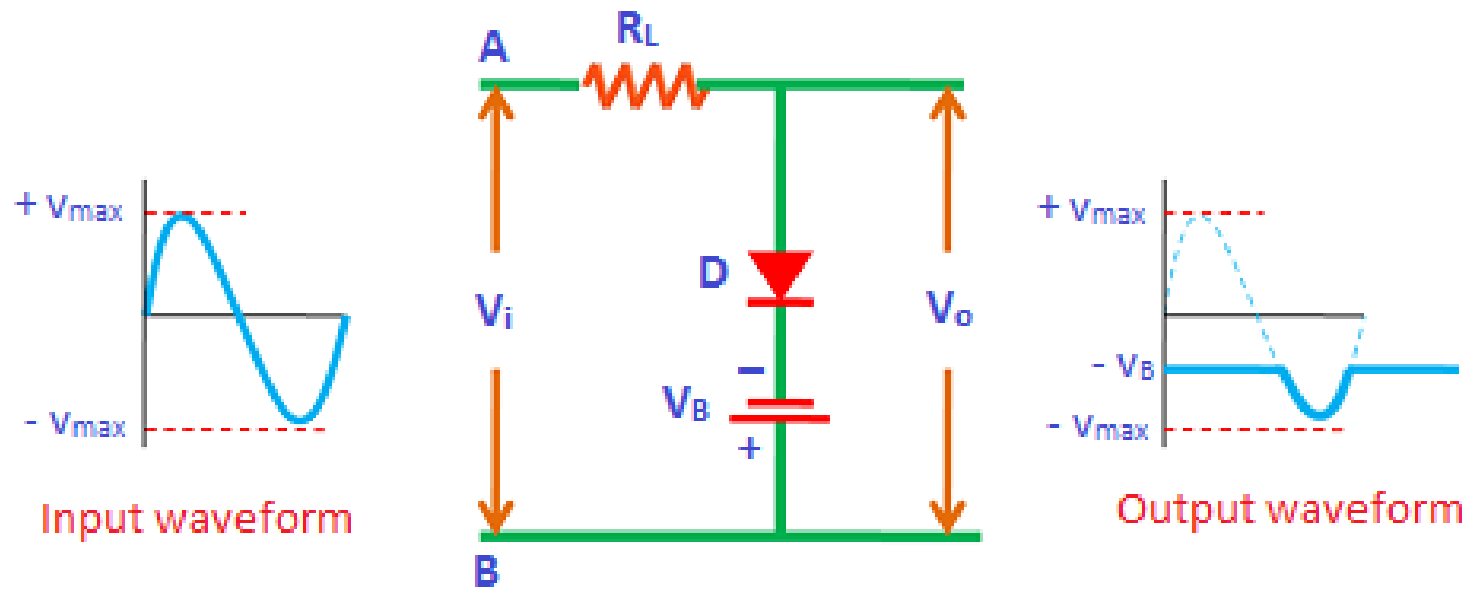

Shunt positive clipper with negative bias

Physics and Radio-Electronics