


Transistor Biasing

Sridevi N


Associate Professor

Dept. of EIE, Dr AIT

DC Load Line

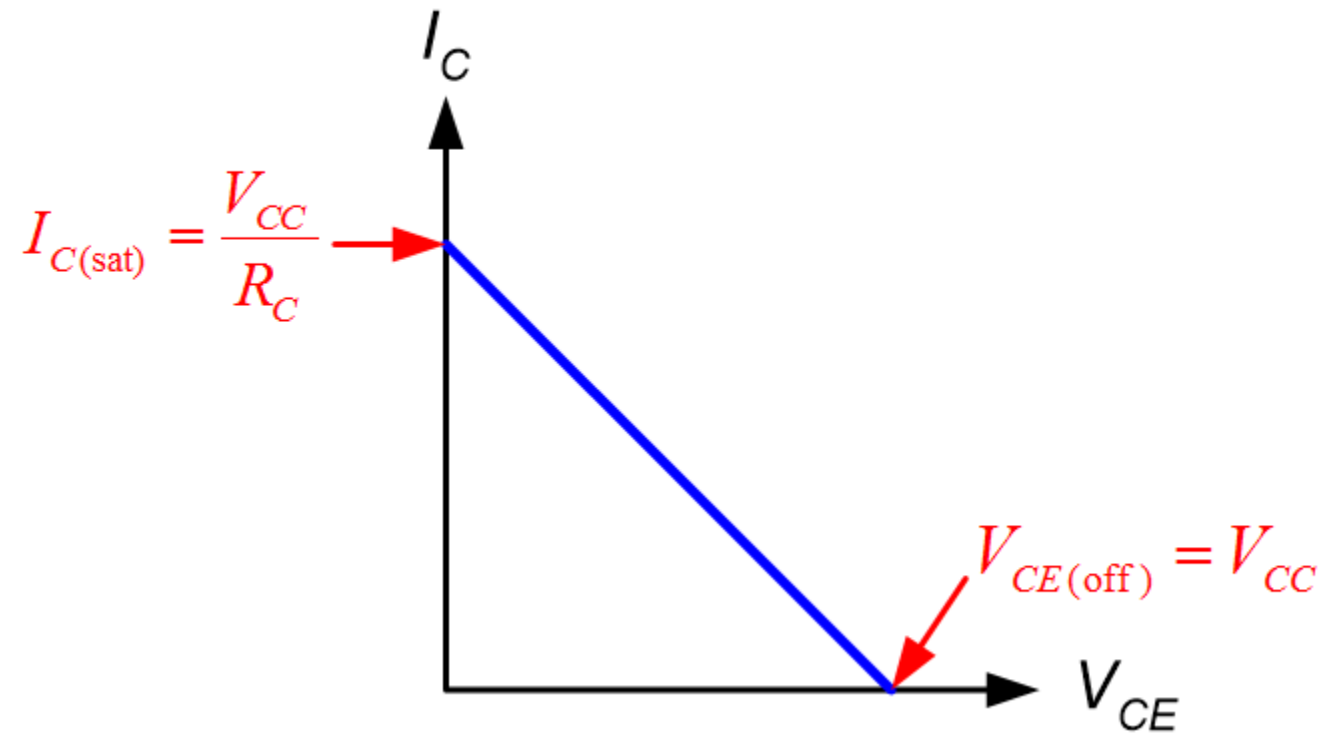

Operating Point

 

Biasing

The analysis or design of a transistor amplifier requires knowledge of both the dc and ac response of the system. In fact, the amplifier increases the strength of a weak signal by transferring the energy from the applied DC source to the weak input ac signal. The analysis or design of any electronic amplifier therefore has two components:

- ❖ The dc portion and
- ❖ The ac portion

During the design stage, the choice of parameters for the required dc levels will affect the ac response.

Biasing: Application of dc voltages to establish a fixed level of current and voltage.


Purpose of the DC biasing circuit

- ❖ To turn the device “ON”
- ❖ To place it in operation in the region of its characteristic where the device operates most linearly .
- ❖ Proper biasing circuit which it operate in linear region and circuit have centered Q-point or midpoint biased
- ❖ Improper biasing cause Improper biasing cause
- ❖ Distortion in the output signal
- ❖ Produce limited or clipped at output signal

BIASING AND BIAS STABILITY


- ❖ Biasing refers to the establishment of suitable dc values of different currents and voltages of a transistor.
- ❖ Through proper biasing, a desired quiescent operating point of the transistor amplifier in the active region (linear region) of the characteristics is obtained.
- ❖ The selection of a proper quiescent point generally depends on the following factors:
 - (a) The amplitude of the signal to be handled by the amplifier and distortion level in signal
 - (b) The load to which the amplifier is to work for a corresponding supply voltage
- ❖ The operating point of a transistor amplifier shifts mainly with changes in temperature, since the transistor parameters — β , I_{CO} and V_{BE} (where the symbols carry their usual meaning)—are functions of temperature.
- ❖ **Circuit Configurations**
 - **Fixed-bias circuit**
 - **Fixed bias with emitter resistance**
 - **Voltage-divider bias**
 - **Voltage-feedback biasing**

Fixed Bias Circuit

 


- This is common emitter (CE) configuration
- 1st step: Locate capacitors and replace them with an open circuit
- 2nd step: Locate 2 main loops which;
 - BE loop (input loop)
 - CE loop(output loop)

 
- **1st step:** Locate capacitors and replace them with an open circuit



- 2nd step: Locate 2 main loops.

 

- BE Loop Analysis

 


■ From KVL;

$$-V_{CC} + I_B R_B + V_{BE} = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B} \quad \text{A}$$

- CE Loop Analysis

 

■ From KVL;

$$-V_{CC} + I_C R_C + V_{CE} = 0$$

$$\therefore V_{CE} = V_{CC} - I_C R_C$$

■ As we know;

$$I_C = \beta I_B \text{ (B)}$$

■ Substituting (A) with (B)


$$I_C = \beta_{DC} \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$

Note that R_C does not affect the value of I_C

Load line analysis

A fixed bias circuit with given values of V_{CC} , R_C and R_B can be analyzed (means, determining the values of I_{BQ} , I_{CQ} and V_{CEQ}) using the concept of load line also.

 Here the input loop KVL equation is not used for the purpose of analysis, instead, the output characteristics of the transistor used in the given circuit and output loop KVL equation are made use of.



➤ Plot load line equation


$$V_{CE} = V_{CC} - I_C R_C$$

➤ $I_{C(sat)}$ occurs when transistor operating in *saturation region*


$$I_{C_{sat}} = \frac{V_{CC}}{R_C} \Big|_{V_{CE}=0}$$

➤ $V_{CE(off)}$ occurs when transistor operating in *cut-off region*


$$V_{CE(off)} = V_{CC} - I_C R_C \Big|_{I_C=0}$$

 


Circuit Values Affect the Q-Point

 

Decreasing V_{CC}

 


Increasing R_C

 

Varying I_B

Problem

 

Determine the following for the fixed-bias configuration

- I_{BQ} and I_{CQ} .
- V_{CEQ} .
- V_B and V_C .
- V_{BC} .

solution

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{240 \text{ k}\Omega} = \mathbf{47.08 \mu\text{A}}$$

$$I_{CQ} = \beta I_{BQ} = (50)(47.08 \mu\text{A}) = \mathbf{2.35 \text{ mA}}$$

$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C R_C \\ &= 12 \text{ V} - (2.35 \text{ mA})(2.2 \text{ k}\Omega) \\ &= \mathbf{6.83 \text{ V}} \end{aligned}$$

$$V_B = V_{BE} = \mathbf{0.7 \text{ V}}$$

$$V_C = V_{CE} = \mathbf{6.83 \text{ V}}$$

$$\begin{aligned} V_{BC} &= V_B - V_C = 0.7 \text{ V} - 6.83 \text{ V} \\ &= \mathbf{-6.13 \text{ V}} \end{aligned}$$

with the negative sign revealing that the junction is reversed-biased, as it should be for linear amplification.


Fixed Bias Circuit

DISADVANTAGE

- Unstable – because it is too dependent on β and produce width change of Q-point
- For improved bias stability , add emitter resistor to dc bias.


VOLTAGE DIVIDER BIAS CIRCUIT

- Provides good Q-point stability with a single polarity supply voltage
 - This is the biasing circuit wherein, I_{CQ} and V_{CEQ} are almost independent of β .
 - The level of I_{BQ} will change with β so as to maintain the values of I_{CQ} and V_{CEQ} almost same, thus maintaining the stability of Q point.
-
- 1st step: Locate capacitors and replace them with an open circuit
 - 2nd step: Simplified circuit using **Thevenin Theorem**
 - 3rd step: Locate 2 main loops which;
 - BE loop
 - CE loop

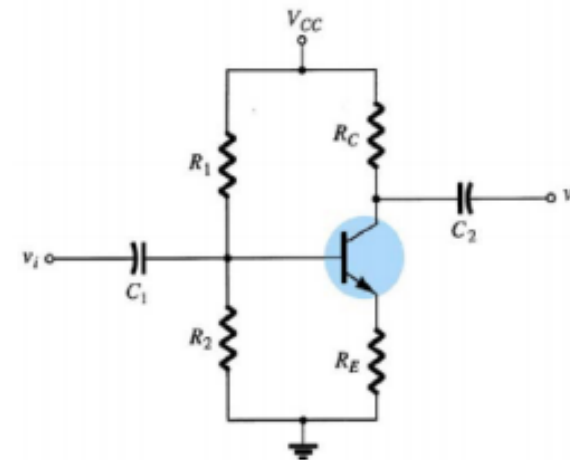

VOLTAGE DIVIDER BIAS CIRCUIT

 - 2nd step: : Simplified circuit using **Thevenin Theorem**




From Thevenin Theorem;

$$R_{TH} = R_1 // R_2 = \frac{R_1 \times R_2}{R_1 + R_2}$$



$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

VOLTAGE DIVIDER BIAS CIRCUIT

- 2nd step: Locate 2 main loops.

 


Thevenin Equivalent Resistance

  


$$R_{Th} = R_1 \parallel R_2$$

Thevenin Equivalent Voltage

 

$$E_{Th} = V_{R_2} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

Base Emitter Loop

 

■ From KVL;

$$-V_{TH} + I_B R_{TH} + V_{BE} + I_E R_E = 0$$

Recall; $I_E = (\beta + 1)I_B$

Substitute for I_E


$$-V_{TH} + I_B R_{TH} + V_{BE} + (\beta + 1)I_B R_E = 0$$

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

VOLTAGE DIVIDER BIAS CIRCUIT

- CE Loop Analysis

 

■ From KVL;

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

■ Assume;

$$I_E \approx I_C$$

■ Therefore;


$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Transistor Analysis

- Transistor Saturation


$$I_{C_{sat}} = I_{C_{max}} = \frac{V_{CC}}{R_C + R_E}$$

- Load Line Analysis

 

 Example

- Determine the I_{CQ} and V_{CEQ} for the voltage divider network shown below



Solution

$$R_{Th} = R_1 \parallel R_2 = 82 \text{ k}\Omega \parallel 22 \text{ k}\Omega = 17.35 \text{ k}\Omega$$

$$E_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{22 \text{ k}\Omega (18 \text{ V})}{82 \text{ k}\Omega + 22 \text{ k}\Omega} = 3.81 \text{ V}$$

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E} = \frac{3.81 \text{ V} - 0.7 \text{ V}}{17.35 \text{ k}\Omega + (51)(1.2 \text{ k}\Omega)} = \frac{3.11 \text{ V}}{78.55 \text{ k}\Omega} = 39.6 \text{ }\mu\text{A}$$

$$I_{C_Q} = \beta I_B = (50)(39.6 \text{ }\mu\text{A}) = \mathbf{1.98 \text{ mA}}$$


$$\begin{aligned} V_{CE_Q} &= V_{CC} - I_C(R_C + R_E) \\ &= 18 \text{ V} - (1.98 \text{ mA})(5.6 \text{ k}\Omega + 1.2 \text{ k}\Omega) \\ &= \mathbf{4.54 \text{ V}} \end{aligned}$$

SMALL-SIGNAL LOW-FREQUENCY OPERATION OF TRANSISTORS

Hybrid Parameters and Two-Port Network

- For the hybrid equivalent model to be described, the parameters are defined at an operating point that may or may not give an actual picture of the operating condition of the amplifier. The quantities h_{ie} , h_{re} , h_{fe} and h_{oe} are called the *hybrid parameters* and are the components of a *small-signal equivalent circuit*. The description of the hybrid equivalent model begins with the general two-port system.

 Two-port system representation (Black model realisation)



$$V_i = h_{11}I_i + h_{12}V_o$$


$$I_o = h_{21}I_i + h_{22}V_o$$

- (i) $h_{11} \rightarrow$ input impedance $\rightarrow h_i$
- (ii) $h_{12} \rightarrow$ reverse transfer voltage ratio $\rightarrow h_r$
- (iii) $h_{21} \rightarrow$ forward transfer current gain $\rightarrow h_f$
- (iv) $h_{22} \rightarrow$ output admittance $\rightarrow h_o$

EQUIVALENT CIRCUITS THROUGH HYBRID PARAMETERS AS A TWO-PORT NETWORK


For the transistor, even though it has three basic configurations, they are all four-terminal configurations, and thus, the resulting equivalent circuit will have the same format. The *h-parameter* will however change with each configuration. To distinguish which parameter has been used or which is available, a second subscript has been added to the *h-parameter notation*.

 - (i) For the common-base configuration: the lower case letter b
- (ii) For the common-emitter configuration: the lower case letter e
- (iii) For the common-collector configuration: the lower case letter c




EXPRESSIONS OF CURRENT GAIN, INPUT RESISTANCE, VOLTAGE GAIN AND OUTPUT RESISTANCE

 
The h -parameter equivalent circuit of a transistor amplifier having a voltage source V_g , with its input resistance R_g connected to the input terminals and a load resistance R_L connected to the output terminals.




h -Parameter equivalent circuit of a transistor

Common Base Configuration

 

 


Fixed Bias Network

 



Steps

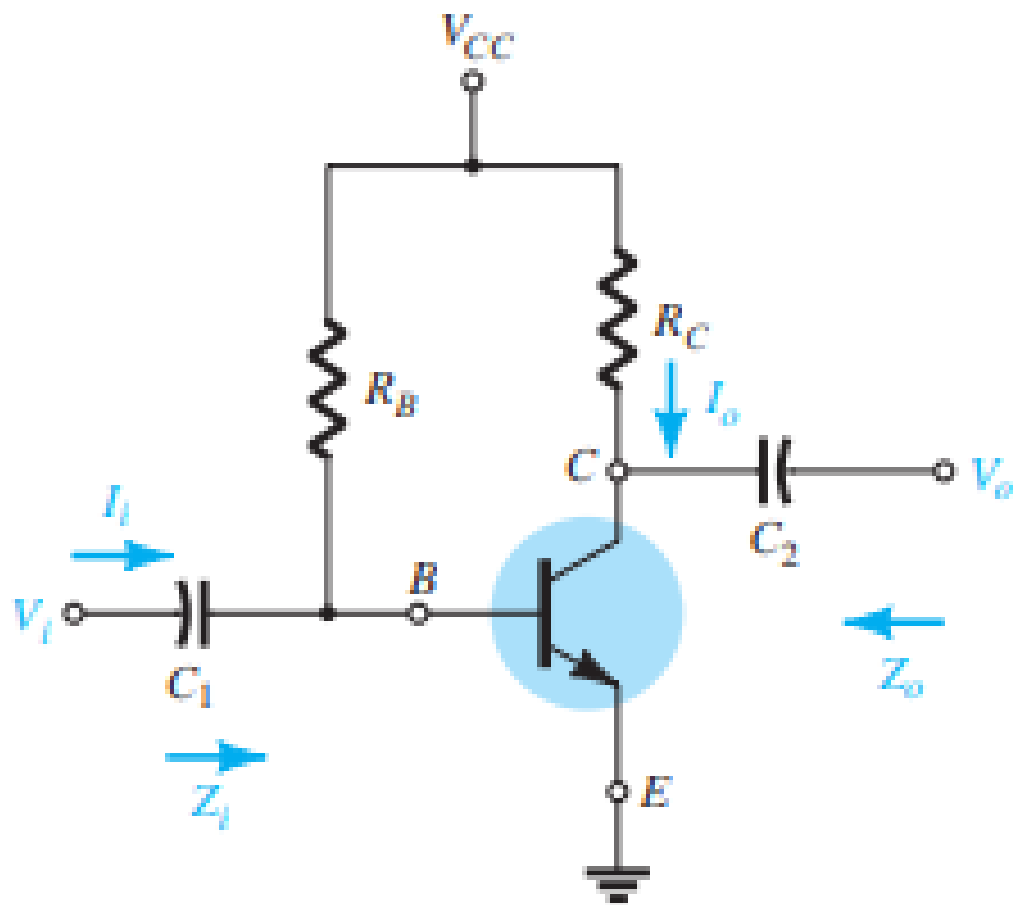- 1. Connect the DC source to ground
- 2. Replace all the capacitance with short circuit
- 3. Re draw the network
- 4. write the AC equivalent circuit
- 5. Determine input impedance, output impedance, voltage gain and current gain




Contd..

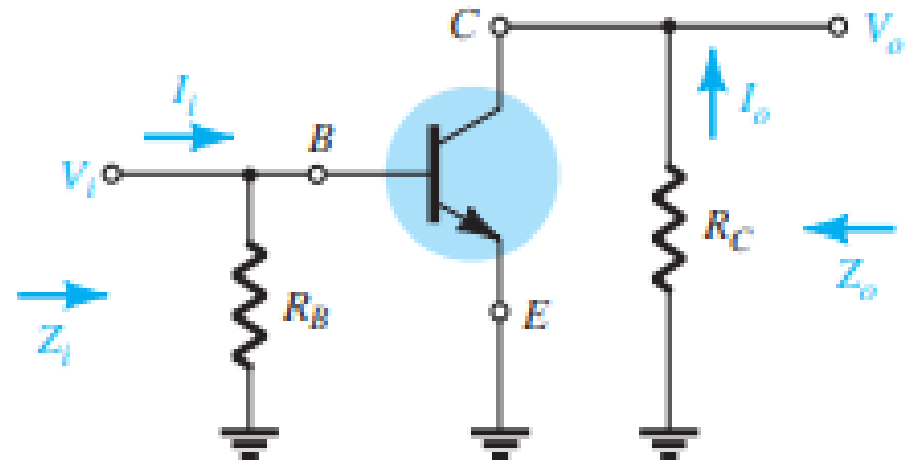

 

Contd..

 

$$Z_i = R_B \parallel h_{ie}$$

$$Z_o = R_C \parallel 1/h_{oe}$$

Using $R' = 1/h_{oe} \parallel R_C$, we obtain

$$\begin{aligned} V_o &= -I_o R' = -I_C R' \\ &= -h_{fe} I_b R' \end{aligned}$$


$$I_b = \frac{V_i}{h_{ie}}$$

$$A_v = \frac{V_o}{V_i} = -\frac{h_{fe}(R_C \parallel 1/h_{oe})}{h_{ie}}$$

A_i Assuming that $R_B \gg h_{ie}$ and $1/h_{oe} \geq 10R_C$, we find $I_b \cong I_i$ and $I_o = I_c = h_{fe}I_b = h_{fe}I_i$, and so

$$A_i = \frac{I_o}{I_i} \cong h_{fe}$$

 - For the network shown in figure determine
- Z_i , Z_o , A_v , A_i



$$Z_i = R_B \parallel h_{ie} = 330 \text{ k}\Omega \parallel 1.175 \text{ k}\Omega$$

$$\cong h_{ie} = \mathbf{1.171 \text{ k}\Omega}$$


$$r_o = \frac{1}{h_{oe}} = \frac{1}{20 \text{ }\mu\text{A/V}} = 50 \text{ k}\Omega$$

$$Z_o = \frac{1}{h_{oe}} \parallel R_C = 50 \text{ k}\Omega \parallel 2.7 \text{ k}\Omega = \mathbf{2.56 \text{ k}\Omega} \cong R_C$$

$$A_v = -\frac{h_{fe}(R_C \parallel 1/h_{oe})}{h_{ie}} = -\frac{(120)(2.7 \text{ k}\Omega \parallel 50 \text{ k}\Omega)}{1.171 \text{ k}\Omega} = \mathbf{-262.34}$$

$$A_i \cong h_{fe} = \mathbf{120}$$

Voltage Divider Bias Network

 

$$Z_i = R_1 \parallel R_2 \parallel h_{ie}$$

$$Z_o \cong R_C$$

$$A_v = -\frac{h_{fe}(R_C \parallel 1/h_{oe})}{h_{ie}}$$

$$A_i = \frac{h_{fe}(R_1 \parallel R_2)}{R_1 \parallel R_2 + h_{ie}}$$

$$Z_i = R_B \parallel \beta r_e \quad \text{ohms}$$

$$Z_o = R_C \parallel r_o \quad \text{ohms}$$

$$Z_i \cong \beta r_e \quad R_B \geq 10\beta r_e \quad \text{ohms}$$


$$Z_o \cong R_C \quad r_o \geq 10R_C$$

Contd..

$$V_o = -\beta I_b (R_C \parallel r_o)$$

$$I_b = \frac{V_i}{\beta r_e}$$
 
$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$



Contd..

$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}$$

$$A_v = -\frac{R_C}{r_e}$$

$$r_o \geq 10R_C$$