


8085 interfacing and Application

\* Basics of LCD interfacing :-

- In recent years the LCD is used widely as it replace LED's (7 segment LED display) this is due to the following reasons.

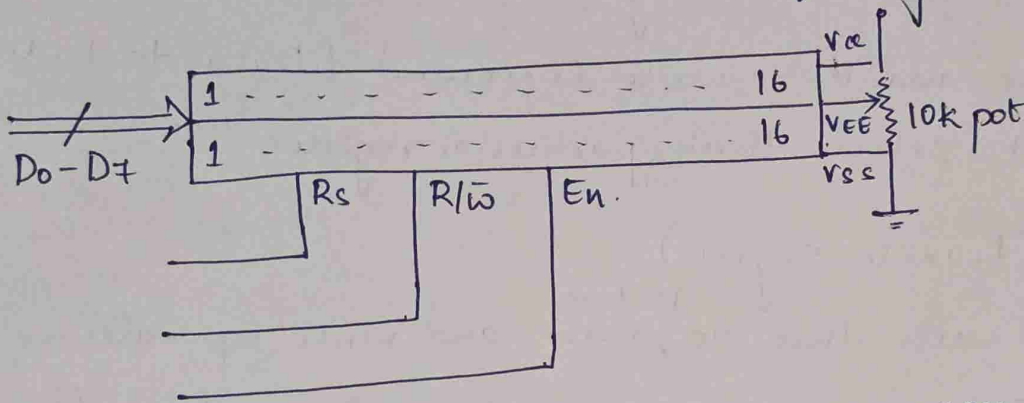1. declining prices of LCD.
2. Ability to display number, character, graphics
3. Ease of programming for character and graphics.

Here we consider a 16 x 2 LCD interfacing :-



- It has two rows and in each row we can display 16 char.
  - It has 8 bit data bus (Do-D7)
  - It has 3 control signal  $R_s$ ,  $R/\bar{w}$ ,  $En.$  (Register Select, Read/Write, Enable)
  - To change the brightness of LCD, 10k $\Omega$  potentiometer is connected to Vcc.
- pot has 3 terminals to connect
1. Connected to Vcc
  2. Variable terminal of pot connected to VEE
  3. Gnd terminal is connected to Vss
- By varying the resistance of the pot we can vary the brightness of the LCD

## \* LCD Control Signals.

- LCD has two internal resistance

1. Command register - user can store the Command  
Such as clear display, display on cursor on, Select  
LCD 16x2

2. Data register - user has to store the ASCII value  
of character that we want to display on LCD

- To select either of the two registers Rs control signal  
is used. Rs  $\rightarrow$  Register Select terminal.

Rs = 0 - Command reg is selected

Rs = 1 - Data register is selected

When ever we want to write Command / Data to LCD we  
have to first select that particular register.

- R/W (Read / Write signal)

we can use this to <sup>perform</sup> read and write operation

1. when R/W = 0 write operation is performed.

which means we can write Command / Data on to  
Command / Data Register.

2. when R/W = 1 - Read a Data / Signal from LCD.

- En (Enable) - when ever we want to latch a data which  
means, 1<sup>st</sup> we will place a Data / Command on  
Data bus i.e (D0 to D7) after that we need to send  
a Enable signal.

En = 1 - 0 pulse (make the signal high and  
after some delay or immediately make it back to low  
this will do the write operation.

So to write a program for LCD interfacing first we have to select Command register / Data register which is done by using Rs control signal

2. place Data on Data bus D0 to D7
3. Select the operation to be performed i.e.  $R\bar{L}\bar{0}$
4. Latch the Data / Command by sending high to low pulse on Enable signal.

\* Commands of LCD:-

Various no of Commands are available for LCD Such as.

- 1 - Clear display screen.
- 2 - Return home
- 4 - Decrement cursor (Shift left)
- 6 - Inc cursor (Shift right)
- 5 - Shift display right and so on.

But generally 3 Commands are used in almost all the programs they are.

1. 38h → used to select LCD of 2 rows of 5x7 matrix Display which means to display each character on LCD Dot matrix pattern 5x7 is used.

2. 0Eh → used to display ON, Cursor ON.

3. 01h → Clear display.

- Before displaying any data on LCD we can send this Command to clear the previous display data on LCD
- generally the sequence of the Command written is Same as mention above (1, 2, 3)

Next important commands for LCD is related to address of character. As we are using 16x2 LCD we will have 16 characters that will be displayed on one row

∴ each character will have its own address  
 the add of 1st row starts from 80h, 2nd row = C0h.


80h	81h	82h				
C0h	C1h	C2h				

- therefore to display character at one particular position first we have to write address of that particular position in Command register

Ex: 90D → I want display <sup>starting</sup> from character address 82h

82h	83h	84h
9	0	D

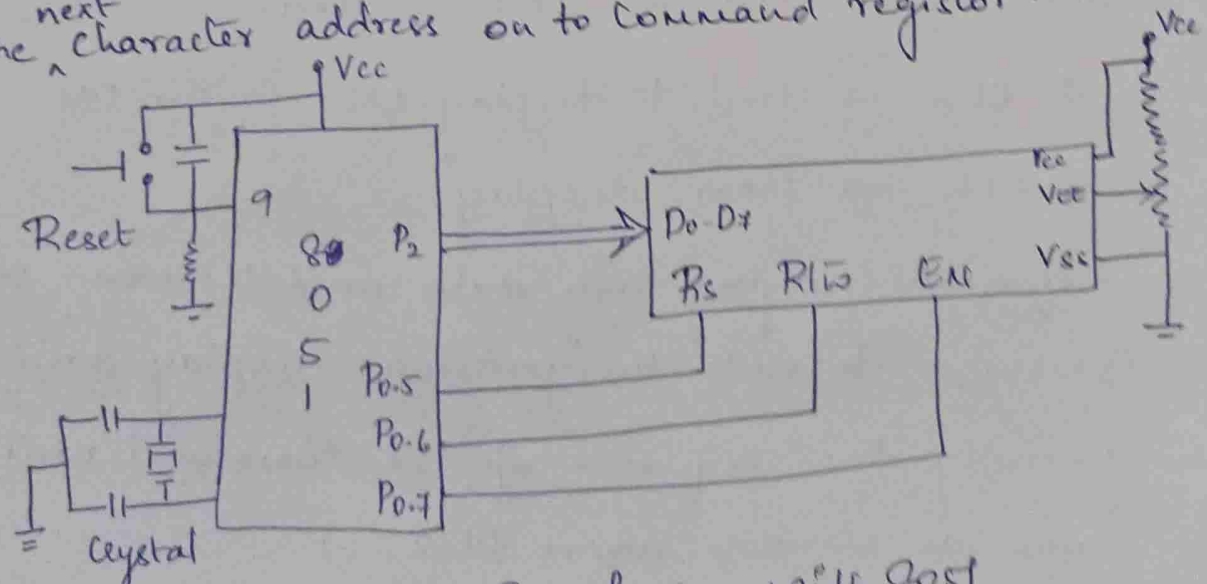1. first write 82h in Command register
2. Send ASCII value of 9 and write it onto Data reg.
3. After writing 9 at 82h automatically cursor position will be incremented by 1 & cursor will point to next position. hence it is not necessary to write the <sup>next</sup> character address on to Command register.



LCD Interfacing With 8051

flow chart:- We will write a program to display a string on LCD using assembly level language. (3)

- We have 8051, reset CRT to reset the device.  
Crystal Oscillator which is connected externally

- Interfacing part of 8051 and LCD is shown

- here D<sub>0</sub> to D<sub>7</sub> is connected to Port 2

Any ports can be used to do the Interfacing.

- R<sub>s</sub> (Register select) which is connected to P<sub>0.5</sub>

- R<sub>W</sub> (Read/Write) is connected to P<sub>0.6</sub>

- E<sub>n</sub> (Enable) is connected to P<sub>0.7</sub>

- we have connected a pot to alter the brightness of the LED.


1. Write a ALP to display a string on the first row of LCD.

\* To write a program we use the concept of lookup table to store the data / string.

the format for this is

String: DB 'HELLO', 0  
→ stores the 8bit value of each character in memory location  
→ end of the string.

 \* Once the ASCII value of 1<sup>st</sup> char is read on to Data Register, pointer is ↑ to the next location.




\* there by every time the value is read from the memory location to which the pointer is pointing and then compare that value with zero. If not equal display the value if equal end the display program.


use pointer which will point to the memory location where 1<sup>st</sup> char is stored

Flow chart :- we use 3 sub routine 1. Delay 2. LCD-Command. 3. LCD-Data → writes data in Data register

flow chart for LCD-Command.

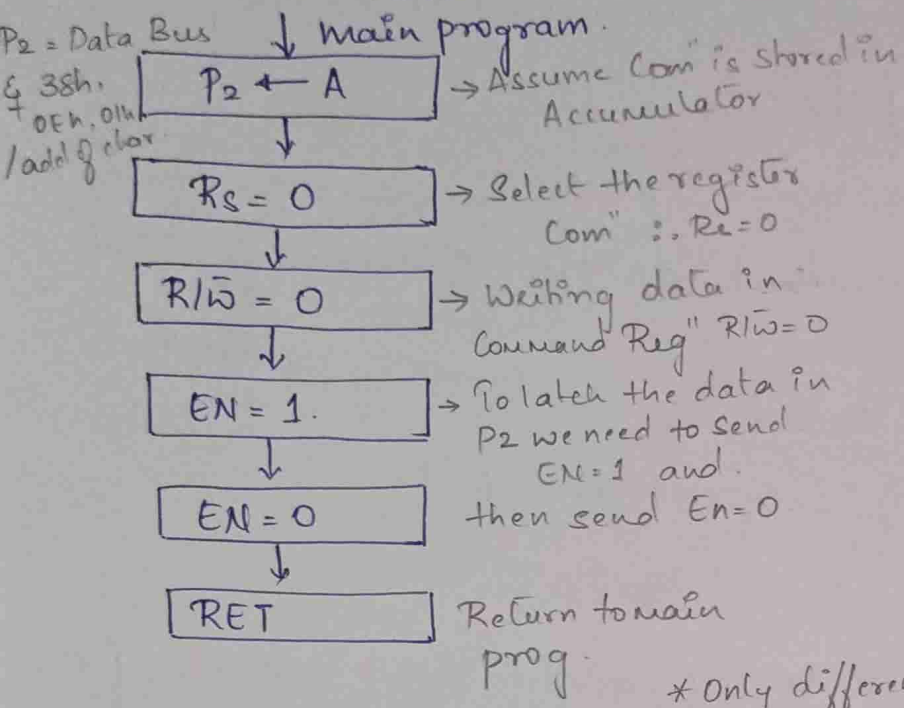


LCD-Data ASCII value

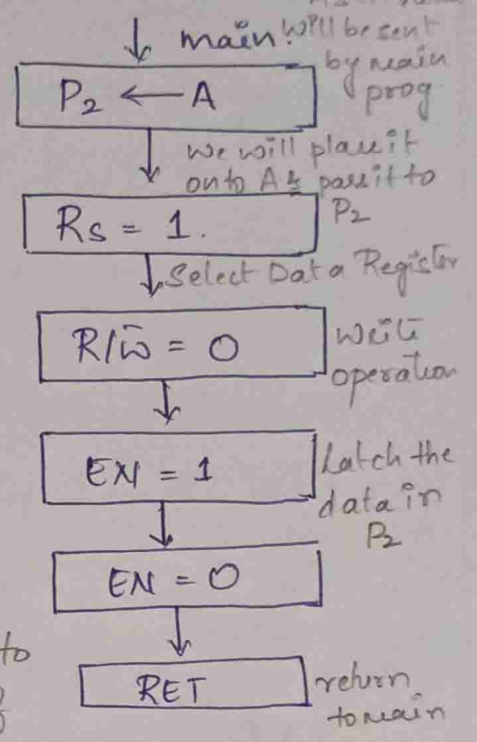


\* main program :-

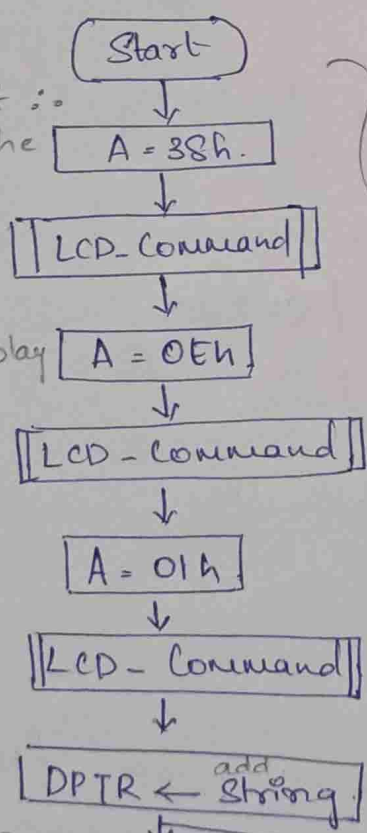- Initial the LCD first :- Send A = 38h, Select the 16x2 display
- Store it in A and call Subroutine LCD-Comm
- A = 0Eh - used to display the cursor ON
- Call Subroutine LCD-Comm
- A = 01h - clears the display
- Call Subroutine LCD-Comm





\* Only difference is to select the type of register

initialize

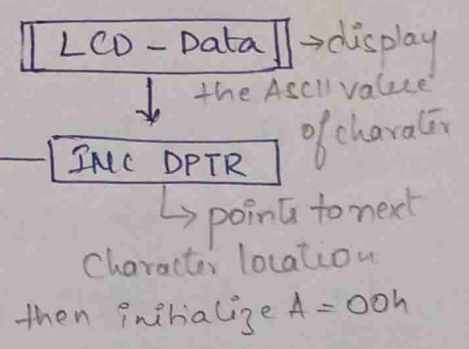

  \* If we want to specify any address to display a char we can use the above command, initialize



- we want write data in data register i.e ASCII value of string  
 - we know we are storing the string  
 - String : DB 'HELLO', 0 - last inst ends with 0  
 - this inst will write the HELLO on to flash memory  
 - to read data from flash - MOVC A, @A+DPTR → point to string

A = address (80h, 82h, C0h, C1h) and then call LCD-command.

① Write a ALP program to Send Command and data to LCD with a time delay. (4)

- ; P2.0 to P2.7 are connected to LCD data pins D<sub>0</sub> to D<sub>7</sub>
- ; P0.5 is connected to R<sub>s</sub> pin.
- ; P0.6 is connected to R<sub>I</sub> $\bar{W}$  pin.
- ; P0.7 is connected to E pin.

Org 00h.

MOV A, #38h → Init. LCD 2 lines, Selects 16x2 display.

ACall LCD\_Command → Calls Subroutine to write Command.

ACall Delay → Apply time delay.

MOV A, #0Eh → LCD turns ON and cursor ON.

ACall LCD\_Command → Calls Subroutine.

ACall Delay → Apply time delay.

MOV A, #01h → Clear the previous display.

ACall LCD\_Command → Calls Subroutine.

ACall Delay → Apply time delay.

MOV A, #84h → Cursor in line 1, position 4

ACall LCD\_Command → Calls Subroutine.

ACall Delay → Apply time Delay.

MOV A, # "0" → display letter '0'

ACall LCD\_Data → Call Subroutine to write Data.

ACall Delay → Apply time delay.

MOV A, # 'N' → display letter 'N'

ACall LCD\_Data → Call Subroutine.

ACall Delay → Apply Delay.

Again: Sjmp Again → Stay here.

↪ Subroutine to send Command to LCD.

LCD\_Command: MOV P<sub>2</sub>, A → Content of A → Port 2.

CLR P0.5 → R<sub>s</sub>=0; Command Register selected

CLR P0.6 → R<sub>I</sub> $\bar{W}$ =0; to write

SETB P0.7 → E=1; latch the Data in Port 2

ACall Delay  $\rightarrow$  Apply time delay.

CLR P0.7  $\rightarrow$  E=0

RET  $\rightarrow$  Return to main program.

LCD-Data: MOV P2, A  $\rightarrow$  Content of A to Port 2.

SETB P0.5  $\rightarrow$  Rs=1 ; Select Data Register.

CLR P0.6  $\rightarrow$  Rlw=0 ; write Data.

SETB P0.7  $\rightarrow$  E=1 ; latch the Data in Port 2

ACall Delay  $\rightarrow$  Apply time delay.

CLR P0.7  $\rightarrow$  E=0

RET  $\rightarrow$  Return to main program.

Delay: Mov R3, #0FFh  $\rightarrow$  Max value 255  $\rightarrow$  R3.

L2: MOV R4, #0FFh  $\rightarrow$  255  $\rightarrow$  R4

Here: DJNZ R4, Here  $\rightarrow$  Stay till R4 = 0

DJNZ R3, L2  $\rightarrow$  stay till R3 = 0

RET  $\rightarrow$  Return to main program.

End.

2. Write a Program to display string "HELLO WORLD" on 16x2 LCD using 8051.

Org 00h

MOV A, #38h

ACall LCD-Command.

MOV A, #0EH

ACall LCD-Command.

MOV A, #01h.

ACall LCD-Command.

MOV A, #82h  $\rightarrow$  Curson in line 1, position 2.

ACall LCD-Command.

MOV DPTR, #String  $\rightarrow$  Assign DPTR with the content of string where Data that has to be displayed is stored.

Back: MOV A, #00h  $\rightarrow$  00 + add "1 char"

MOVC A, @A+DPTR

Copy the data from memory location to A

initialization of LCD.

Point DPTR to string look up table.

1 char add" will be stored in DPTR

of string where Data that has to be displayed is stored.



JZ exist → Jump if A=0 to exist

(5)

ACall LCD-Data → ASCII value will be written on A and the

INC DPTR → next character. data will be displayed on LCD.

~~back~~ SJMP back → jump to back

exist: SJMP exist. → stay here.

LCD-Command: ACall delay.

MOV P<sub>2</sub>, A

CLR P<sub>0.5</sub>

CLR P<sub>0.6</sub>

SETB P<sub>0.7</sub>

CLR P<sub>0.7</sub>

RET

LCD-Data: ACall delay.

MOV P<sub>2</sub>, A

SETB P<sub>0.5</sub>

CLR P<sub>0.6</sub>

SETB P<sub>0.7</sub>

CLR P<sub>0.7</sub>

RET

Delay: MOV R<sub>3</sub>, #0FFh

l<sub>2</sub>: MOV R<sub>4</sub>, #0FFh.

Here: DJNZ R<sub>4</sub>, Here.

DJNZ R<sub>3</sub>, l<sub>2</sub>

RET

String: DB 'HELLO WORLD', 0

End.

## \* Interface ADC and DAC with 8051 micro controller :-

1. ADC devices :- Devices which are used to convert analog signal to digital signal.

ADC devices are most widely used for data acquisition.

- In physical world everything is analog & temp, velocity, pressure etc need to be converted to digital number so that the micro controller can read and process the info provided.

- ADC has  $n$  bit resolution, where  $n = 8, 10, 12, 16, 24$  bits. High resolution ADC will have smaller step size.

Step Size = smallest change that can be detected by an ADC.

$n$	No of step	Step size.
8	256	$5/256 = 19.53 \text{ mV}$
10	1024	$5/1024 = 4.88 \text{ V}$
12	4096	1.2 mV
16	65536	0.076 mV

$$5 = V_{cc}$$


- Apart from resolution, Conversion time is another major factor in ADC.

Conversion time = time taken by ADC to convert analog i/p to a digital number.

- ADC chips are of two kinds.   
 1. Parallel      2. Serial.   
  $\rightarrow$  only one pin for data out.   
  $\rightarrow$  8 or more dedicated pins to bring out binary data.

# 1. Parallel ADC (0804) chip

- It is a 8bit parallel ADC in the family of ADC08000 Series from National Semiconductors.
- It works on +5Volt and has a resolution of 8bits.
- Conversion time depends on the clocking signal applied at the clk in pin. (It cannot be faster than 10µs).

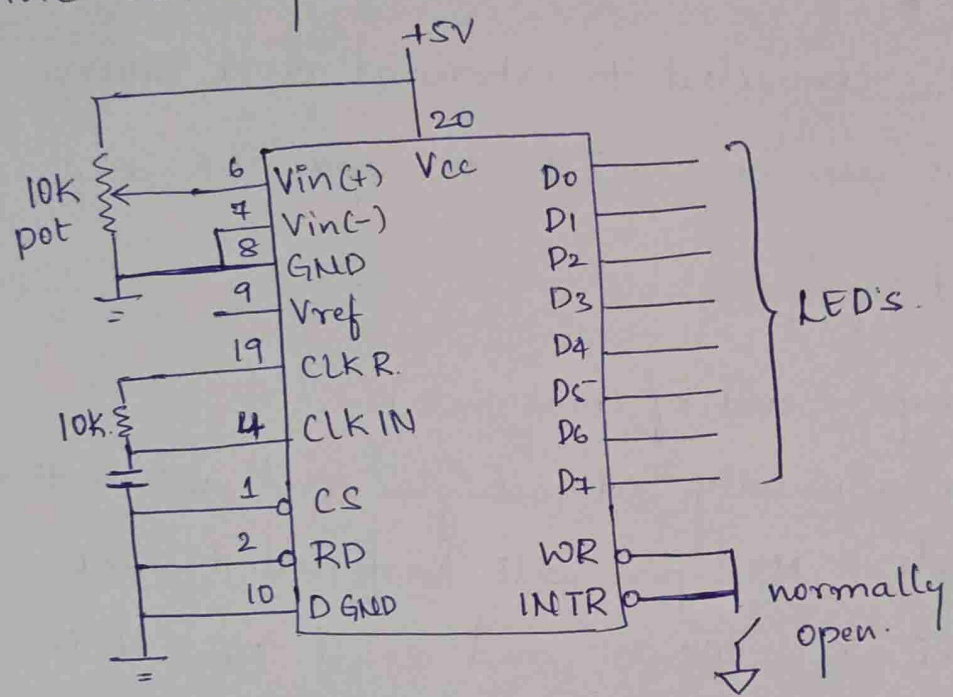

ADC0804

## 1. CS → Chip Select

this pin has to be set to low to activate the ADC chip.

## 2. RD → Read data.

- ADC converts the analog i/p to its binary equivalent and stores the data in internal Register.
- RD is used to get the converted data out of ADC when CS=0, if a high to low pulse is applied at RD, then digital o/p shows up at D0 - D7 data pins.
- It is also referred as O/p enable (OE).

3. WR (Write / Start Conversion).

- If  $CS=0$  & WR = low to high pulse.

then ADC starts to convert analog i/p value  $V_{in}$  to a 8bit digital number.

- time taken to convert depends on CLK IN & CLK R values.

4. CLK IN & CLK R

- clock pins connected to external clock source

- these pins are connected to capacitor and resistor

$$\therefore f = \frac{1}{1.1 RC}$$

5. INTR (Interrupt / end of conversion):-

- This pin is usually set to high and when the conversion ends INTR pin will be forced to zero.


- once  $INTR=0$ ,  $CS=0$  and send high to low pulse to RD to get the data out of ADC chip.

6.  $V_{in(+)}$  &  $V_{in(-)}$


two different analog i/p

$$V_{in} = V_{in(+)} + V_{in(-)}$$

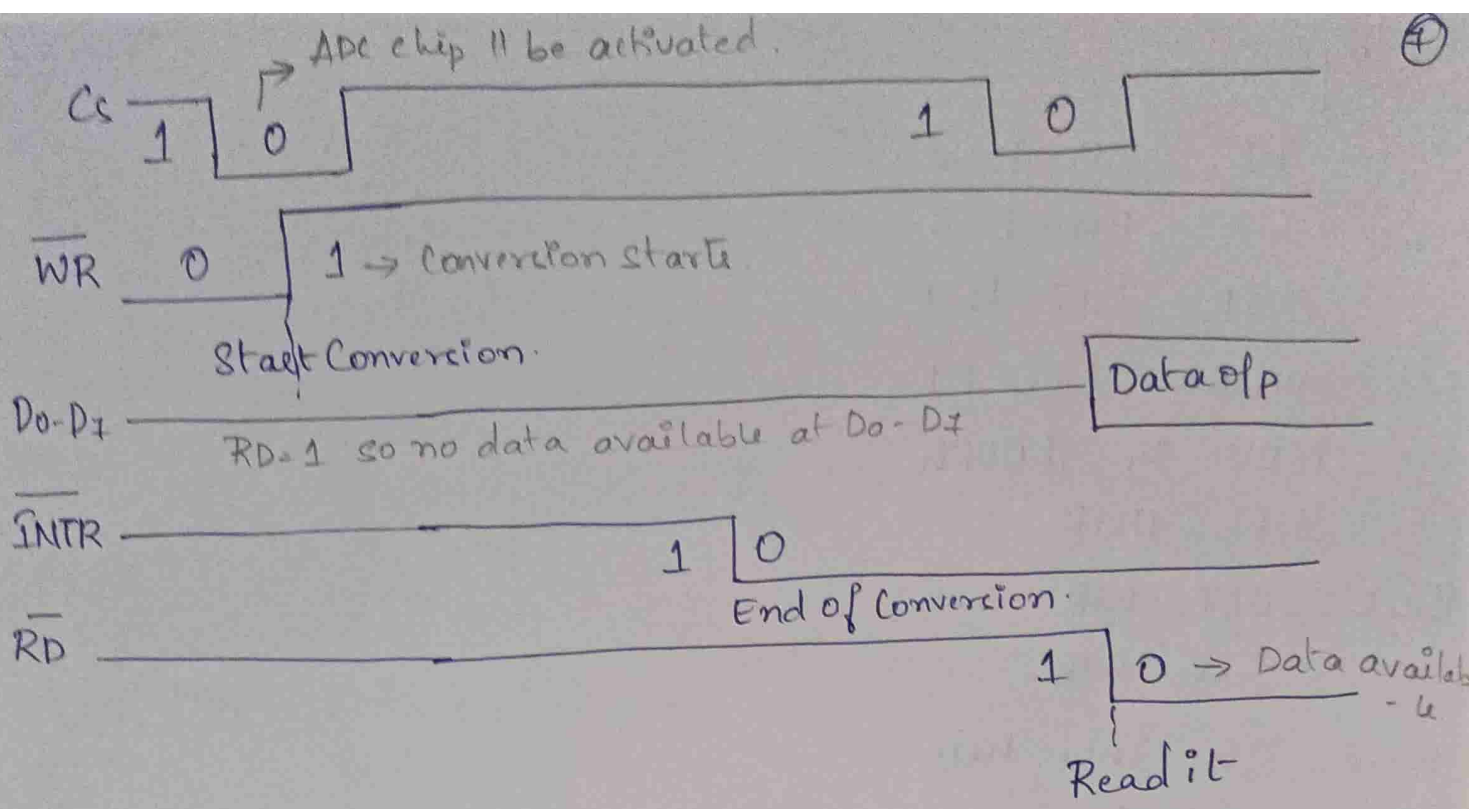$V_{in(-)}$  is connected to ground &  $V_{in(+)}$  is used as analog i/p to convert to digital.



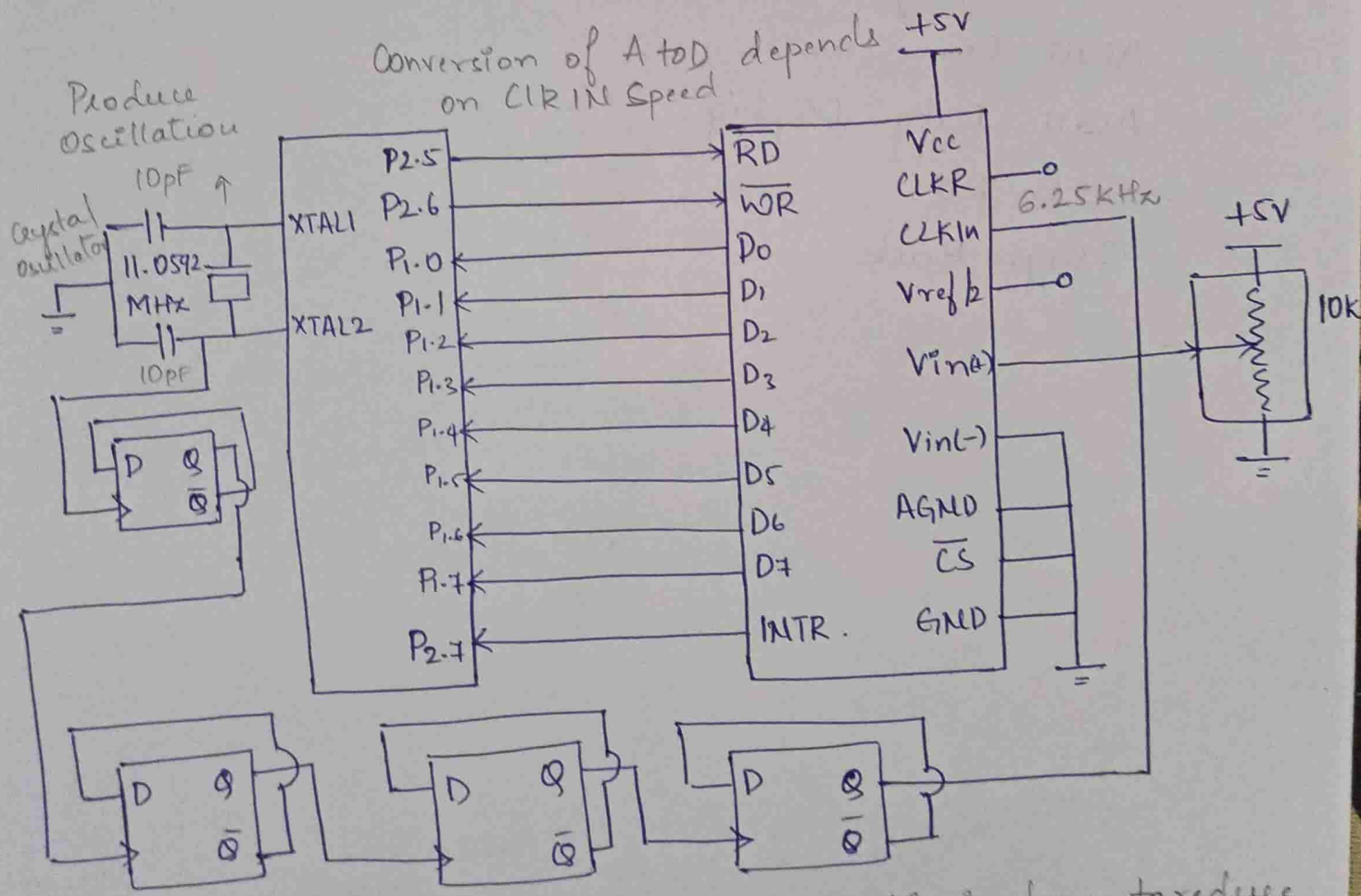\* Connection to ADC0804 with clock from external clock



this is done to reduce 4 to 5 D flip flops are used. - the speed of the external clock so that we get the correct speed of the clock.

ADC chip.

D flip flop divides the frequency by 2.


Program: -

```
RD    BIT P2.5  
WR    BIT P2.6  
INTR  BIT P2.7  
MYData EQU P1.  
MOV  P1, #0FFh.  
Setb INTR.
```

Back: CLR WR  
Setb WR.

here: JB Intr, here.
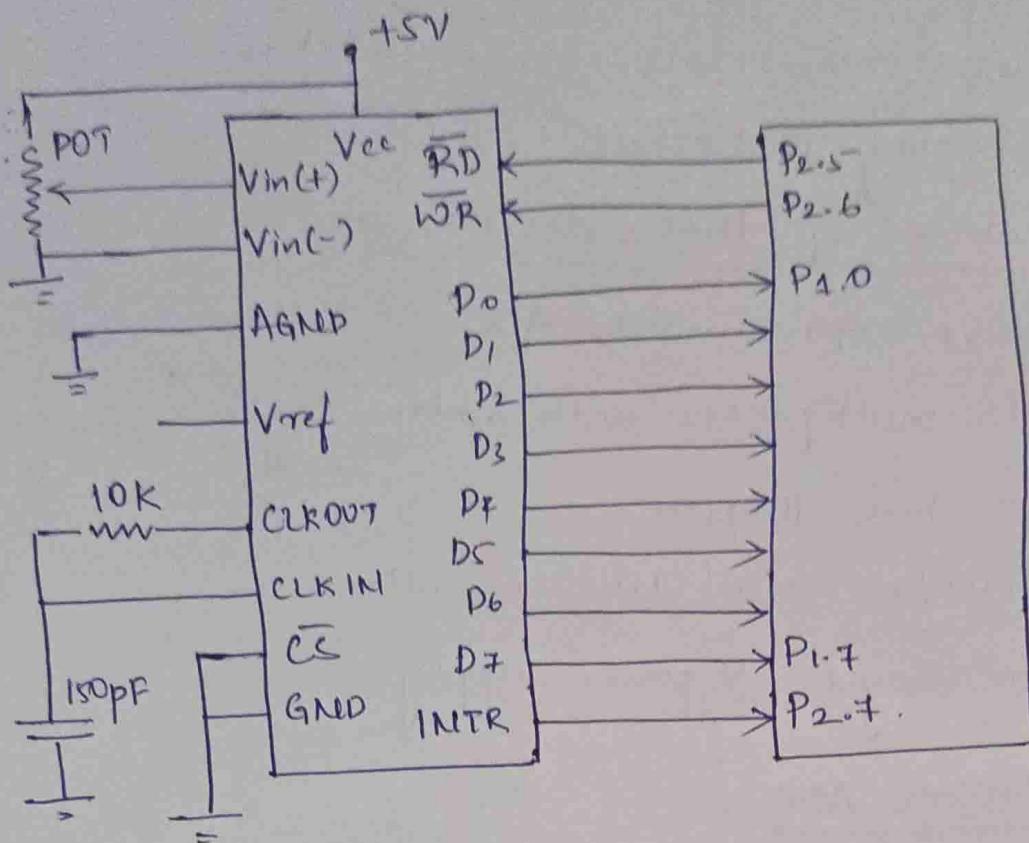
```
CLR RD  
MOV A, Mydata.  
Acall Convercion.  
Acall Data-Display.  
SetB RD  
SJmp Back.
```



AD Conversion program :-

MOV P1, #0FFH ; P1 configured as i/p port.

Back: CLR P2.6 ;  $\overline{WR} = 0$

ACALL Delay ; call the Delay

SETB P2.6 ;  $\overline{WR} = 1$ . → indicates the start of conversion.

Again: JB P2.7, Again ; P2.7 = 1 wait for the conversion to end.

CLR P2.5 ;  $\overline{RD} = 0$  - enable the read operation.

MOV A, P1 ; Read the data to port 1.

SETB P2.5 ;  $\overline{RD} = 1$  - disables the reading operation.

SJMP back ; go for the next conversion cycle.

\* ADC 0808 / 0809 family :-


- then a monolithic CMOS devices with 8-channel multiplexer.

- they are designed to operate from a common microcontroller control bus, with tristate o/p latch driving data bus.

the main features of these device are.

- 8bit Successive approximation ADC.
- 8-channel multiplexer with address logic.
- Conversion time 100µsec.
- Easy to interface to all microcontrollers.
- Operates on single 5V power supply.

Pin diagram of 0808 ADC.

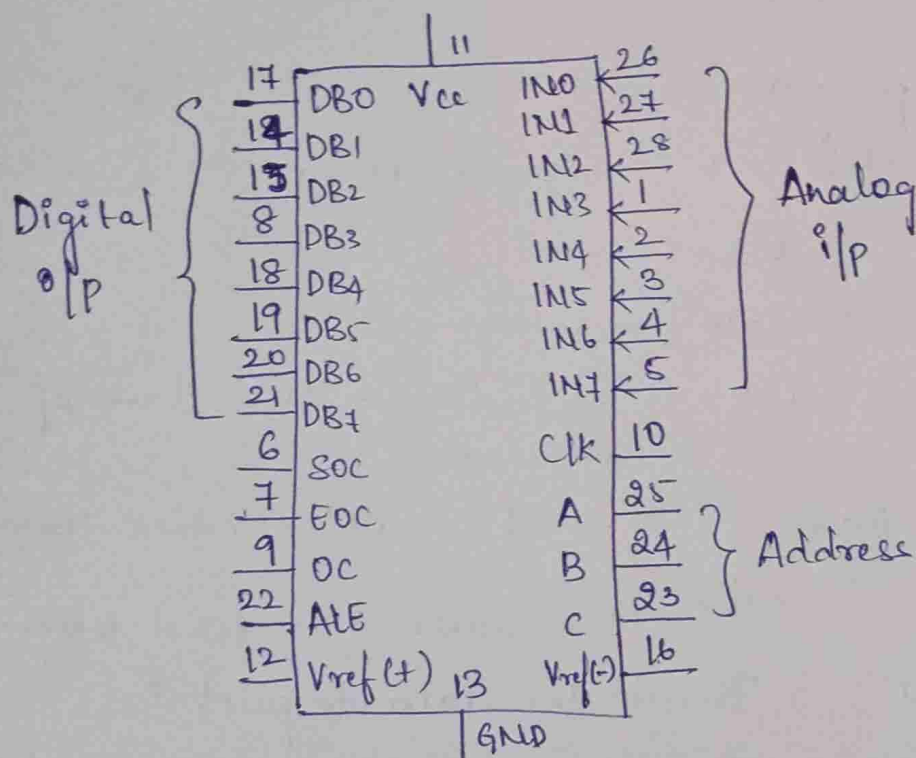


- It has 8 i/p channels, to select desired i/p channel it is necessary to send 3bit address on ABC i/p pins.

- the Analog i/p is sent through Desired channel and the address of the i/p line is latched by sending ALE signal - low to high.




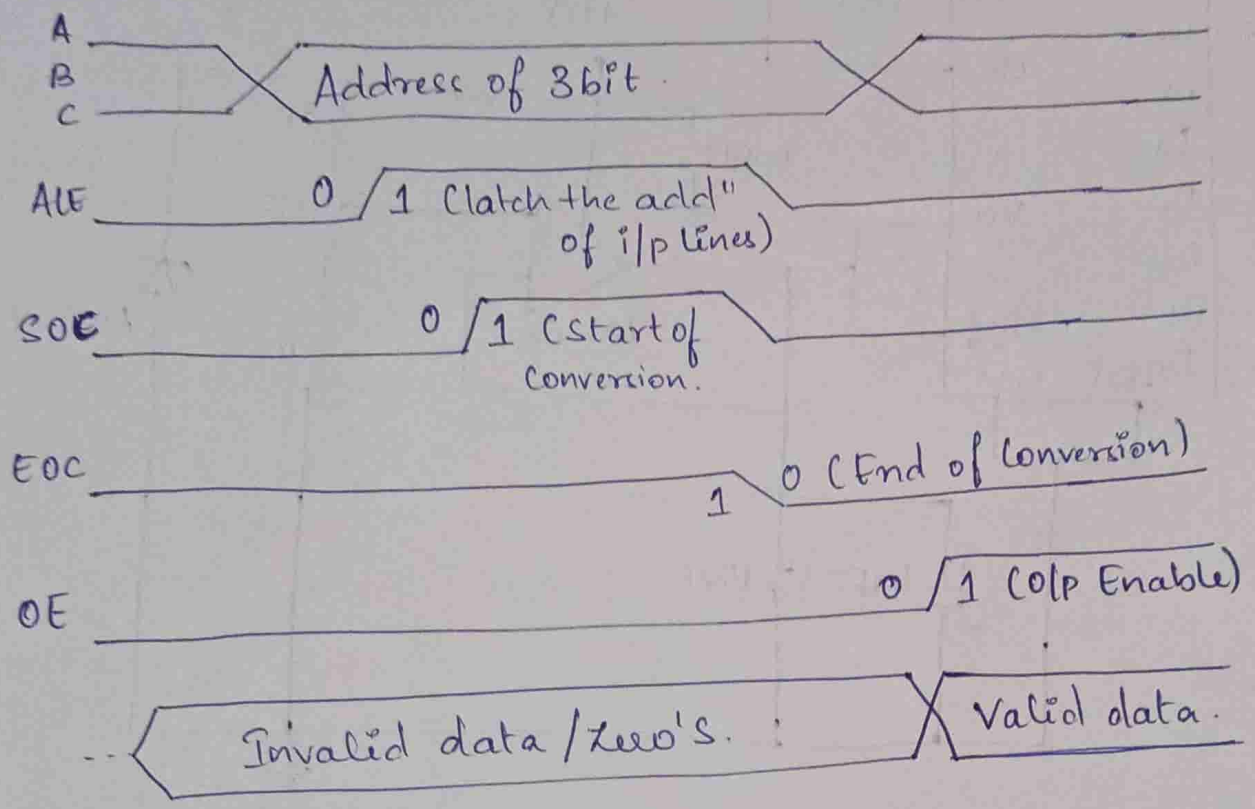- To indicate start of conversion SOC must be switched from high to low.
- Once the conversion is completed EOC [End of Conversion] must be forced from high to low.
- the converted digital o/p can be read through databus by enabling the o/p control pin (OE=1) after EOC is activated.



Ex Interface 8bit, 8channel ADC to 8051. Write asp to convert ch0, ch3, ch7 and store result in external memory location starting from C000h. Repeat procedure by giving delay.

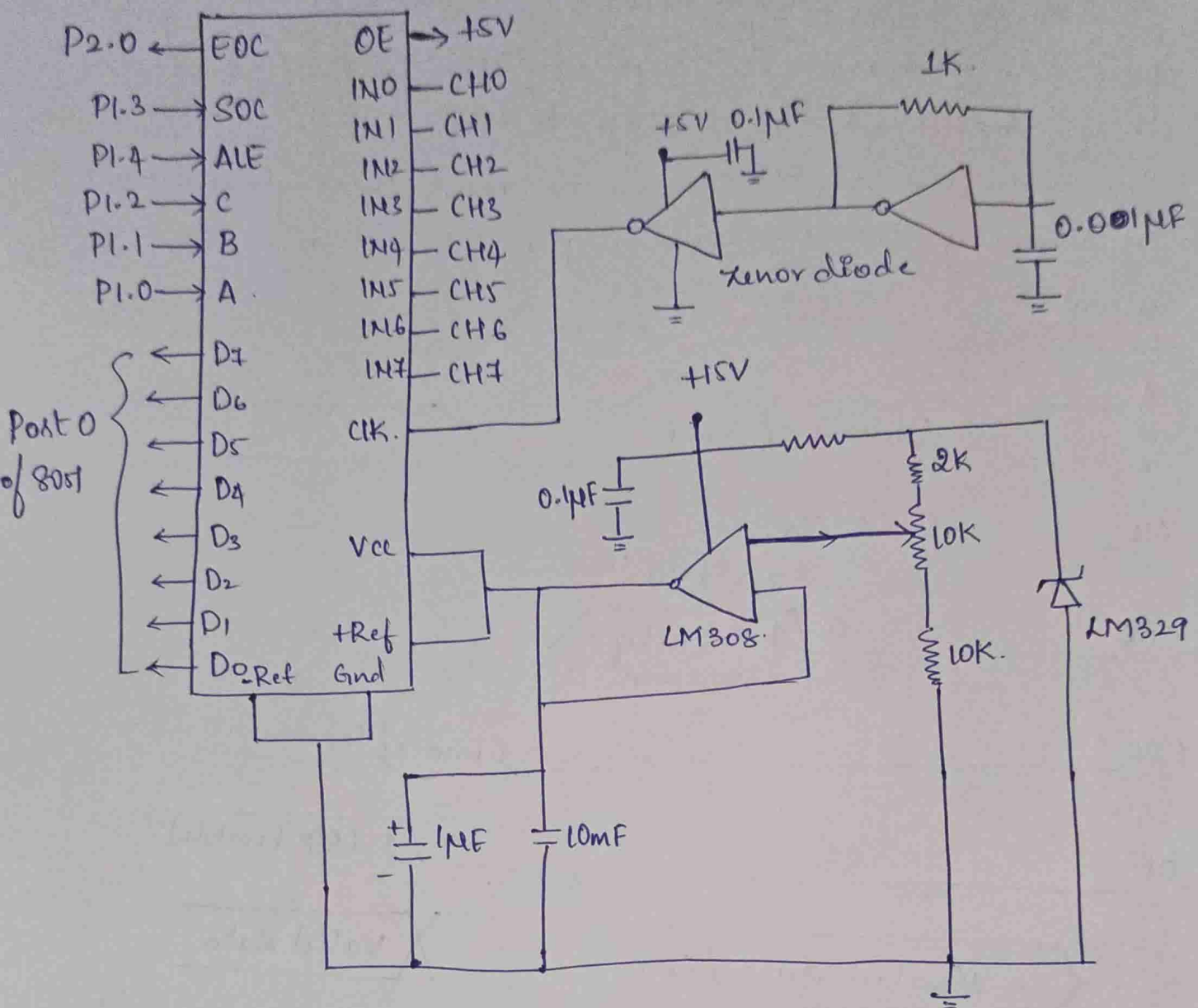- Step 1: Send 3bit address on ~~ADC~~, B, A [PI.2, PI.1, PI.0]
- Step 2: provide delay ALE - ~~low~~ high to low.
- Step 3: SOE - high to low start conversion.
- Step 4: EOC - activate  
Send converted data.



Program :-

CLR P1.3 → Make SOC low.

CLR P1.4 → Make ALE low.

MOV P0, #0FFh → P0 as i/p port.

MOV P2, #0FFh → P2 as i/p port.

Back: MOV DPTR, #0C000h → memory pointer.

MOV A, #00h → Set address for CH0

ACall R\_ADC → Call ADC Sub routine.

MOVX @DPTR, A → Converted data to DPTR location

INC DPTR → Increment DPTR.

ACall Delay. → Call Delay Subroutine.

```

MOV A, #03h
ACall R-ADC
MOVX @DPTR, A
INC DPTR.
ACall Delay

```

Conversion of i/p data at channel 3.

```

MOV A, #07h.
ACall R-ADC
MOVX @DPTR, A
INC DPTR.
ACall Delay.

```

Conversion of i/p data at channel 7.

Sjmp back → Repeat.

```

R-ADC: MOV P1, A → get channel no and set its add"
SetB P1.4 → ALE = 1 (latch the address)
NOP → Pulse delay.
CLR P1.4 → ALE = 0
SetB P1.3 → SOC = 1 (start of conversion)
NOP → Pulse delay.
CLR P1.3 → SOC = 0

```

Wait : JB P2.0, wait → wait till EOC = 0.

~~wait1: JNB P2.0, wait~~

MOV A, P0. → get digital data onto A


RET. → Return to main program.

\* Interfacing DAC to 8051


Under this we are going to interface DAC 1408, 8bit R/2R ladder type DAC with 8051.

- It is compatible with TTL and CMOS logic.

Pin diagram:-

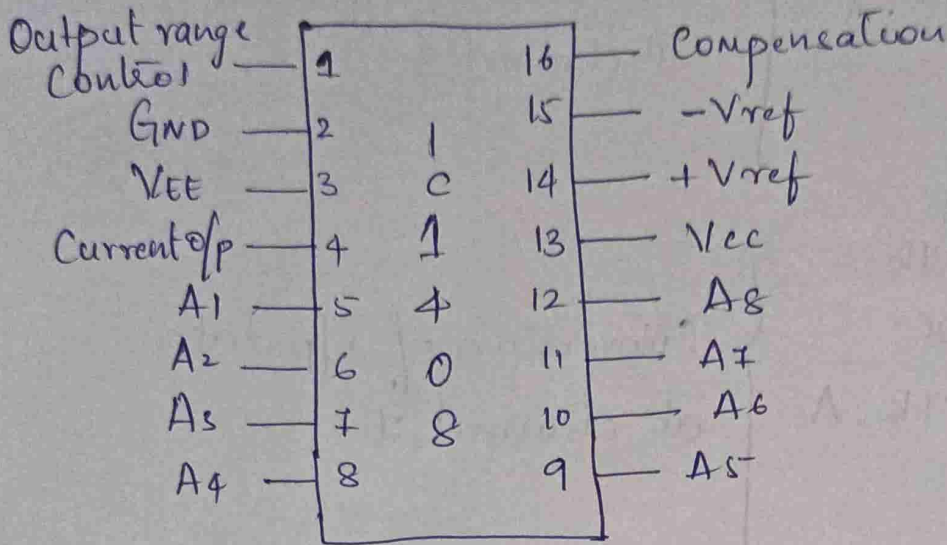


Block diagram:-

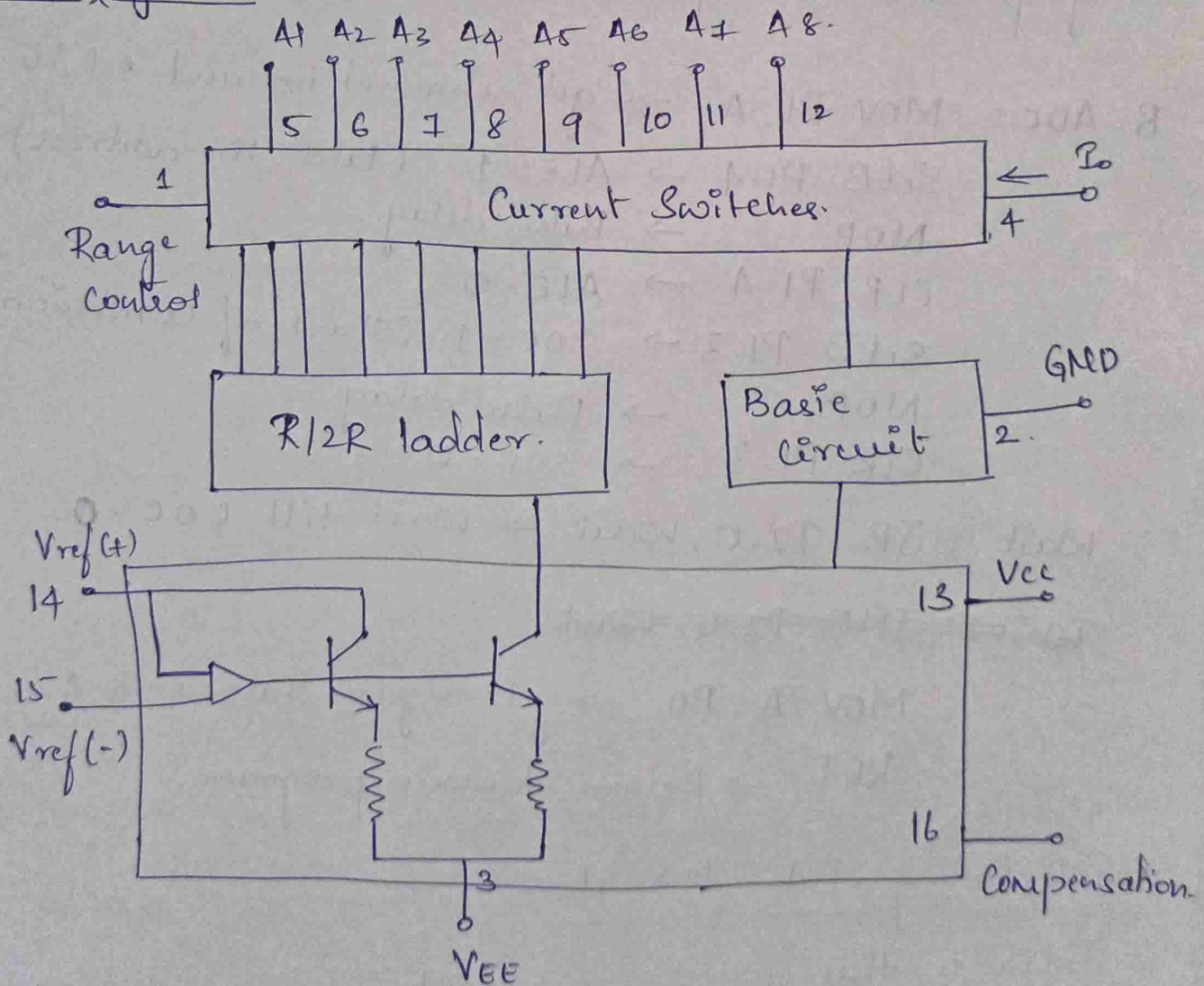

- 1408 consist of reference current amplifier.  
R/2R ladder, 8 high speed current switch

- It has 8 i/p data lines  $A_1$  (MSB) to  $A_8$  (LSB) which control the position of current switches.
- It requires 2mA reference current from full scale i/p two power supply  $V_{CC} = +5V$ ,  $V_{EE} = -15V$

Typical circuit for IC 1408.

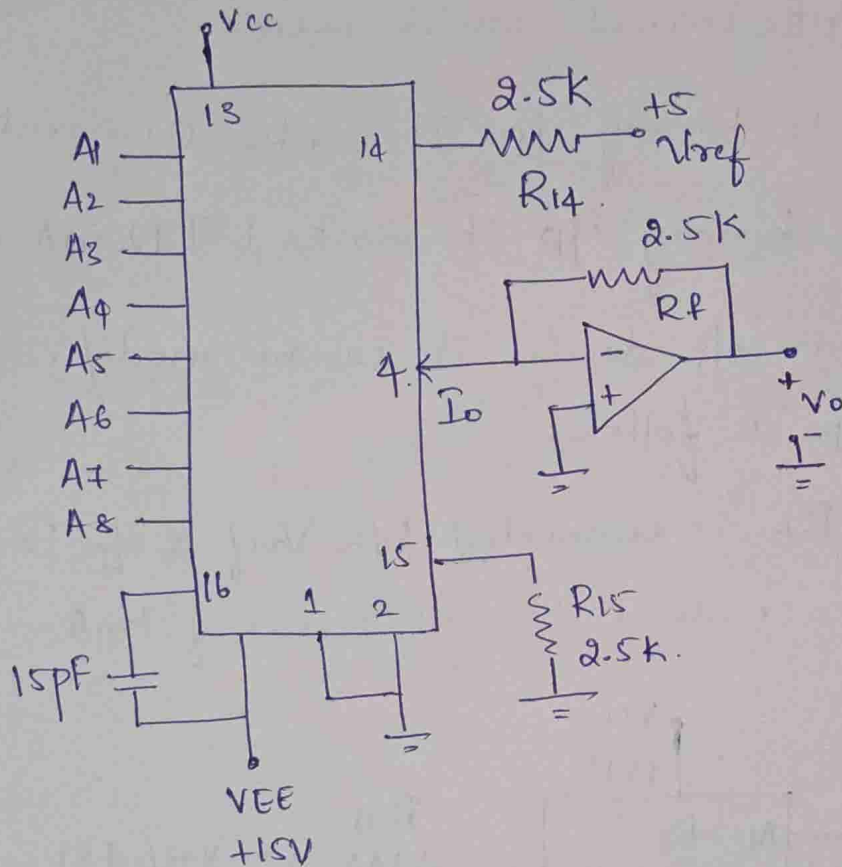

- $V_{ref}$  and  $R_{14}$  determines the total reference current source. and  $R_{15} = R_{14}$  to match the i/p impedance of the reference current amplifiers.

$\therefore$  o/p current  $I_o$  is given by.

$$I_o = \frac{V_{ref}}{R_{14}} \left[ \frac{A_1}{2} + \frac{A_2}{4} + \frac{A_3}{8} + \frac{A_4}{16} + \frac{A_5}{32} + \frac{A_6}{64} + \frac{A_7}{128} + \frac{A_8}{256} \right]$$

i/p  $A_1$  through  $A_8$  can be either 0 or 1.  $\therefore$  full scale current

$$I_o = \frac{5}{2.5k} \left[ \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \frac{1}{32} + \frac{1}{64} + \frac{1}{128} + \frac{1}{256} \right]$$

$$= \frac{2\text{mA} \times 255}{256} = 1.992\text{mA}$$

the o/p voltage for full scale i/p is given by.

$$V_o = 1.992 \times 2.5\text{k} = 4.98\text{V}$$

- Arrow on pin 4 is inwards. this means.


IC 1408 sinks current, which means;

At  $(0000\ 0000)_2$  binary i/p it sinks 0 current

At  $(1111\ 1111)_2$  binary i/p it sinks 1.992mA current.

- It is a unipolar o/p device it can be modified to get a bipolar o/p as follows.

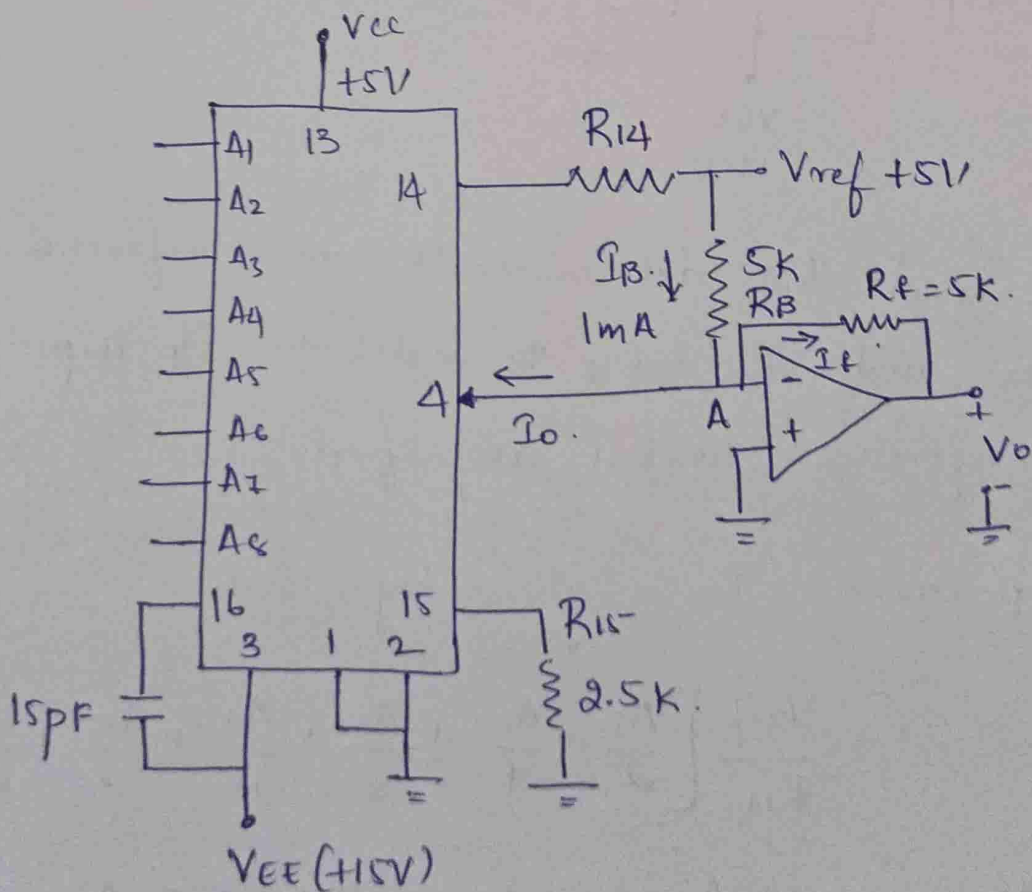A resistor  $R_B$  is connected b/w  $V_{ref}$  & o/p terminal, which gives a constant current source of 1mA.



Operation can be observed for three condition. (12)

1. Binary i/p (00H)

When i/p = 00h o/p current  $I_o$  @ pin 4 = 0.

Due to current flow in  $R_B$ , the same flows through  $R_A$  giving  $V_o = -5V$ .

$$V = V_{ref} \left[ \frac{0}{2} + \frac{0}{4} + \dots \right]$$

2. for Binary i/p 80h. [1000 0000]

i/p = 80h, o/p current  $I_o = 1mA$ . By applying

KCL at node A. we get.

$$-I_B + I_o + I_f = 0.$$

$$I_B = 1mA$$

$$I_o = 1mA$$

$$-(1mA) + (1mA) + I_f = 0$$

$$I_f = 0.$$

$\therefore$  o/p Voltage is zero.

3. for Binary i/p FFh. [1111 1111]

o/p current  $I_o = 2mA$ , apply KCL @ node A.

$$-I_B + I_o + I_f = 0$$

$$-1mA + 2mA + I_f = 0$$


$$I_f = -1mA.$$

$\therefore$  o/p voltage is +5V hence o/p is Bipolar.

\* Interfacing D/AE 1408 / D/AE 0808 with 8051

- microcontroller generates o/p which is in the digital form.

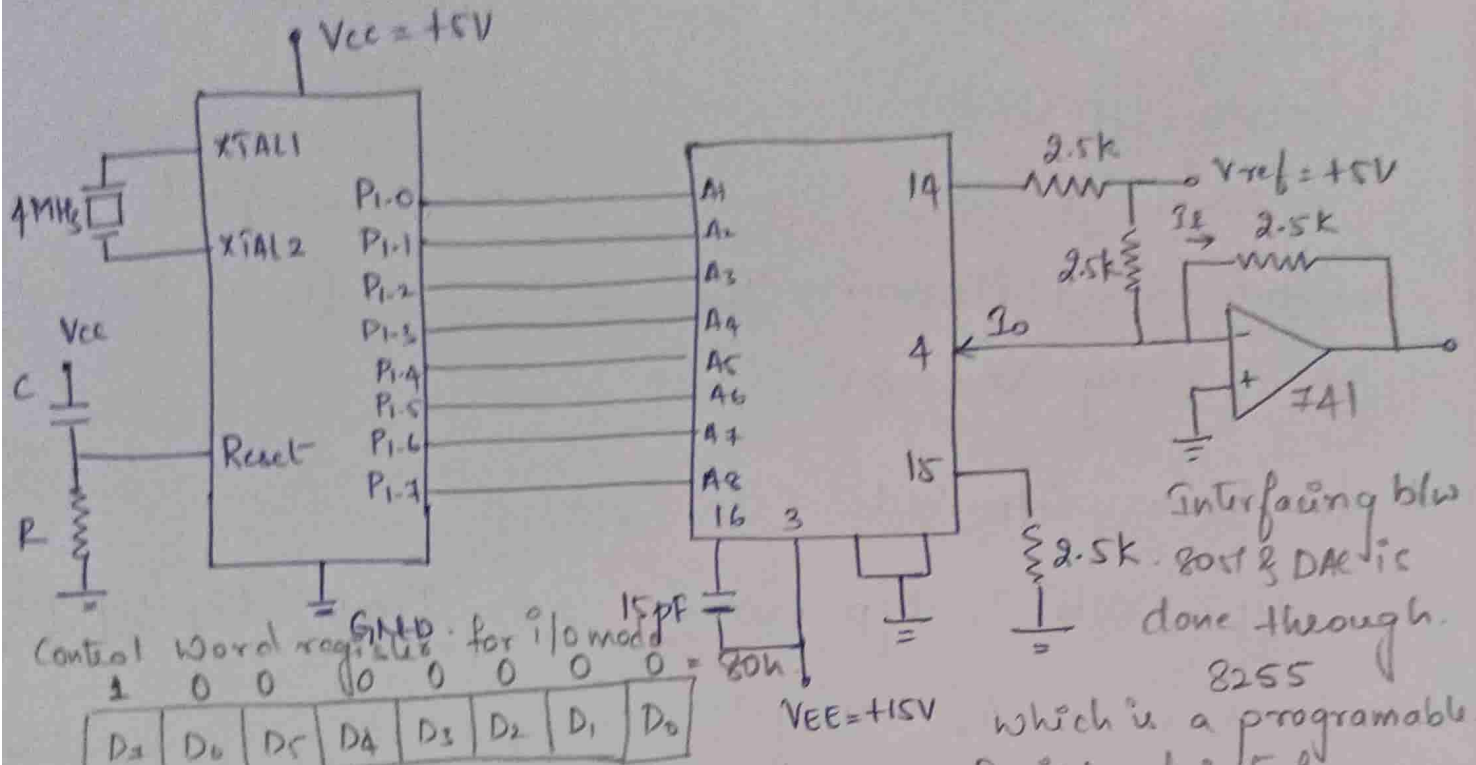I.e 1408/0808 converts digital data into eq<sup>n</sup> analog current.



Control Word register for i/o mode

1	0	0	0	0	0	0	0
D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
PA	PCu	GB	PB	PCl			

1. Square Wave generation

To generate square wave we have to load 00h on port 1.

Program: Org 00h

```
Repeat: MOV P1, #0FFh ;
        hcall Delay.
        MOV P1, #00h ;
        hcall Delay.
        ljmp Repeat ;
```

```
Delay: MOV Ro, #0FFh ;
Back:  DJNZ Ro, Back ;
        RET.
```

- D<sub>7</sub> = 1 for i/o mode
- D<sub>6</sub> & D<sub>5</sub> = 00 mode 1 = Simple i/o
- 01 - mode 2
- 1x - mode 3
- PA - 1 i/p, 0 - o/p
- Port C upper (PCu) } 1 - i/p
- Port C lower (PCl) } 0 - o/p
- Group B mode selector
- PB - 1 i/p, 0 - o/p
- PA = 0 we do not accept i/p we just sent data to convert
- load all 1's in port 1
- load all 0's in port 1
- Repeat data to convert
- load delay count
- Decrement & check whether delay count is zero if not repeat the operation.

2. triangular wave:-

- 1 o/p data = 00h then increment to FFh
2. when reached FFh then decrement to 00h.



Program:-

13

Org 00h.

MOV R0, #00h.

back: MOV P<sub>1</sub>, R0 ; Send digital data to i/p of DAC

INC R0 ; increment digital data

CJNE P<sub>1</sub>, #0FFh, back ; check for peak value

next: MOV P<sub>1</sub>, R0 ; Send Peak value to P<sub>1</sub>

DJNZ R0, next ; Decrement digital data

SJMP back ; jump to repeat the same

End.

\* Sine Wave generation:-

- To generate sine wave we have to o/p digital equivalent values which represents a wave [Sine]

- Digital data 00h represents -2.5V, 80h represents 0V and FFh represents +2.5V.

- digital equivalent for is calculated as shown.

$$\sin 0 = 0 \quad \sin 90 = 1.$$

∴ the range  $\sin 0$  to  $\sin 90$  is distributed over the digital range 80h to FFh.  $(80 + FF) = 127$  decimal steps.

∴ Digital equivalent for  $\sin x = (128 + 128 \times \sin x)$

where  $x$  is the angle in degrees.

$$\sin 0 = 128 + 128 \times \sin 0 = 128 = 80h$$

$$\sin 10 = 128 + 128 \times \sin 10 = 150 = 96h$$

$$\sin 90 = 128 + 128 \times \sin 90 = 256 \rightarrow 255 = FFh.$$

$$\sin 180 = 128 - 80h, \quad \sin 270 = 0 = 0h, \quad \sin 360 = 128 = 80h.$$

Program:-

~~CLR A~~

again: MOV DPTR, #Sine ; Initialize the pointer to lookuptable.  
MOV R0, #24 ; Counter

Begin: CLR A  
MOVC A, @ANDPTR ; data from lookuptable to A

MOV P1, A ; Move it to port 1.

INC DPTR ; point to next lookuptable entry.

DJNZ R0, Begin ; Decrement counter & repeat.


Sjmp again ; Repeat entire process.

Sine: DB, 128, 150, 192, 217, 237, 250, 255, 250,  
237, 217, 192, 150, 128, 94, 63, 37,  
17, 4, 0, 4, 17, 37, 63, 94, 128, 0

End.
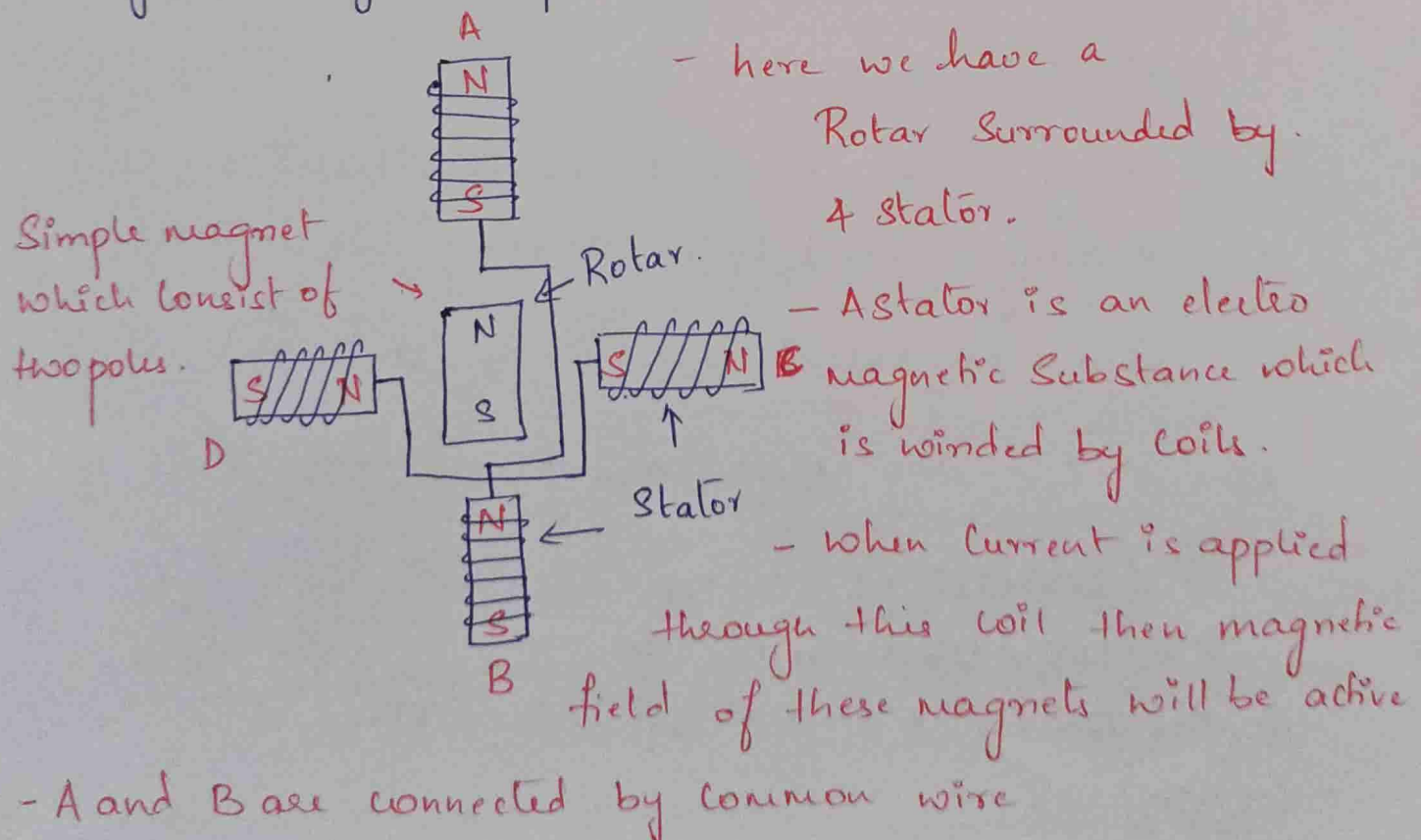
### \* Stepper motor interface :-

Stepper motor is a digital motor driven by digital signal. A typical 2 phase motor is as shown below.



- C and D connected by common wire.
- when current is applied through A then magnetic field of Both A and B will be activated.
- when current is applied through B then the direction of current changes and hence polarity of magnets will be reversed.

1. full step sequence.

- we have 4 stators A, B, C, D.
- In full step sequence we perform
- 4 steps to complete 1 rotation which means in each step the rotor rotates by 90° angle.
- Initially we assume current is flowing through A and C.



A	B	C	D	
1	0	1	0	0A
0	1	1	0	0B
0	1	0	1	0C
1	0	0	1	0D

$A=1, B=0, C=1, D=0$

∴ the N pole of rotor will be equally attracted by the S pole of A and C.

the S pole of rotor will be equally attracted by the N pole of B and D.



∴ the position will be

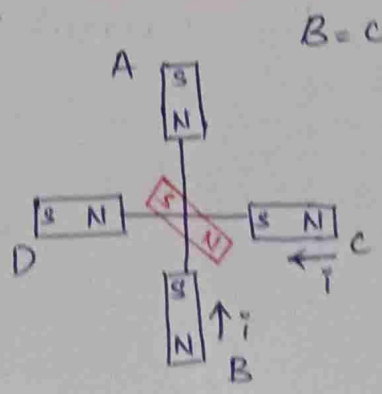 

Current applied through B  
∴ polarities change

$$B = D = 1$$

$$A = D = 1$$

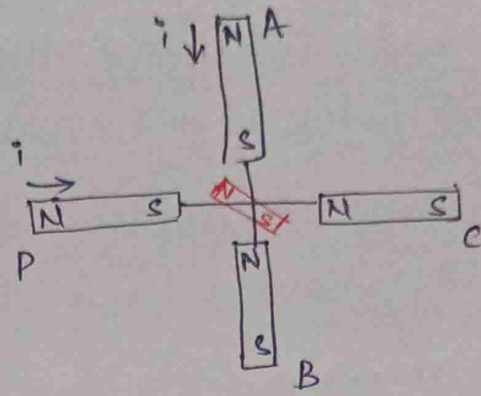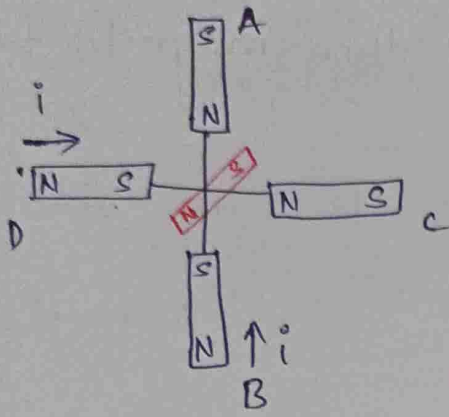

∴ rotor has completed 1 rotation

- half step sequence then 8 steps to complete 1 complete rotation and rotor rotates with an angle of  $45^\circ$

A	B	C	D
1	0	1	0
0	0	1	0
0	1	1	0
0	1	0	0
0	1	0	1
0	0	0	1
1	0	0	1
1	0	0	0

0A → A and C = ON supply current

02 → A & B = inactive hence rotor will be horizontally placed as it is  
04 → CSP attracted only by C and D.

05

01 → AB inactive

09

08 → C & D inactive.

- If we observe the rotor rotates in clock wise direction in case we want it to rotate anticlock wise apply the current in reverse order.

Q.1. Write an 8085 ALP program to control stepper motor (5)

~~Org 00h~~

~~Jmp 100h~~

~~Org 100h~~

~~MOV DPTR, #110h ; DPTR with memory location 100h~~

~~MOV A, #0Ah~~

~~MOVX @DPTR, A~~

~~MOV P1, DPTR~~

Solution: MOV R0, #Count ; initialize the rotation count

Again: MOV DPTR, #Data ; point to the data in lookup table

~~Back~~: MOV R1, #04 ; counter to get data from lookup table

Back: MOVX A, @DPTR ; get the data from code

MOV P1, A ; send the data to the port

LCALL Delay ; given delay to observe the slow rotation

INC DPTR ; increment the pointer

DJNZ R1, Back ; R1 ≠ 0, jump to back

DJNZ R0, Again ; R0 ≠ 0, jump to Again

SJMP \$ ; looped jumping ; SJMP here


Data: DB 0Ah, 06h, 05h, 09h, 0 ; code sequence for clock wise rotation

\* DC motor interfacing:-


- DC motor → Direct current motor which rotates continuously.

- It has two terminals +ve & -ve.

- Connecting DC power supply to these terminals rotate motor in one direction and on reversing the polarity of the power supply reverses the direction of rotation
- Speed is measured in rotation per minute (RPM).
- Speed increases with increase in the supply voltage.
- Speed of DC motor depends on the load
  - At no load speed is high.
  - As load  $\uparrow$  speed  $\downarrow$
  - Overloading will damage DC motor because of the excess heat produced by the load.

 


Clock wise rotation

 

anticlockwise.

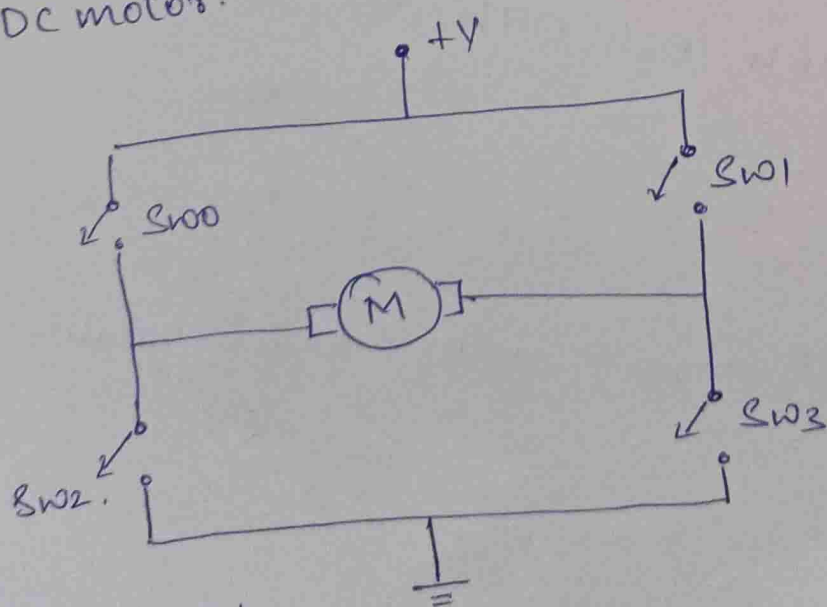By using switches for changing the power supply we can control the direction of rotation of the DC motor.



Bidirectional

When all the switches are off motor does not run.

SW3	SW2	SW1	SW0	
ON	OFF	OFF	ON	clock
OFF	ON	ON	OFF	anti clock

Write an ALP to control the direction of the DC motor according to the status of bit P1.0. Assume the port pin P2.0, P2.1, P2.2 and P2.3 control the switches SW0, SW1, SW2, SW3 respectively. (16)

```
Org 00h.  
CLR P2.0  
CLR P2.1  
CLR P2.2  
CLR P2.3  
SetB P1.0
```

} make all switches OFF

check: JNB P1.0, clockwise.; jump if P1.0 ≠ 1

```
CLR P2.0 ; SW0 = OFF  
SETB P2.1 ; SW1 = ON  
SETB P2.2 ; SW2 = ON  
CLR P2.3 ; SW3 = OFF
```

Sjmp check.


```
clockwise: SetB P2.0 ; SW0 = ON  
CLR P2.1 ; SW1 = OFF  
CLR P2.2 ; SW2 = OFF  
SetB P2.3 ; SW3 = ON
```

Sjmp check.

End.

\* Temperature sensor [LM35]:-

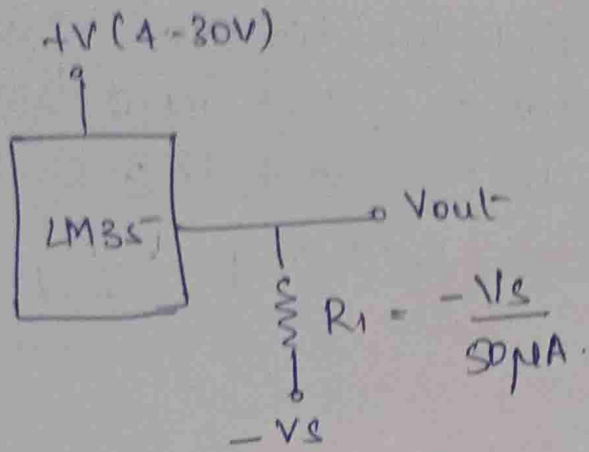
LM35 is a temperature sensitive voltage source. Its o/p voltage increases by 10mV for each  $^{\circ}\text{C}$   $\uparrow$  in temperature.



- o/p voltage is connected to a -ve reference voltage.  
this sensor will get a meaningful o/p for a temperature range of  $-55^{\circ}\text{C}$  to  $150^{\circ}\text{C}$
- o/p is adjusted to 0V for  $0^{\circ}\text{C}$ .
- o/p voltage from LM35 is applied to ADC to get digital equivalent of analog voltage.

\* ADS90 - temperature sensitive current source.

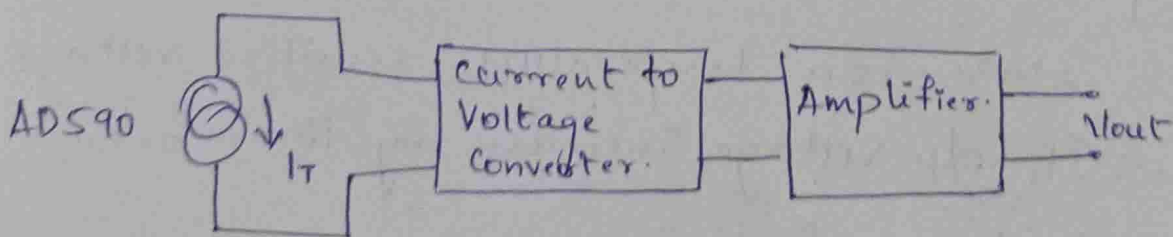- It produce a current of  $1\mu\text{A}/^{\circ}\text{K}$ .
- this can be converted to voltage by using a current to voltage converter.
- Advantage is voltage drop in long connecting wire doesnot effect the o/p value.



the o/p of amplifier is applied to ADC to get digital equivalent of current temp.